



Electromagnetic Compatibility (*EMC*)

Basic knowledge used in EMC





Agenda

- *Circuit Analysis*
 - Use of Network Theory
 - Capacitor Coupling
 - Inductor Coupling
 - Discrimination
- Practical Model of Component and Frequency Response
- Common mode and Differential mode
- Near Field and Far Field
- Antenna Effect
- Transmission Line Analysis





Use of Network Theory

- Circuit analysis assumes the following
 - All *electric fields* are confined to the interiors of *capacitors*.
 - All *magnetic fields* are confined to the interiors of *inductors*.
 - Dimensions of the circuits are very small compared to the wavelength under consideration.





Capacitor Coupling



■ Noise voltage :
$$V_N = \frac{j\omega[C_{12}/(C_{12} + C_2)]}{j\omega + 1/R_L(C_{12} + C_2)} \cdot V_S$$

for $R_L \ll \frac{1}{j\omega(C_{12} + C_2)}$

$$V_N = j\omega R_L C_{12} V_S$$

- Assuming the voltage and frequency of the noise source cannot be changed

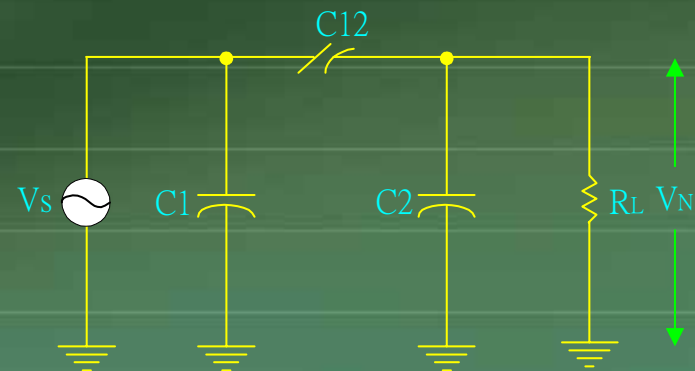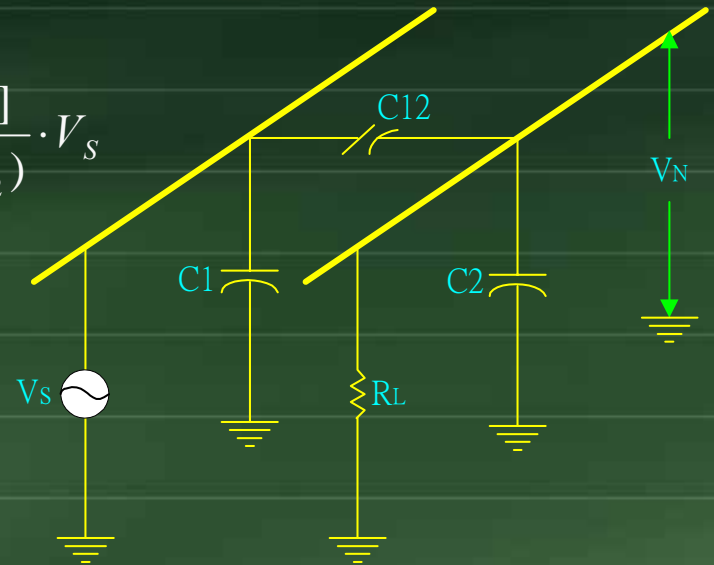- *Decreasing capacitance C_{12}*
- Let receiver circuit operate at a lower resistance level R_L






Capacitor Coupling

□ Noise voltage : $V_N = \frac{j\omega[C_{12}/(C_{12} + C_2)]}{j\omega + 1/R(C_{12} + C_2)} \cdot V_S$

for $R_L \gg \frac{1}{j\omega(C_1 + C_2)}$
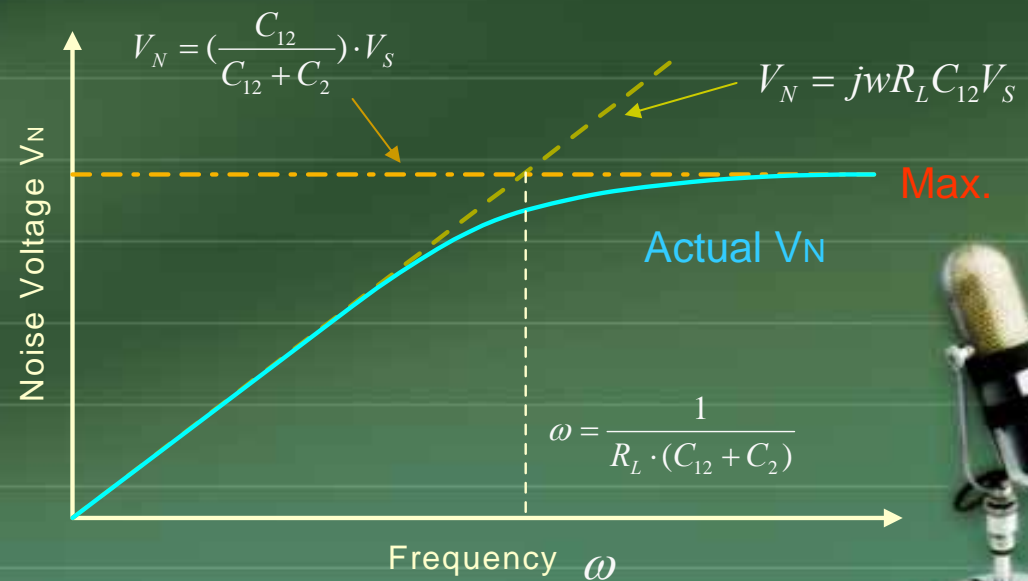
$$V_N = V_{N(\max)} = \left(\frac{C_{12}}{C_{12} + C_2} \right) \cdot V_S$$






Capacitor Coupling With Shielding

■ Noise voltage :
$$V_N = \left(\frac{C_{12}}{C_{12} + C_{2G} + C_{2S}} \right) \cdot V_S$$

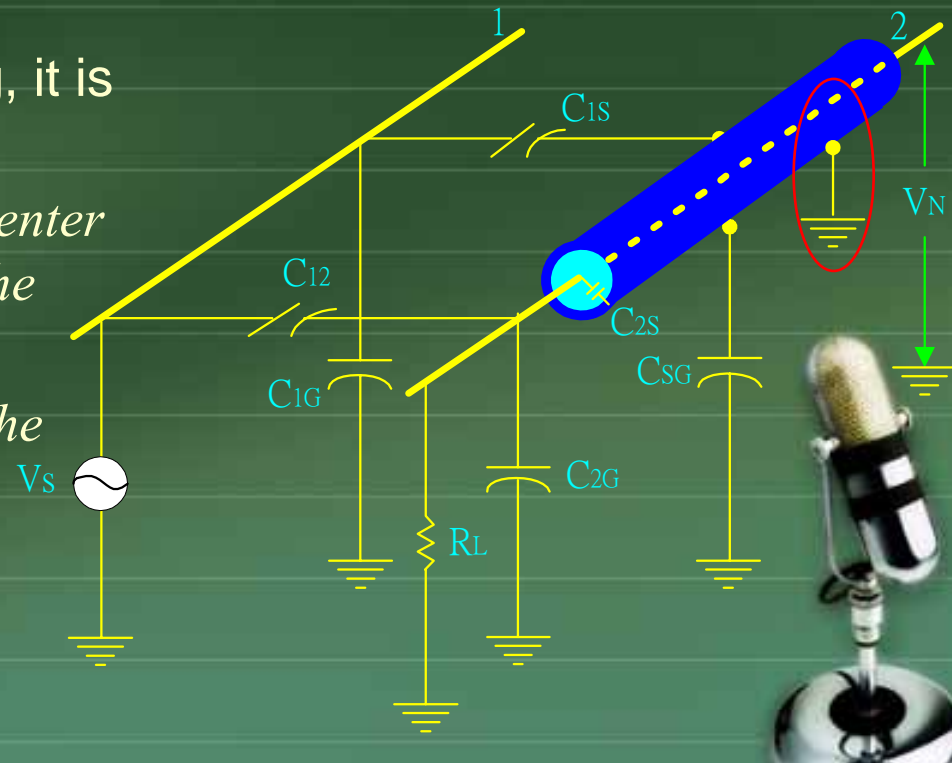- C_{12} depends on the length of conductor 2 that extends beyond the shield.
- For good electric field shielding, it is therefore necessary
 - *to minimize the length of the center conductor extending beyond the shield.*
 - *to provide a good ground on the shield.*






Inductor Coupling

■ Noise voltage : $V_N = j\omega BA \cos \theta = j\omega M_{12} \cdot I$

- \vec{B} is the rms value of the sinusoidally varying flux density produced by current I in circuit 1.
- \vec{A} is the area of closed loop in circuit 2.
- M_{12} is the mutual inductance between conductor 1 and 2.


Strategies

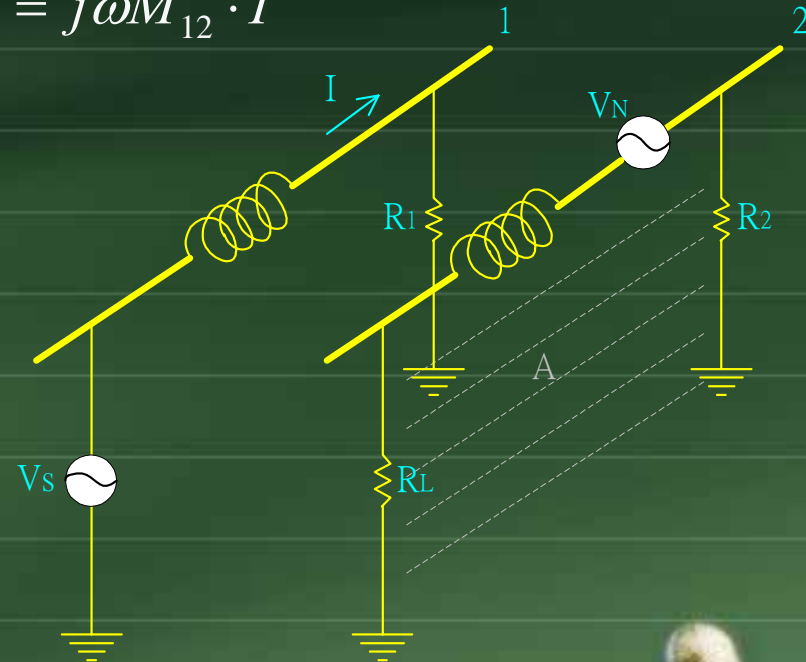- Decreasing loop area \vec{A}
 - Twisted line, proper grounding, shielding ...
- Decreasing flux density \vec{B} or mutual inductance M_{12}
 - Physical separation of the circuits, current flowing in the twisted pair...






Cable Shield Grounding

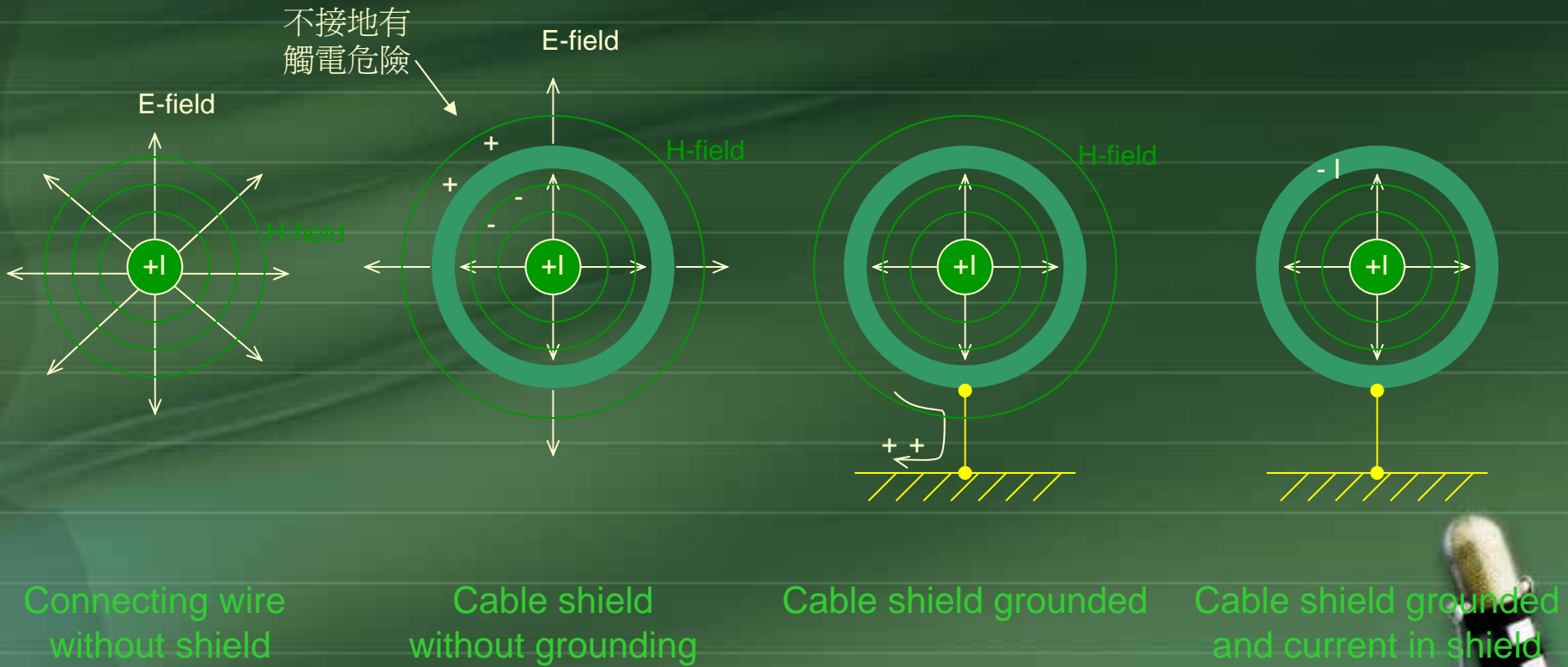




Discrimination

Electric coupling

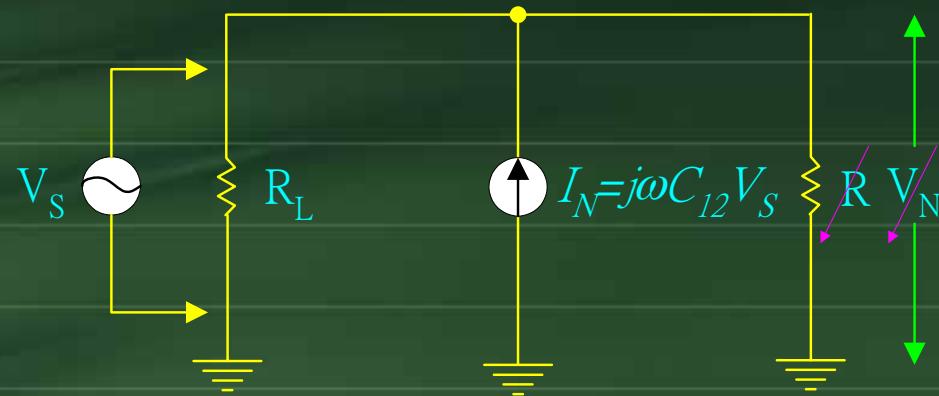

Magnetic coupling

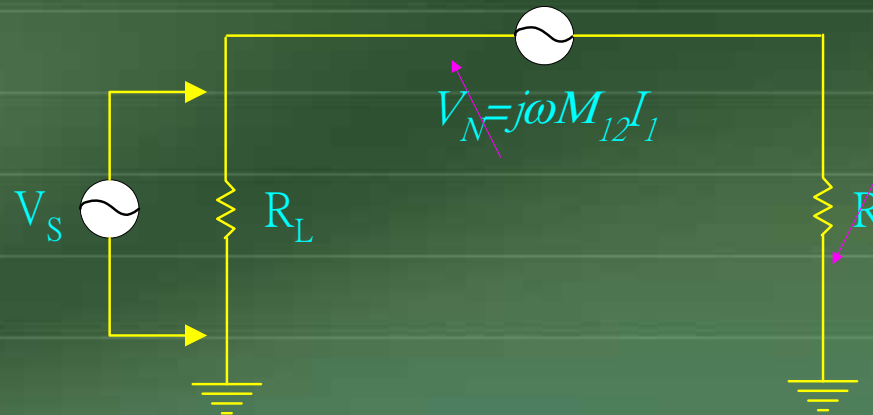



Agenda

- Circuit Analysis
- *Practical Model of Component and Frequency Response*
 - Capacitor
 - Inductor
- Common mode and Differential mode
- Near Field and Far Field
- Antenna Effect
- Transmission Line Analysis









Practical Model of Component

Capacitor

Measurement setup

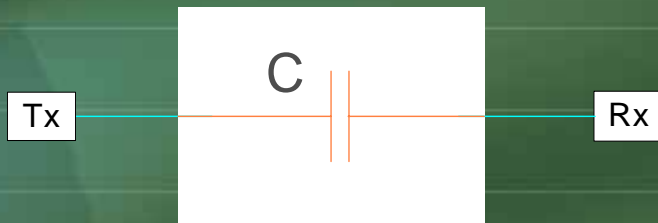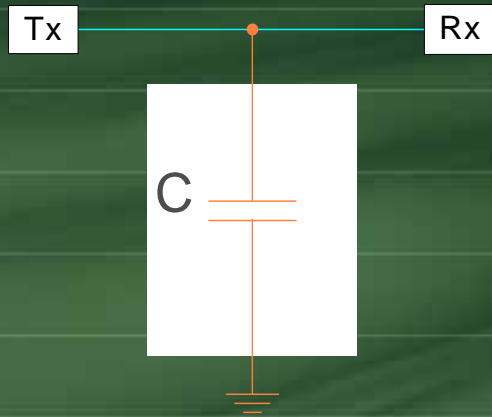

Practical Capacitor

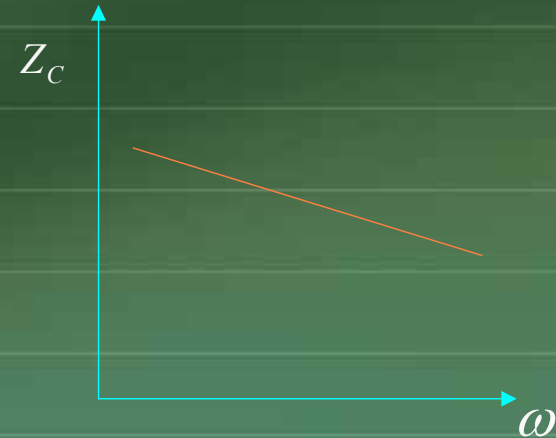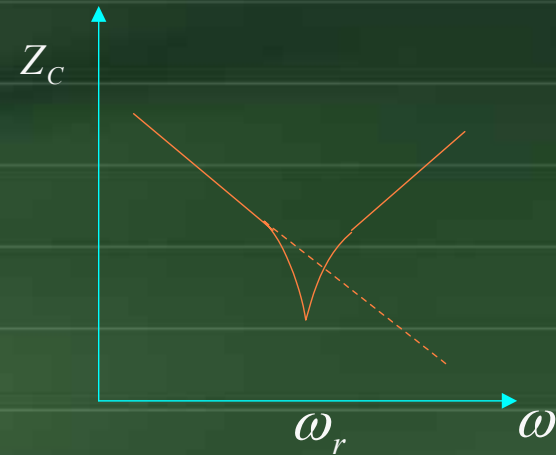




Practical Model of Component


Capacitor

Ideal Capacitor

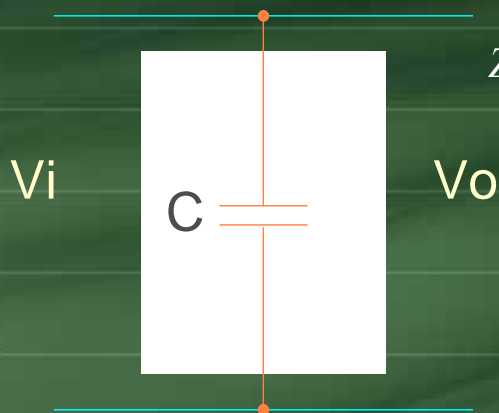


$$Z_C = \frac{1}{j\omega C}$$




Impedance

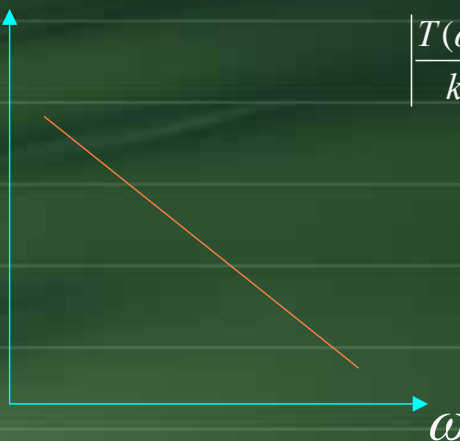

Transfer Function

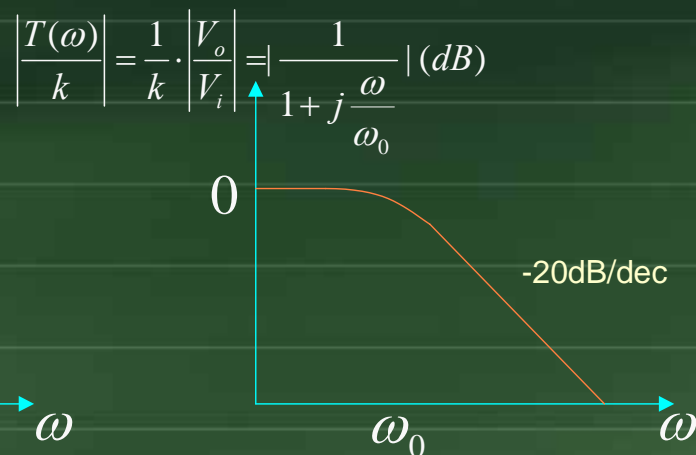


Practical Capacitor

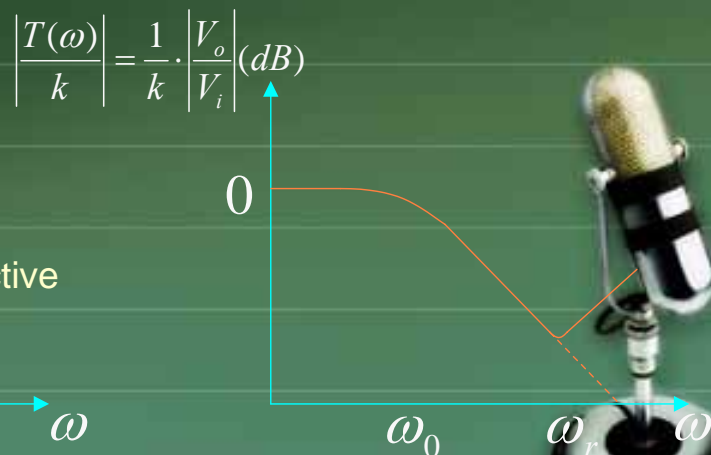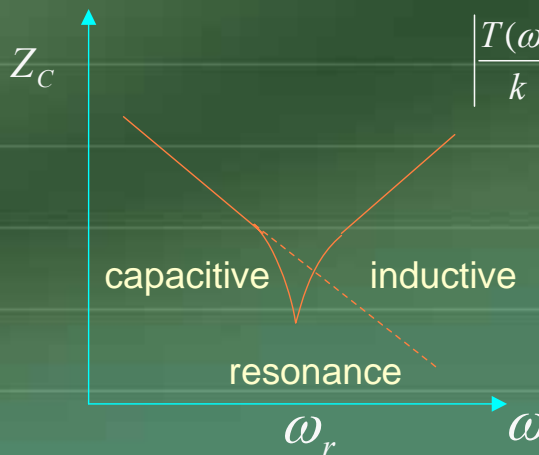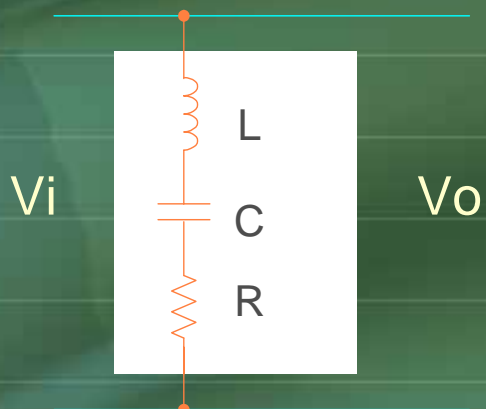



Practical Model of Component Capacitor

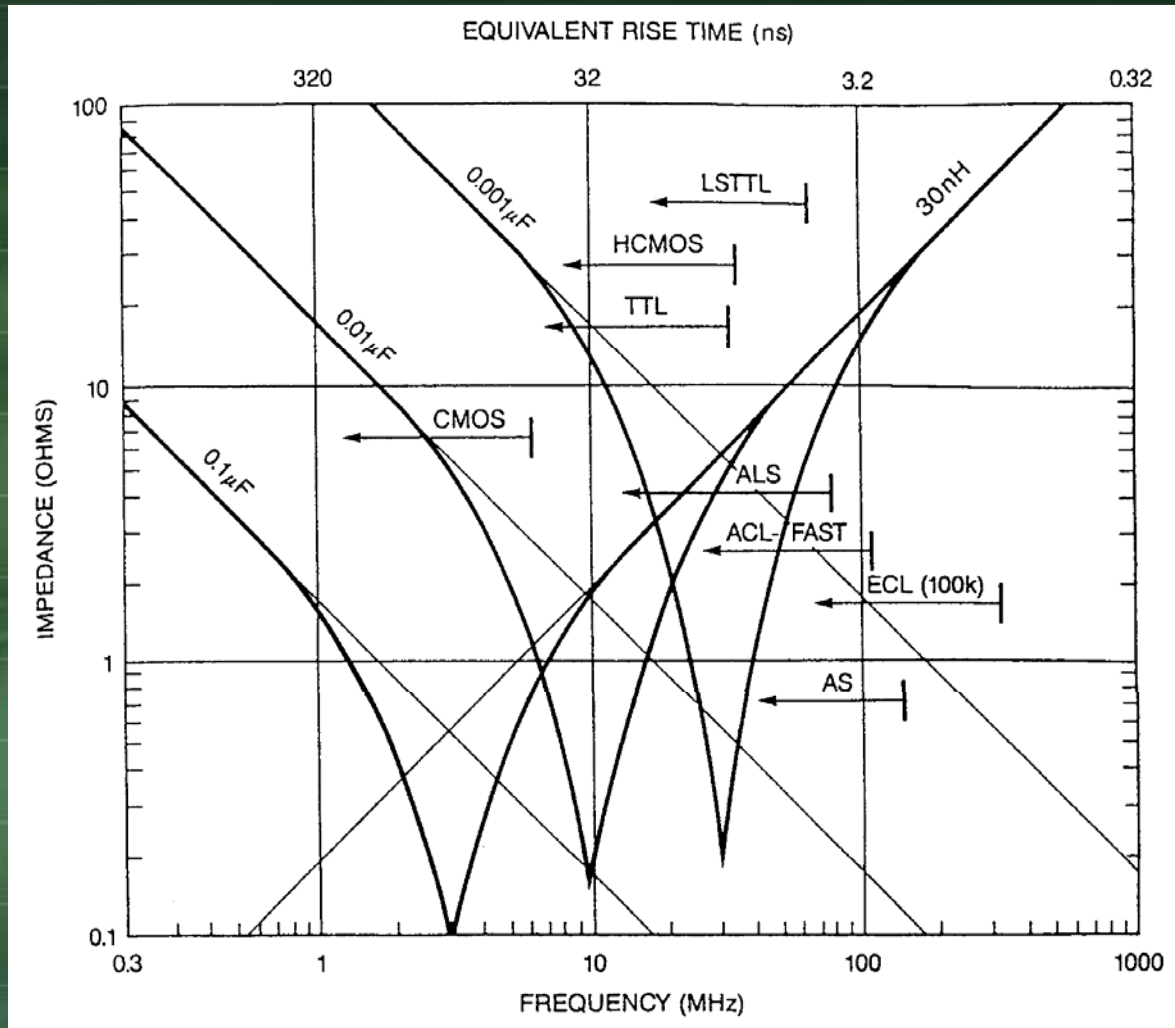

Impedance of various value decoupling capacitors in series with 30nH of inductance





Practical Model of Component

Capacitor

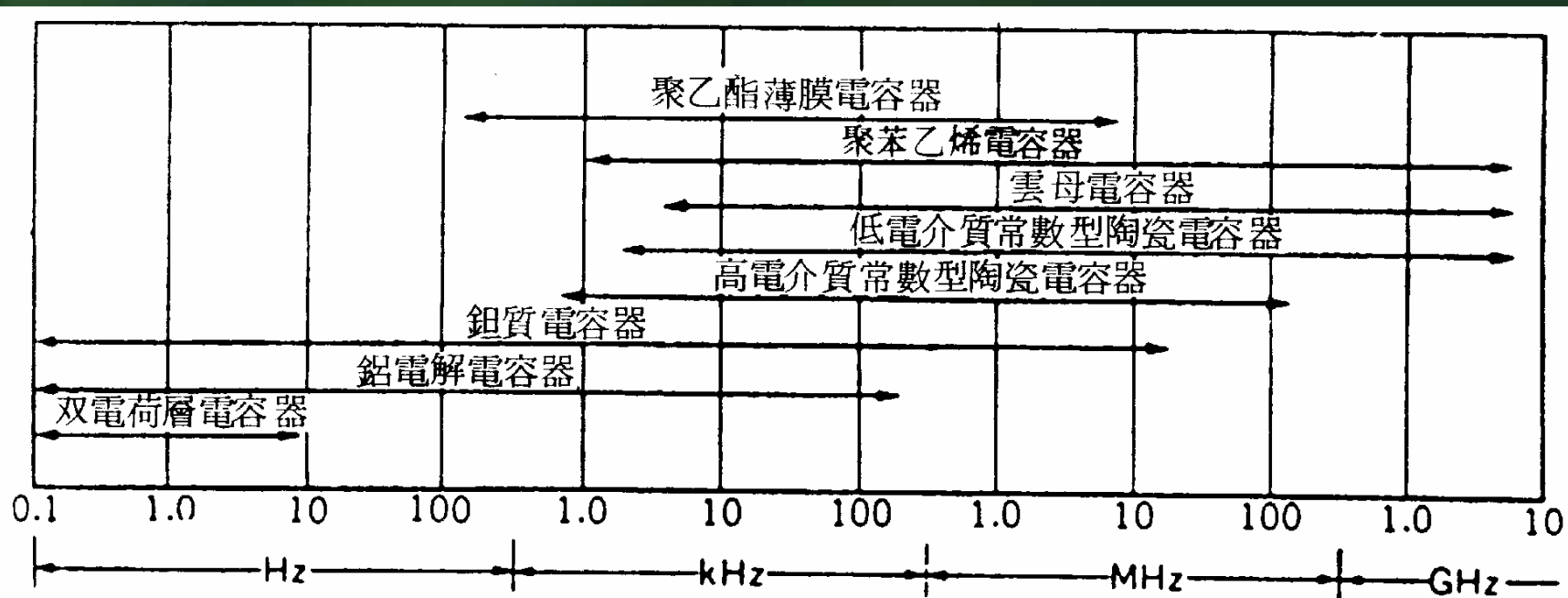


圖 3-5 主要電容器的頻率特性



Practical Model of Component Capacitor

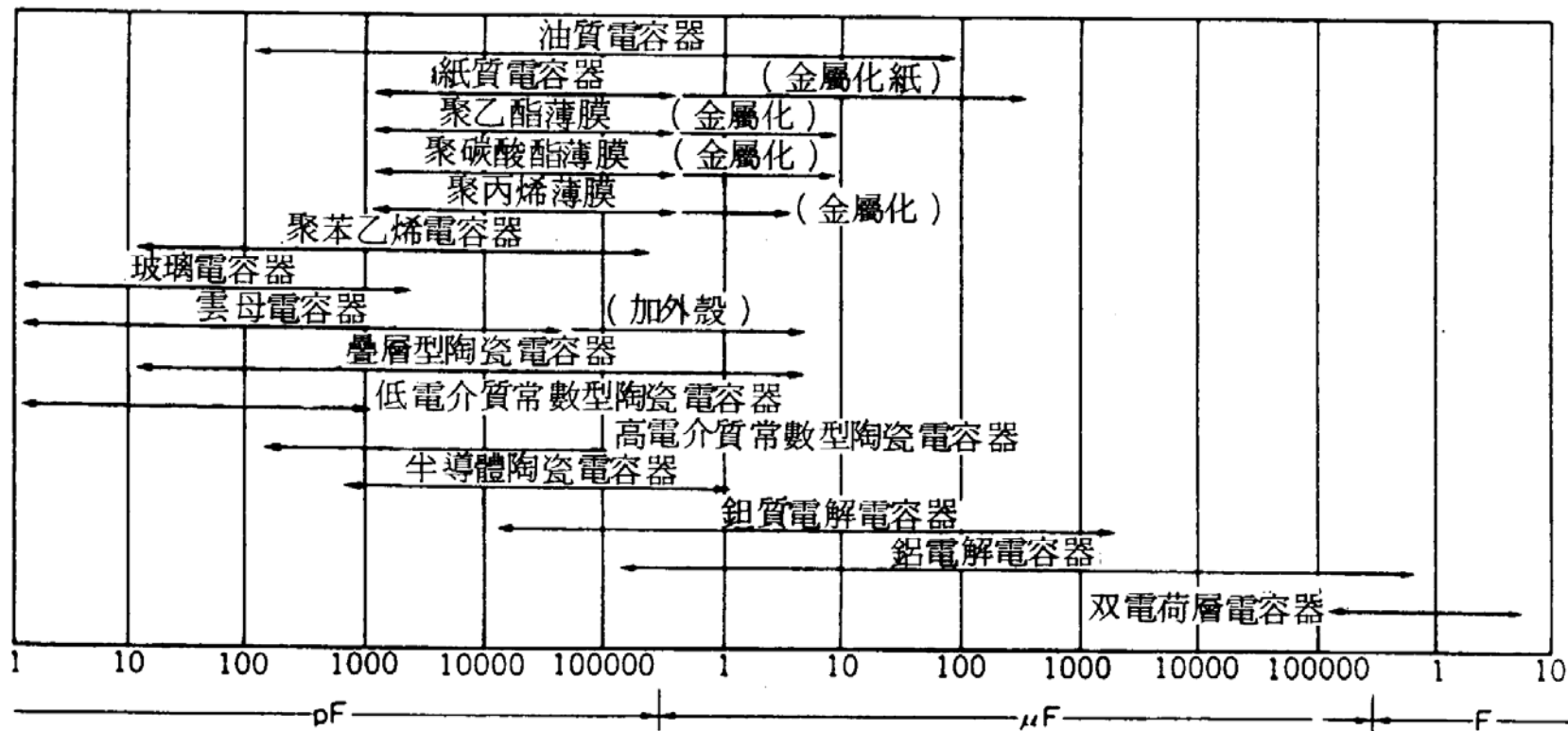


圖 3-6 各種電容器的靜電容量




Practical Model of Component

Inductor


Ideal Inductor






Impedance

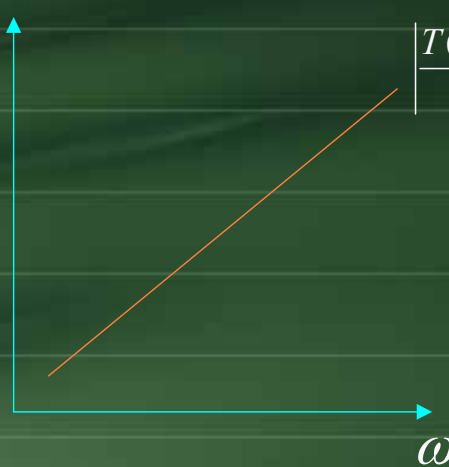

Transfer Function

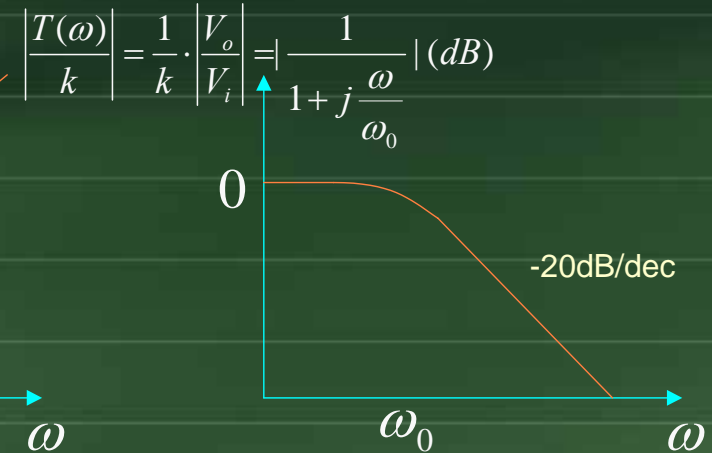

Practical Inductor

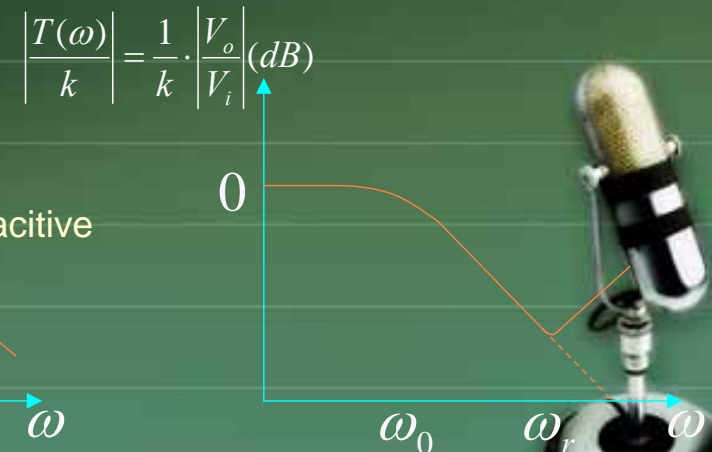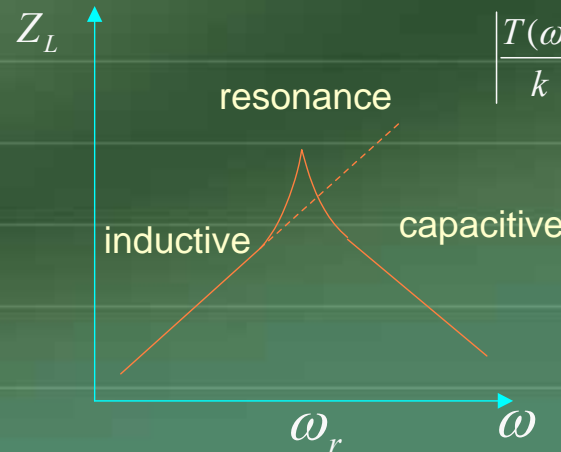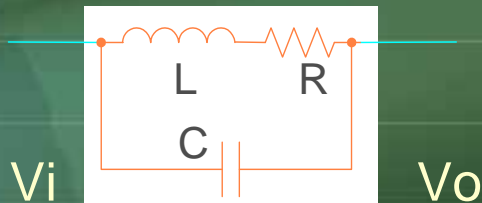



Agenda

- Circuit Analysis
- Practical Model of Component and Frequency Response
 - Capacitor
 - Inductor
- *Common mode and Differential mode*
- Near Field and Far Field
- Antenna Effect
- Transmission Line Analysis





Common Mode and Differential Mode


- Common-Mode(CM) – Balance Circuit
 - Cause of ground impedance in design or measurement system
- Differential-Mode(DM) – Unbalance Circuit
 - Cause of internal circuit operation or unbalance

V_{PG} : Voltage between phase and ground

V_{NG} : Voltage between neutral and ground


CM : $V_C = (V_{PG} + V_{NG}) / 2$

DM : $V_D = (V_{PG} - V_{NG}) / 2$

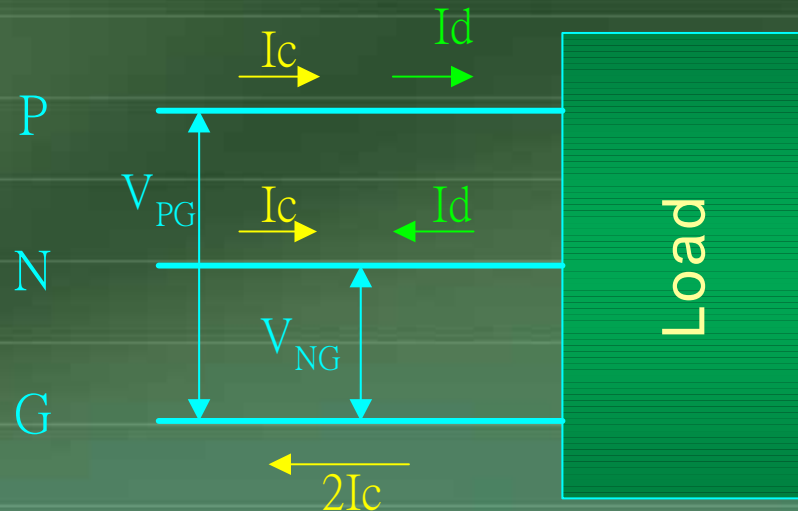




Common Mode and Differential Mode

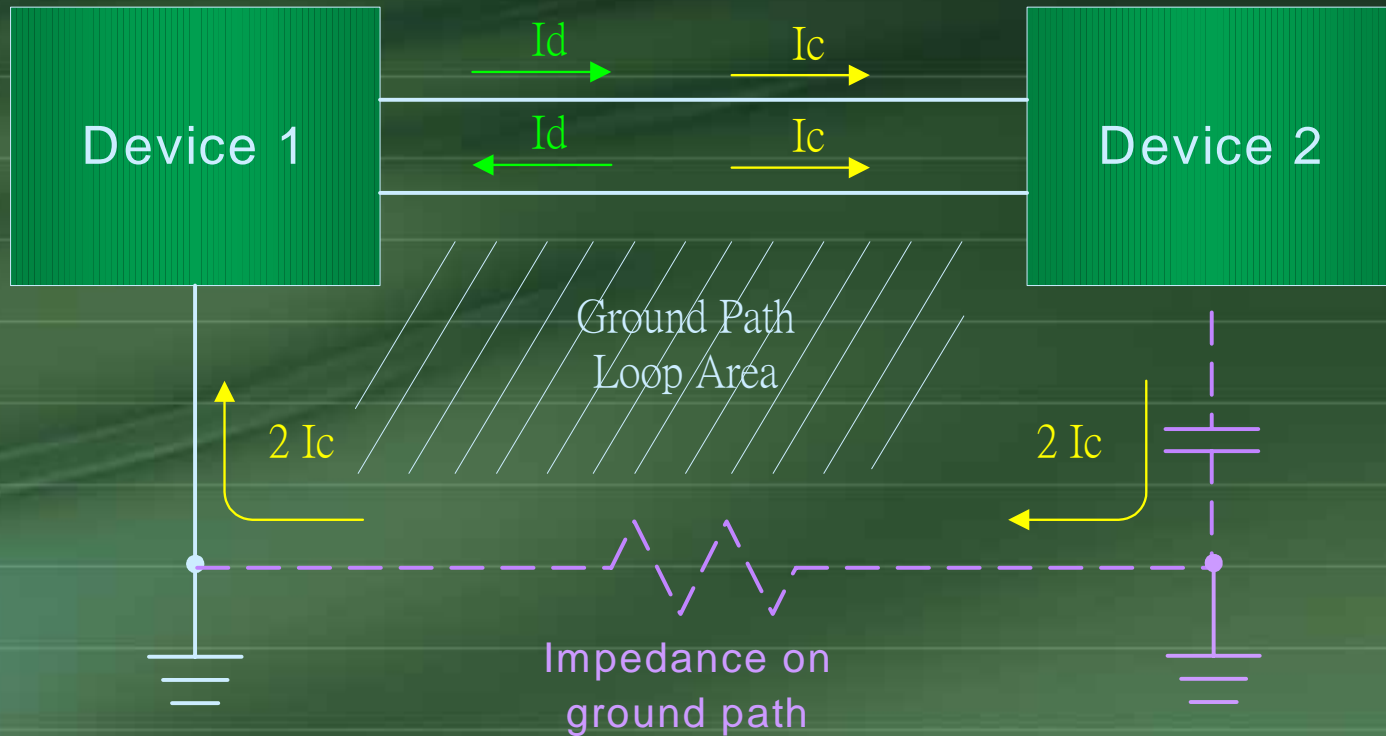



Balanced Circuitry

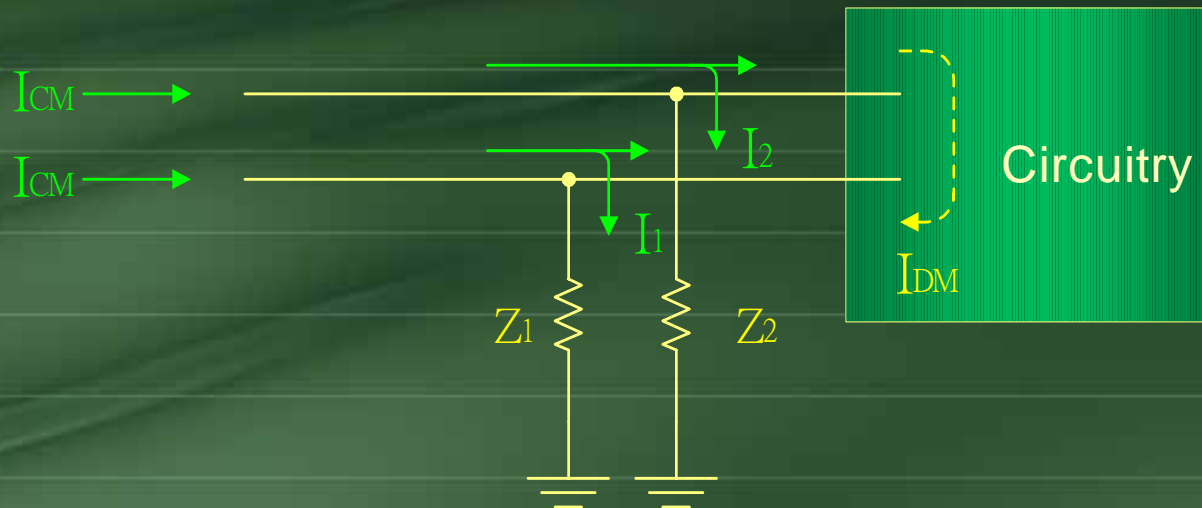


- If $Z_1 = Z_2$ then $I_1 = I_2$ and $I_{DM} = 0$.
 - No DM current flows into the circuitry.
- If $Z_1 \neq Z_2$ then $I_1 \neq I_2$ and $I_{DM} \neq 0$.
 - There is DM current flows into the circuitry, which is transferred from CM.





Balanced Circuitry

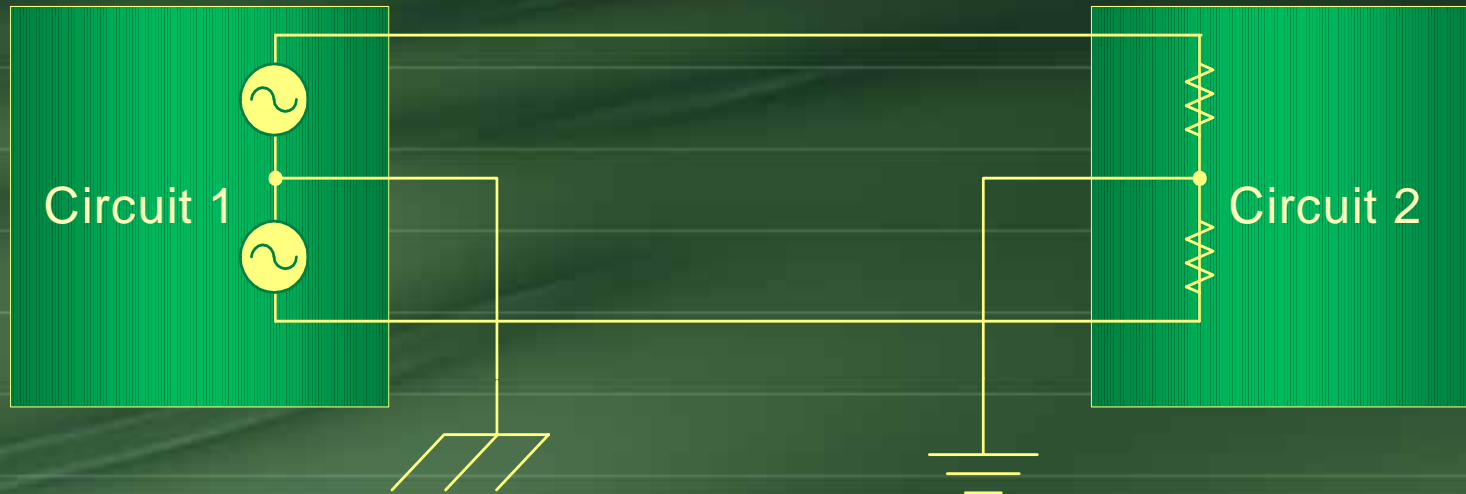


- The balanced receiver responds only to the difference between the two inputs.
- *The better the balance is, the larger the CM rejection is.*





Balanced Circuitry

Example -- Differential Amplifiers

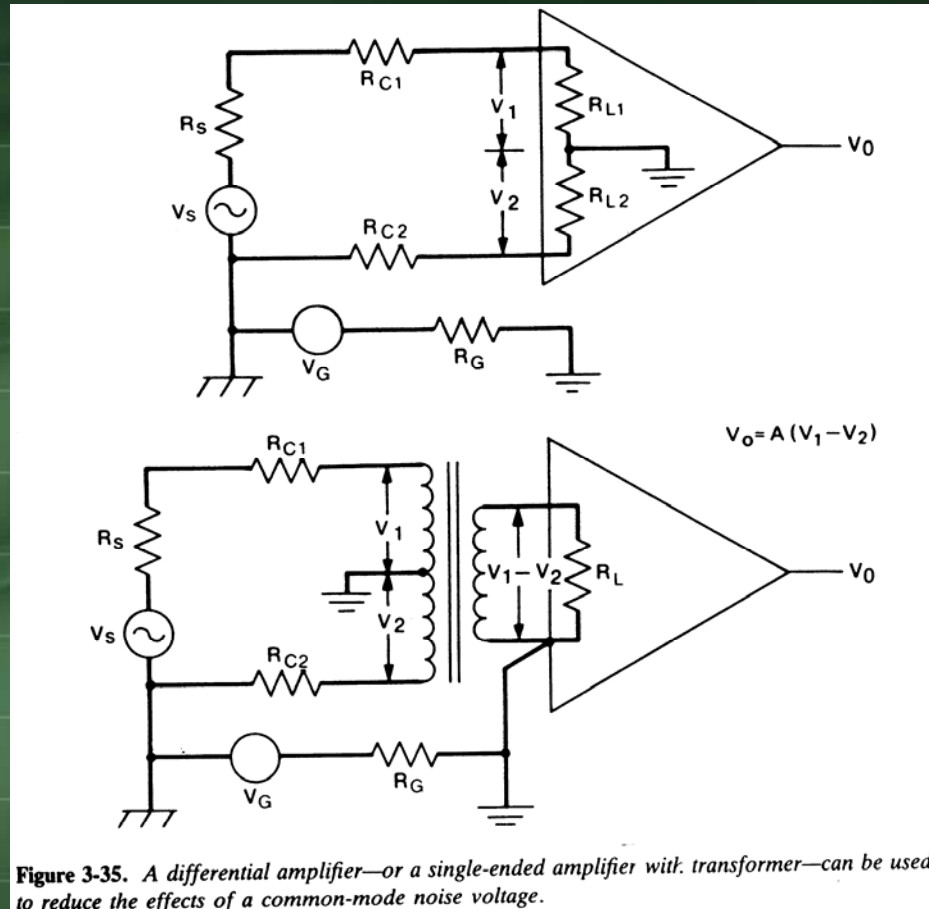


- A single-ended (or unbalanced) amplifier with transformer can be used to simulate the performance of a balanced amplifier.
- Using a transformer






CM / DM Example

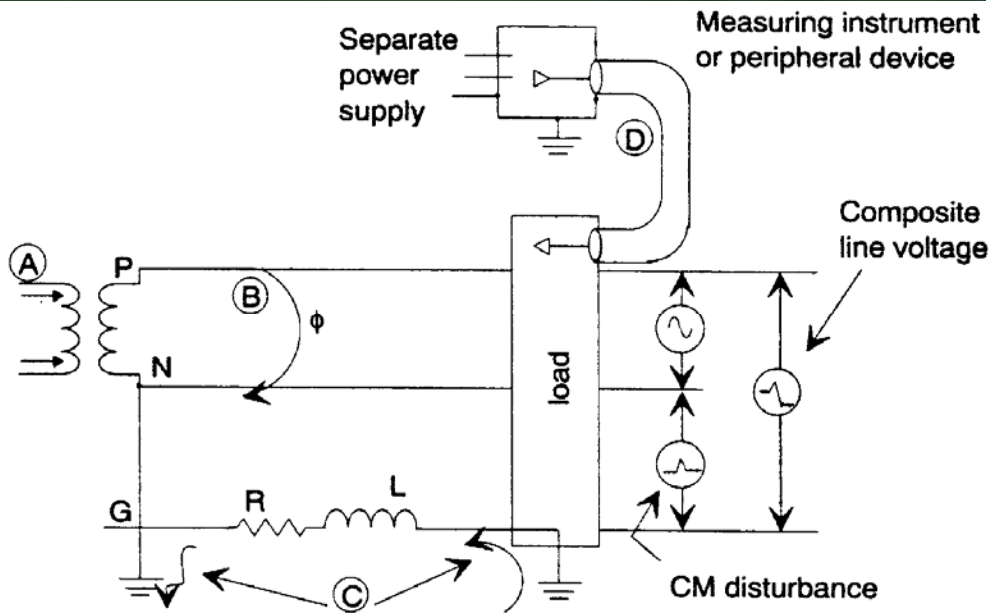

CM

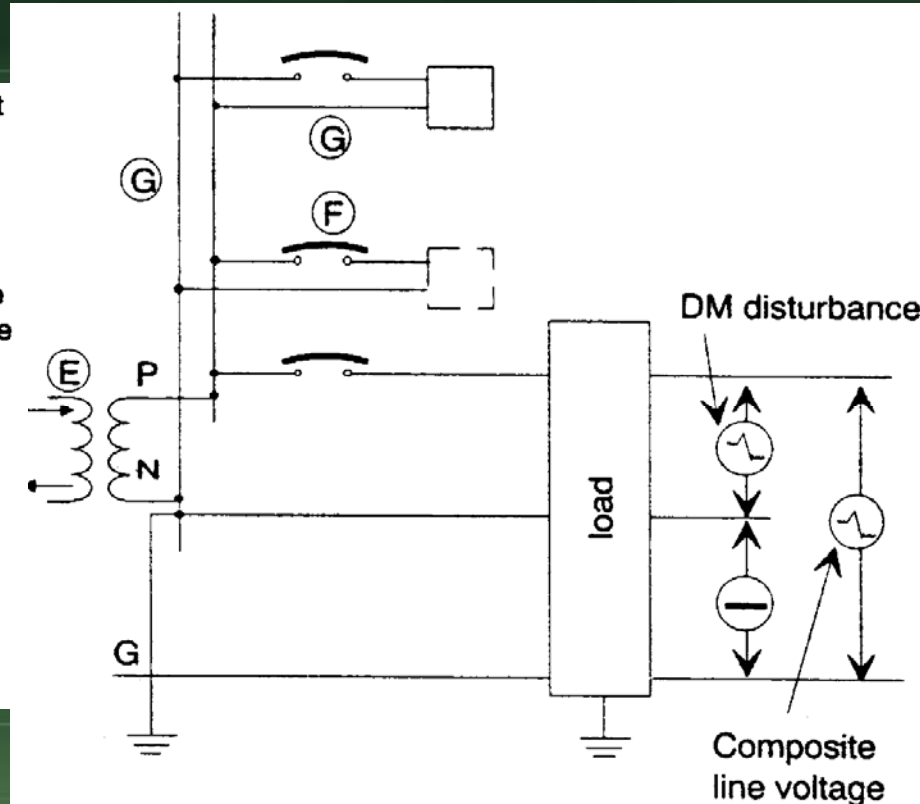

DM






CM / DM Radiation

CM radiation

- A low current and high voltage source, like a rod or straight antenna.
- 用電場探棒量

DM radiation

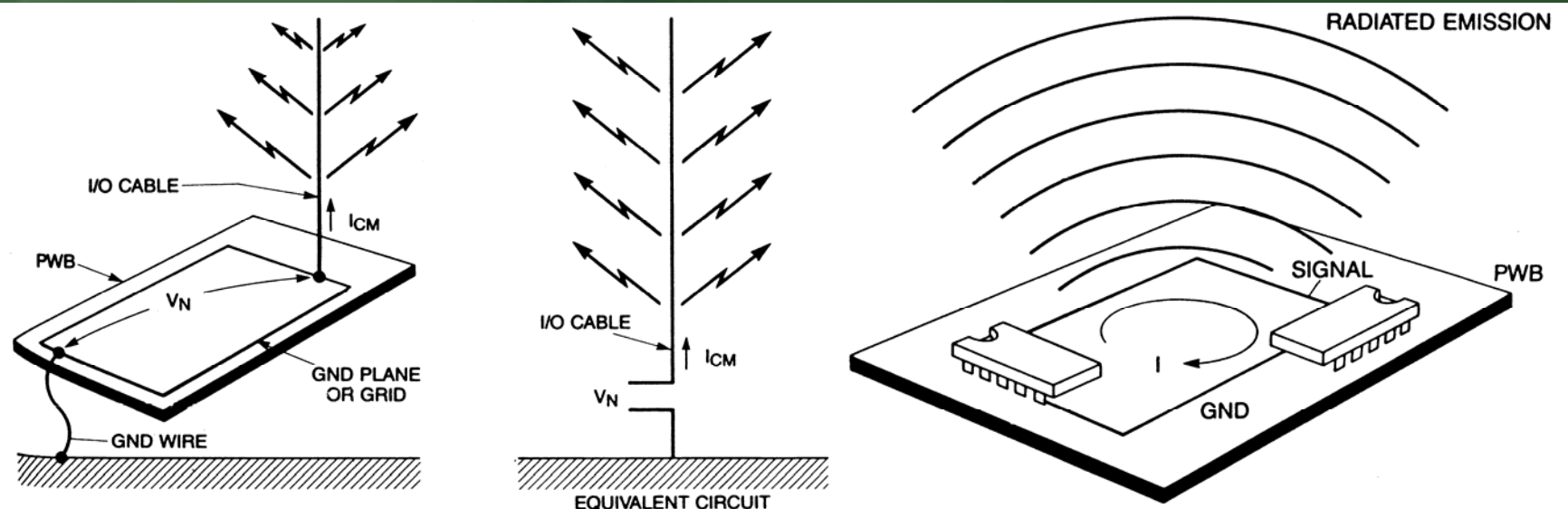- A high current and low voltage source, like a loop antenna.
- 用磁場探棒量





Agenda

- Circuit Analysis
- Practical Model of Component and Frequency Response
 - Capacitor
 - Inductor
- Common mode and Differential mode
- *Near Field and Far Field*
- Antenna Effect
- Transmission Line Analysis





Near Fields and Far Fields

□ *Wave Impedance* : $Z_w = \frac{|\vec{E}_t|}{|\vec{H}_t|} \Leftrightarrow R = \frac{V}{I}$

E-field SE(dB) = 20 log₁₀(E₁/E₂)
H-field SE(dB) = 20 log₁₀(H₁/H₂)








Near Fields and Far Fields

- Field characteristics are determined by the source, the media surrounding the source, and the distance between the source and the point observed.
- *Near (Induction) field*
 - *For a high current and low voltage source (like a loop antenna), the near field is predominantly magnetic.*
 - *For a low current and high voltage source (like a rod or straight antenna), the near field is predominantly electric.*
- *Far (Radiation) field*
 - *The wave impedance equals the characteristic impedance of the medium (e.g. 377Ω for air)*
 - *Magnetic and electric effects don't need to concern separately.*






Near Fields and Far Fields

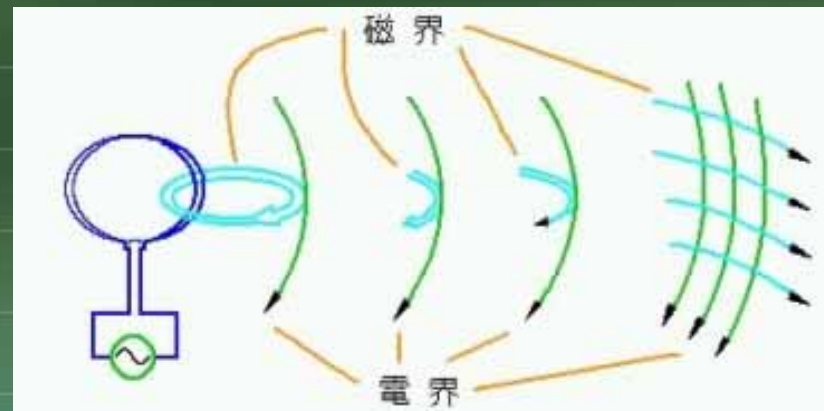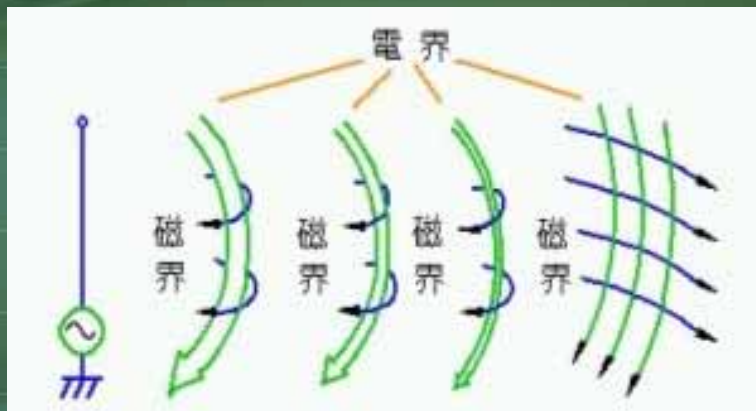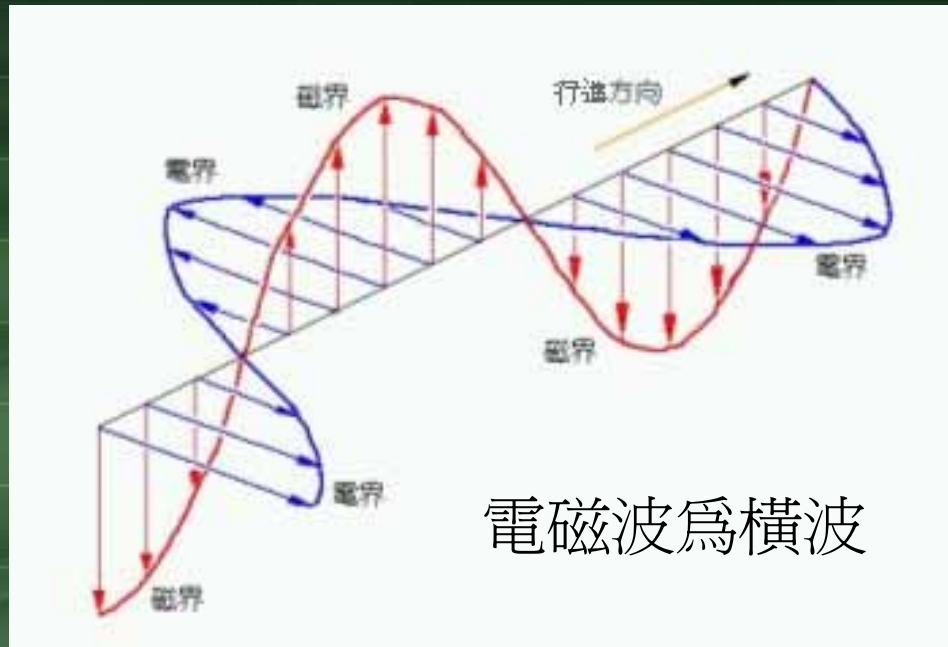



Near Fields and Far Fields

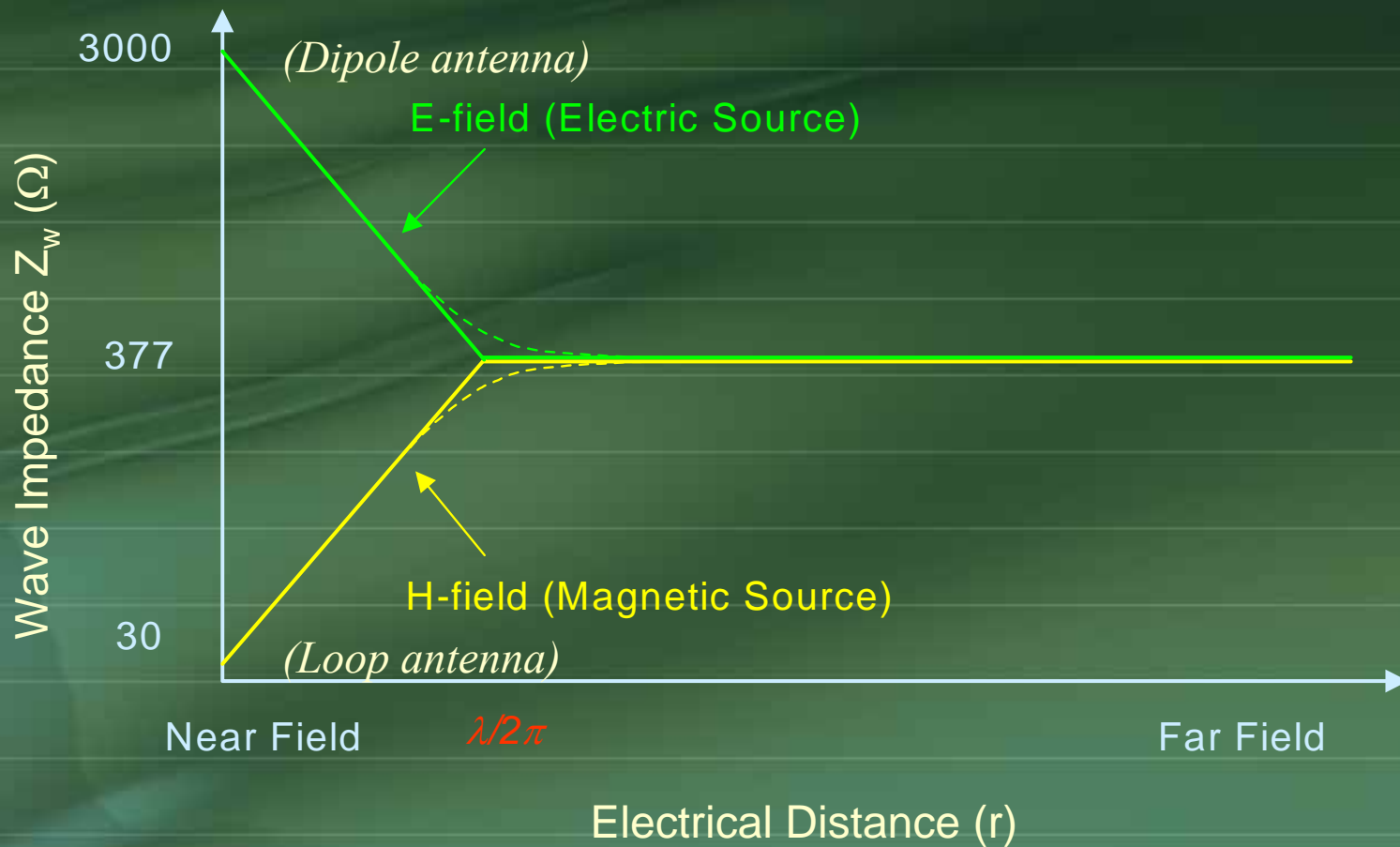



Agenda

- Circuit Analysis
- Practical Model of Component and Frequency Response
 - Capacitor
 - Inductor
- Common mode and Differential mode
- Near Field and Far Field
- *Antenna Effect*
- Transmission Line Analysis





Antenna Effect


- If the length of a cable is longer than $\lambda/4$ it can be seen as a good polar antenna.
- As cables approach a quarter-wavelength in length, some of the current in the cable is out of phase. When the cable is a half-wavelength long the out-of-phase currents will cause the external coupling to be zero due to **cancellation** of effects.





Antenna Effect

Coupling factor

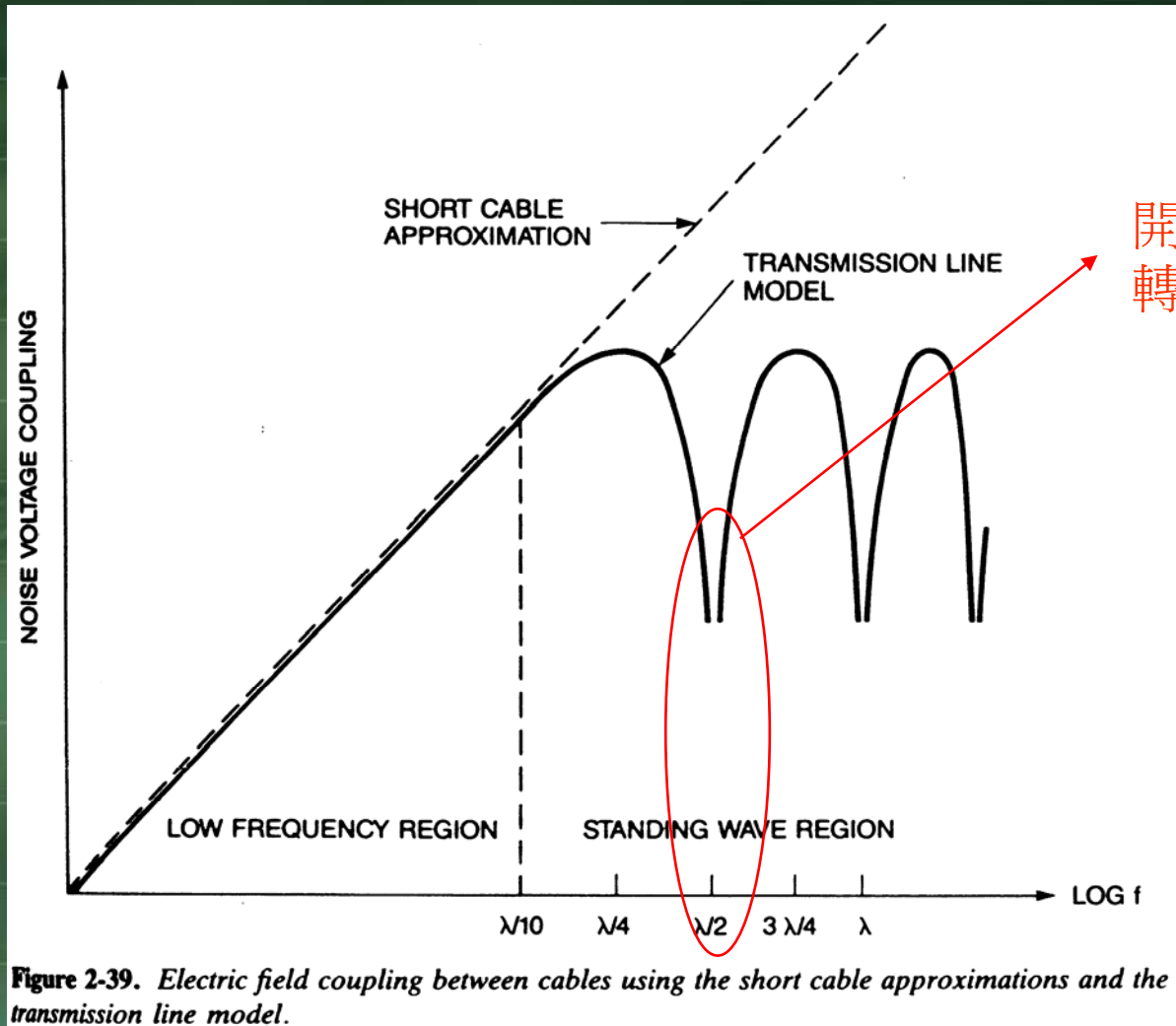



Agenda

- ✦ Circuit Analysis
- ✦ Practical Model of Component and Frequency Response
- ✦ Common mode and Differential mode
- ✦ Near Field and Far Field
- ✦ Antenna Effect
- ✦ *Transmission Line Analysis*
 - ✦ Transmission Line Model
 - ✦ Transfer Impedance
 - ✦ Characteristic Impedance
 - ✦ Reflection





Transmission Line Model

- If $L \leq \frac{1}{6} \cdot t_r$, *lumped model* is used ([4], p8)
- If $L > \frac{1}{6} \cdot t_r$, *distributed model* is used

L : *Electrical line length* ; it is the time that a electron spends on running through a lead (pico-sec)

t_r : Rising time of the signal transmitting on the lead

Furthermore,

$$L = \frac{t_r \cdot V_p}{8}, \quad V_p = \frac{C}{\sqrt{\epsilon_r}}$$

V_p : Propagation velocity

C : 3×10^8 m/s, ϵ_r : dielectric constant = ϵ / ϵ_0






Transmission Line Model

Lumped Model

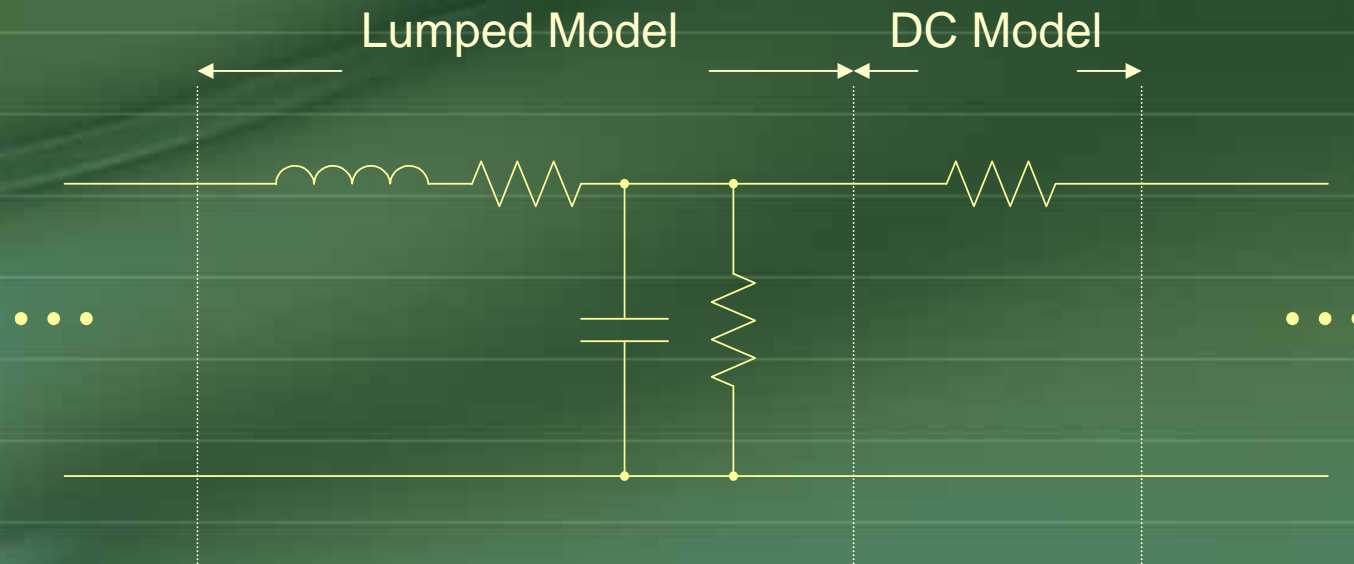- Delay for entire line \ll Signal transition time
- Every point on the transmission line can be seen *with the same voltage potential.*






Transmission Line Model

Distributed Model

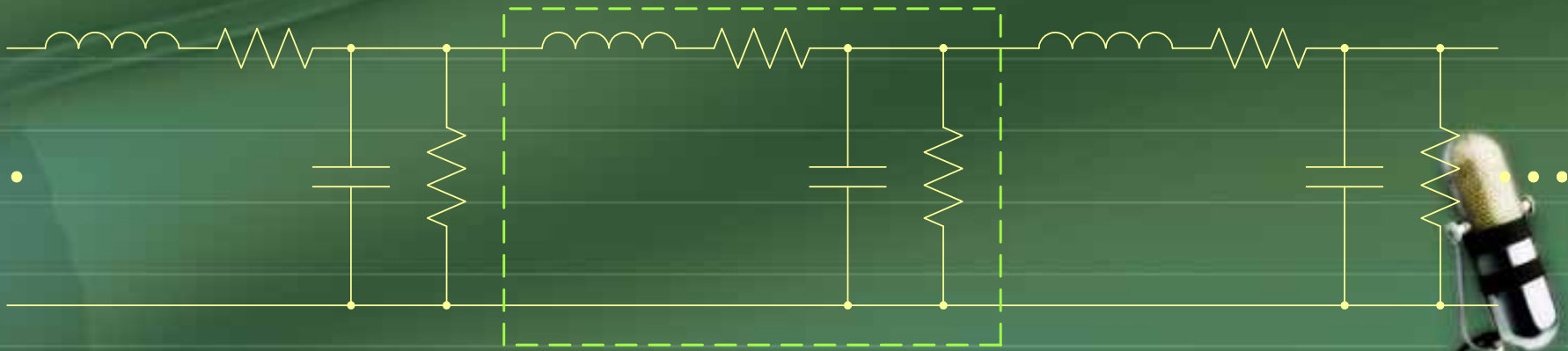- Delay per section \ll Signal transition time
- Every point on the transmission line should be seen as a point *with different voltage potential*.
- Ringling, overshoot, reflection, and crosstalk will be more serious in the condition.*





Transmission Line Model

- *Keeping design within the DC-modeled or lump-modeled region as far as possible is the key point.*
 - Traces (wires) of critical signals, such as clock sources, should be as short as possible
 - Rising time and falling time of the fastest frequency signal in a circuitry should be as slow as possible.
 - The lead running high frequency should have small propagation delay (ϵ_r is small).
 - Circuitry and components should be scale down.




Transmission Line Model


Cross sections of popular transmission line geometries

Transmission line – two conductors ([4], p.140,187)

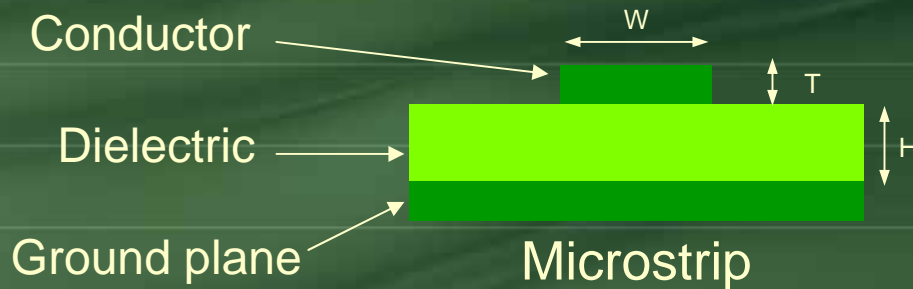
$Z_0 = f(\epsilon_r, W, H, T, \text{topology})$



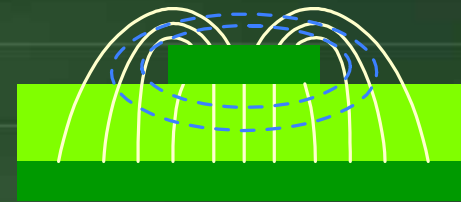
$$Z_0 = \frac{87}{\sqrt{\epsilon_r + 1.414}} \cdot \ln\left(\frac{5.98H}{0.8W + T}\right)$$



Dielectric constant=2.8~4.5
→ fast

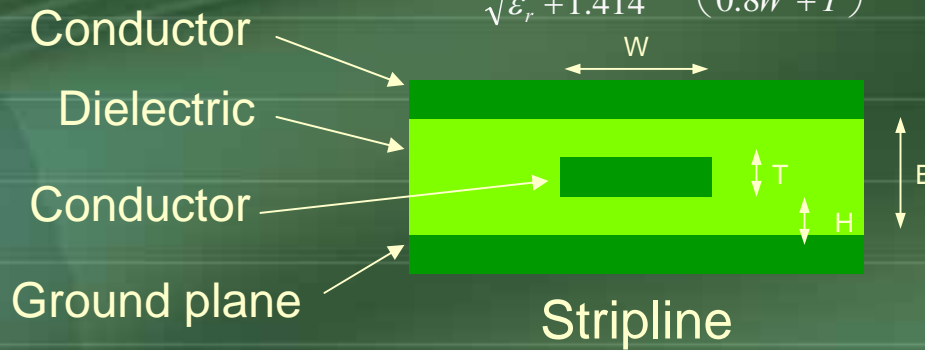
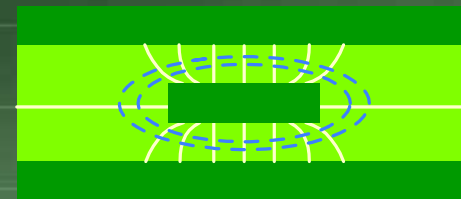
$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \cdot \ln\left[\frac{4H}{0.67\pi W \left(0.8 + \frac{T}{W}\right)}\right]$$




Dielectric constant=4.5
→ slow, but good for noise





Transmission Line Model

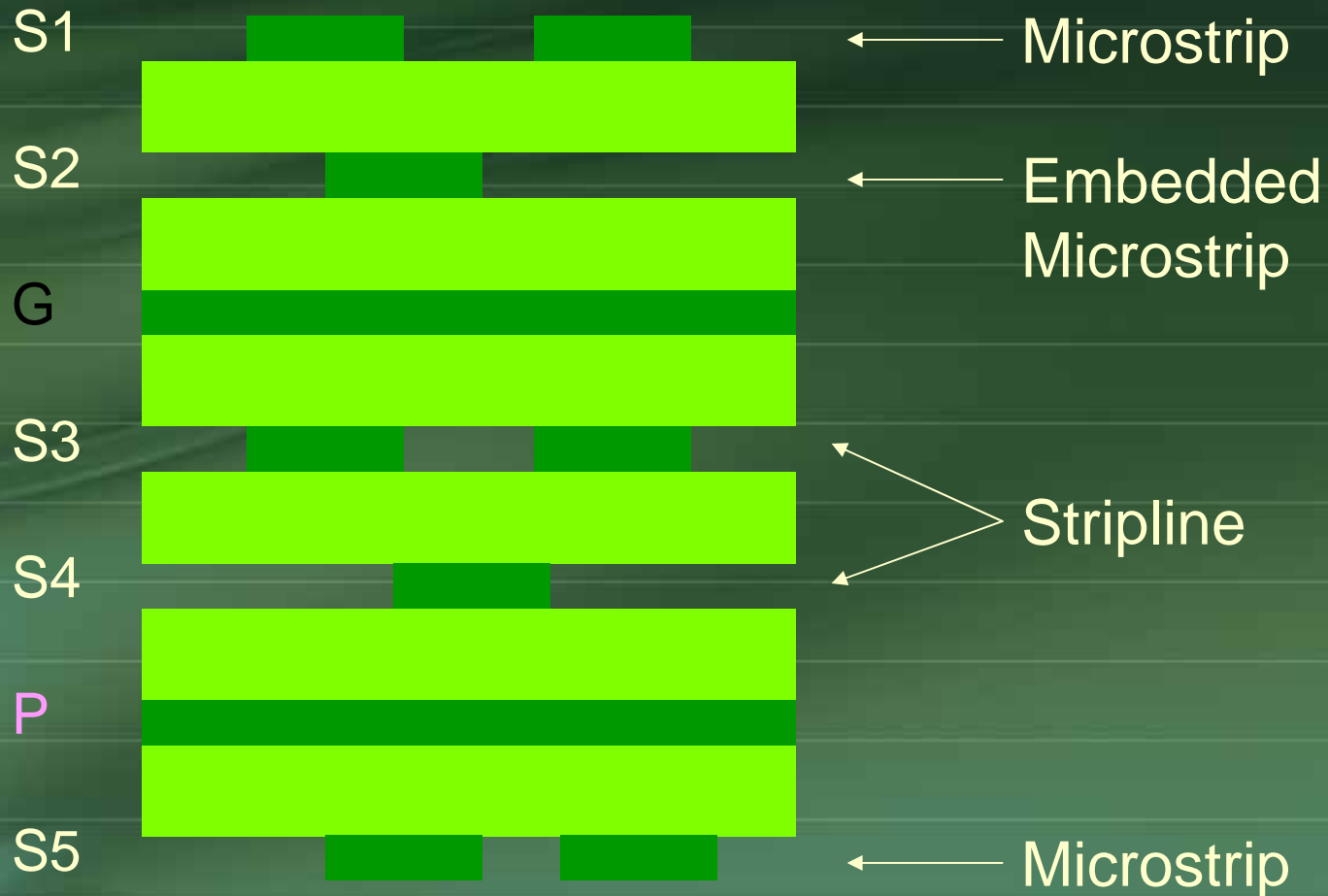



Transmission Line Model

Dielectric material	Propagation delay(ps/in.)	Dielectric constant ϵ_r
Air	85	1.0
Coaxial cable(75%)	113	1.8
Coaxial cable(66%)	129	2.3
FR-4 PCB, outer conductor	140 ~ 180	2.8 ~ 4.5
FR-4 PCB, inner conductor	180	4.5
Al PCB, inner conductor	240 ~270	8 ~ 10






Transfer Impedance

- The transfer impedance of a cable shield :

$$Z_t = \frac{V_s}{I_s} = \frac{1}{I_s} \left(\frac{dV_i}{dl} \right) \quad (\Omega / m)$$

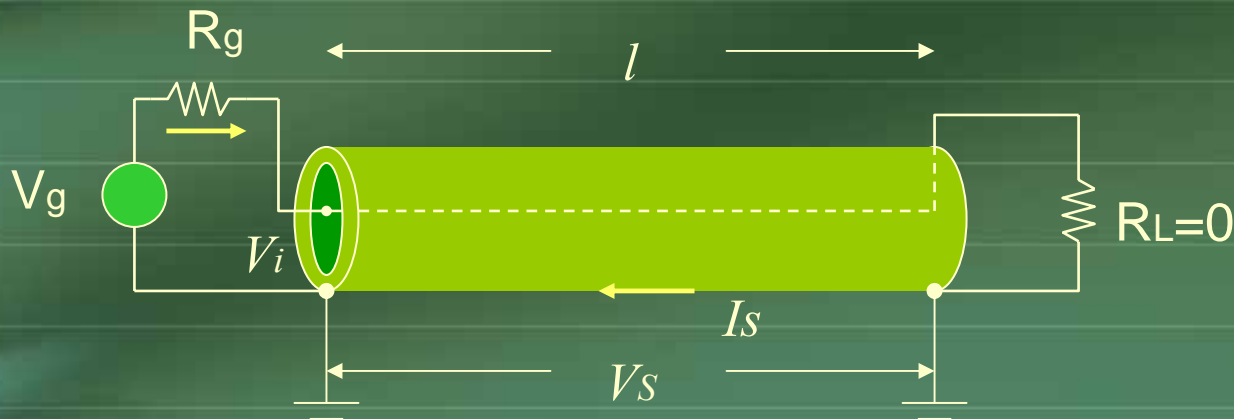
- The shielding effectiveness of a cable can be expressed in terms of the shield transfer impedance. *Lower Z_t results from a better shielding.*






Characteristic Impedance

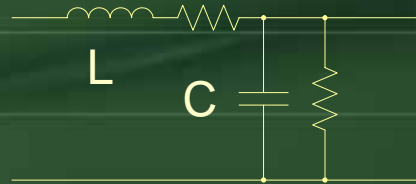- The characteristic impedance of an *ideal* transmission line : $Z_0 = \sqrt{\frac{L}{C}}$
It is a constant.



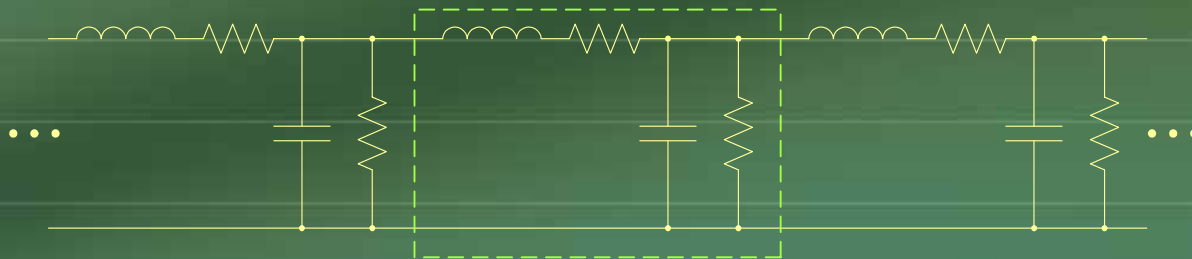- The characteristic impedance of an *practical* transmission line :
it is a function with frequency.
 - Z_0 can be defined as the ratio of voltage to current while a high-frequency current is flowing on the transmission line.






Characteristic Impedance

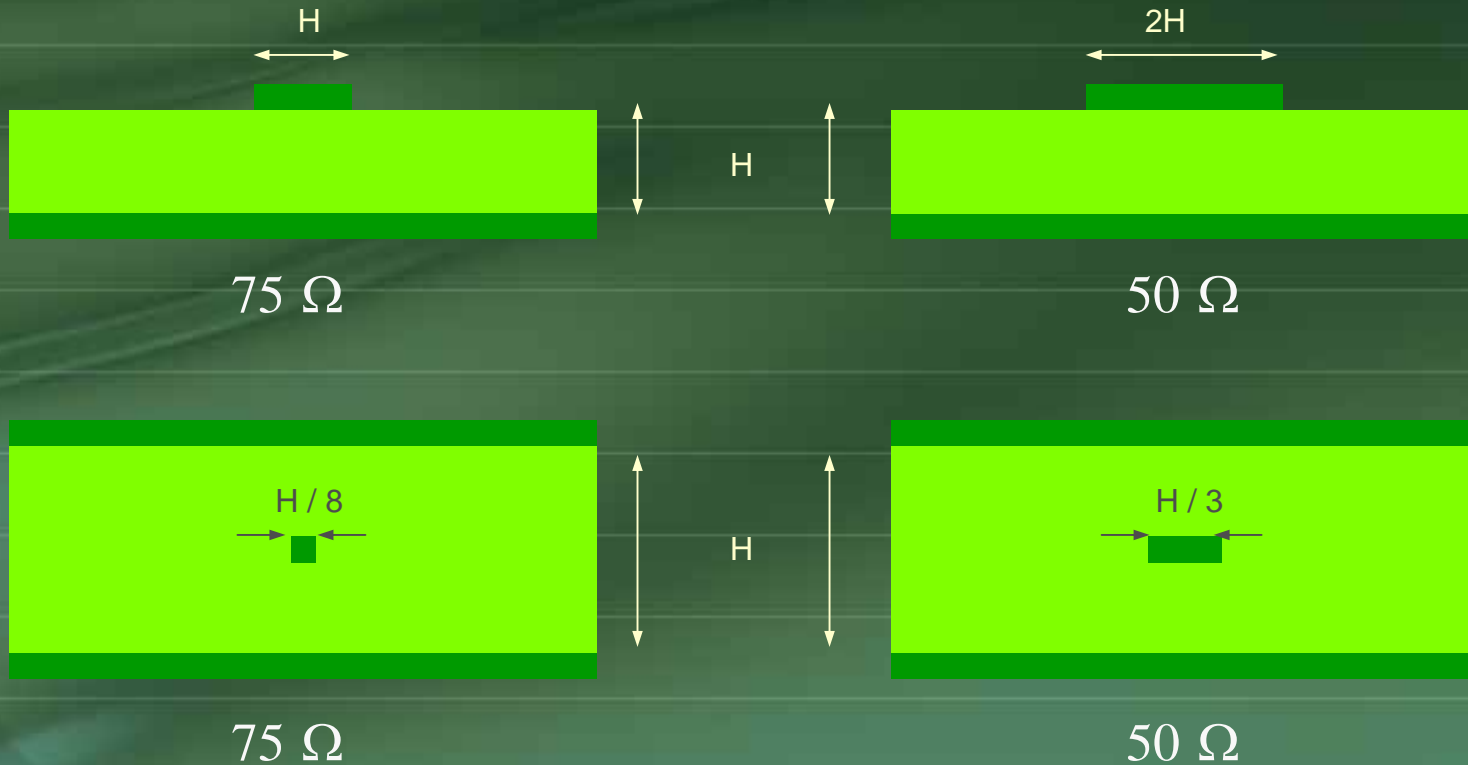Example

- All substrate FR-4 ; $\epsilon_r=4.5$, Z_0 accuracy $\pm 30\%$





Reflection

■ Reflection coefficient :

$$\Gamma_R = \frac{Z_r - Z_0}{Z_r + Z_0}$$

Z_r : characteristic impedance of termination

Z_0 : characteristic impedance of transmission line

■ Reflected signal = input signal $\times \Gamma_R$







Reflection

Example

$$Z_0 > (Z_0' = \frac{1}{2} \cdot Z_0)$$

$$0 > (\Gamma_R = -\frac{1}{3}) > -1$$

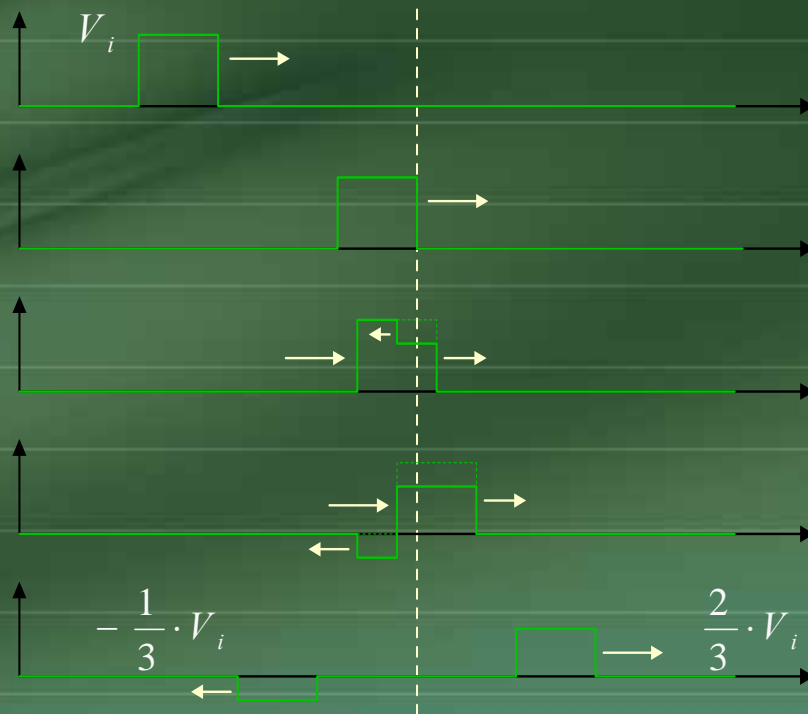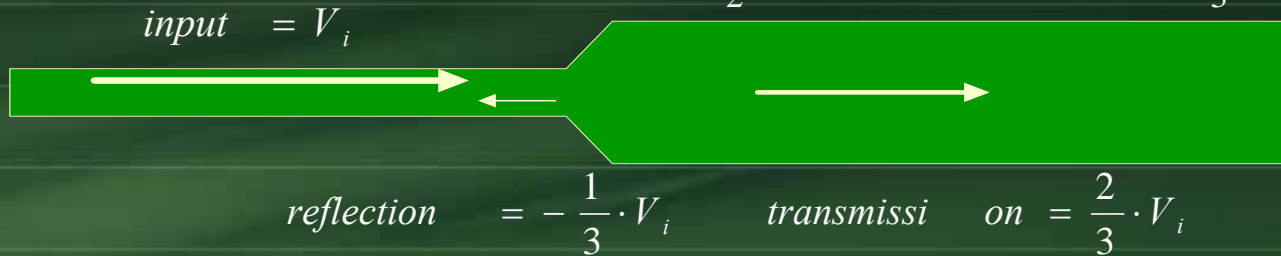




Reflection

Example

$$\text{input} = V_i$$


$$Z_0 < (Z_0' = 2 \cdot Z_0)$$

$$1 > (\Gamma_R = \frac{1}{3}) > 0$$

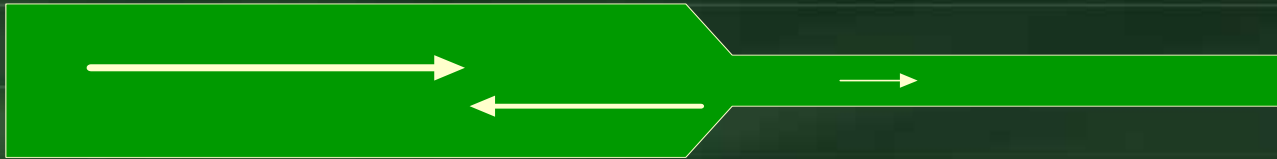



$$\text{reflection} = \frac{2}{3} \cdot V_i$$
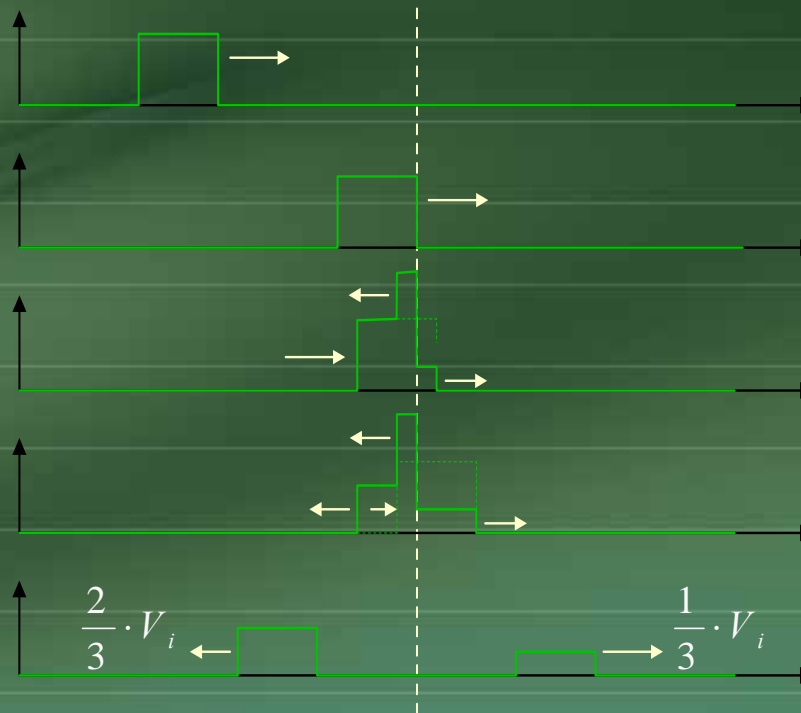
$$\text{transmission} = \frac{1}{3} \cdot V_i$$








Reflection Example

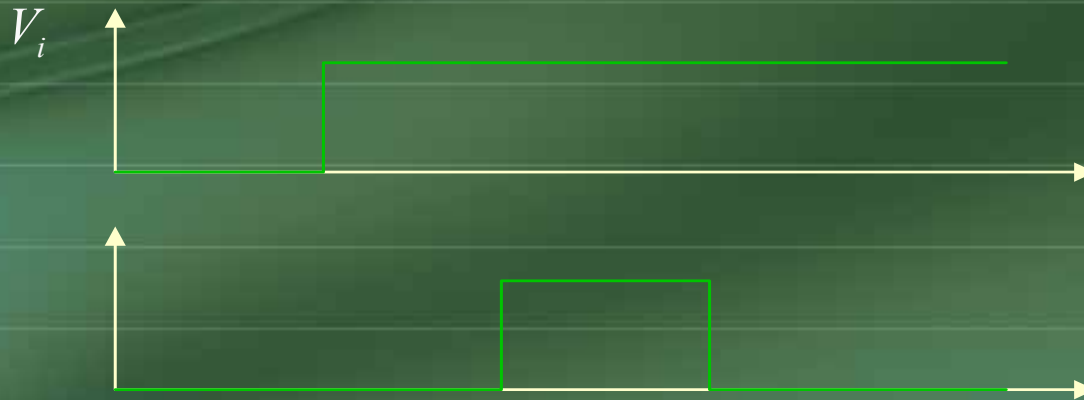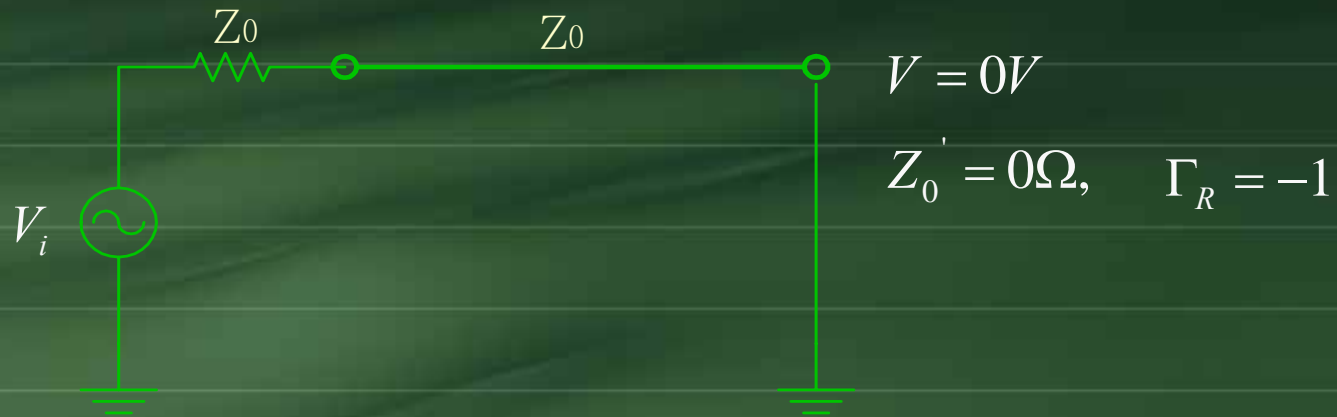




Reflection Example

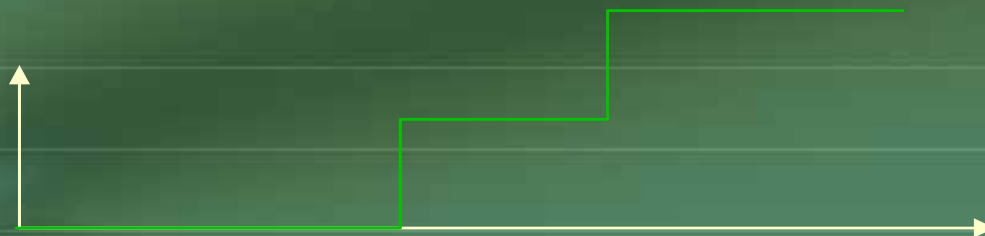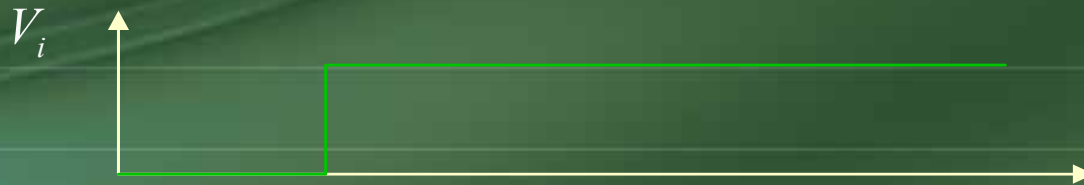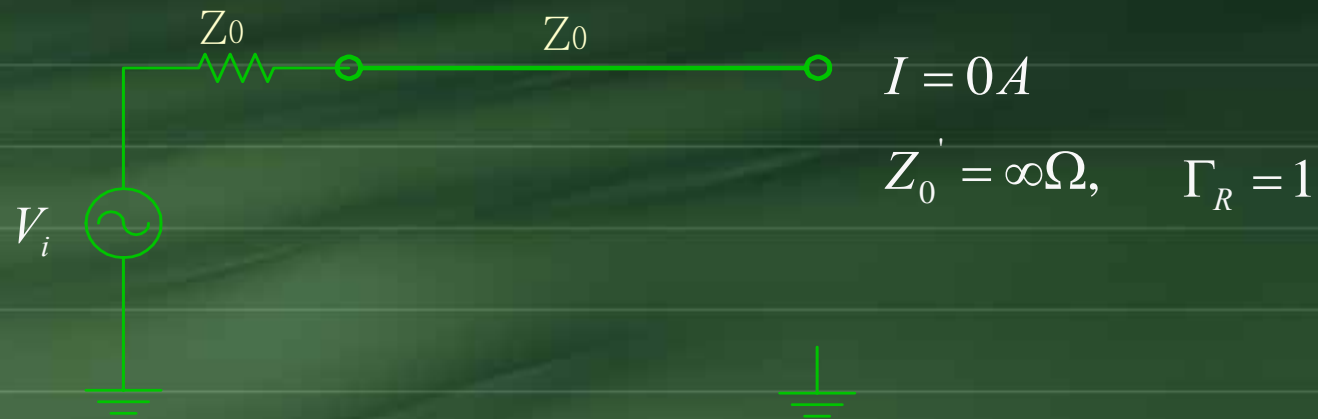



Reflection

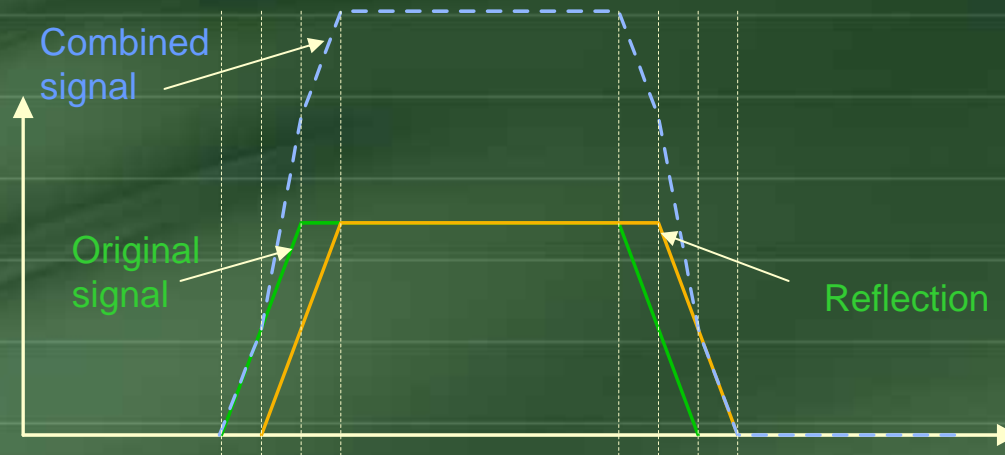- Low-speed circuit : $2 \cdot T_{pd} < t_r, t_f$
 - Reflections are masked by rising/falling edges -- insignificant



- High-speed circuit : $2 \cdot T_{pd} > t_r, t_f$
 - Reflections cause ringing – overshoot / undershoot

