



Electromagnetic Compatibility (*EMC*)

Introduction about Filters





Agenda

❑ Characteristics of Filters

❑ Impedance Mismatch Effects ([2] 10-2-1)

❑ Low-Pass Filters

❑ High-Pass Filters

❑ Power Line Filter Design

❑ Common-Mode Filter

❑ Differential-Mode Filter

❑ Combined CM and DM Filter

❑ Inductor Design


❑ Filter Installation





Characteristic of Filters

- Filters are designed to attenuate at certain frequencies, while permitting energy at other frequencies to pass.
- Filters performance characteristics
 - Insertion loss : $IL(dB) = 20 \cdot \log_{10} \frac{V_1}{V_L}$
 - V_1 , the output voltage of signal source without filter
 - V_L , the output voltage of signal source at the output terminals of the filter with filter
 - Input and output impedances
 - Attenuation in the pass-band
 - Skirt fall-off
 - Steady-state and transient voltage ratings

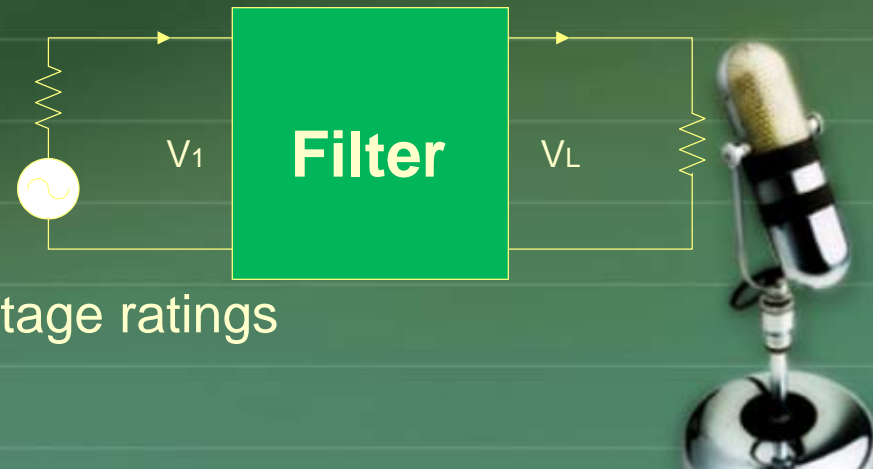



Characteristic of Filters

Impedance Mismatch Effects

- ✦ Filters are usually designed to operate between specified input and output impedances.
 - ✦ When source and load impedances are different from the specified impedances of the designed filter, the output response changes.
- ✦ *Impedance mismatch can result in an increase of interference level at the filter output, rather than the desired decrease.*





Characteristic of Filters

Impedance Mismatch Effects

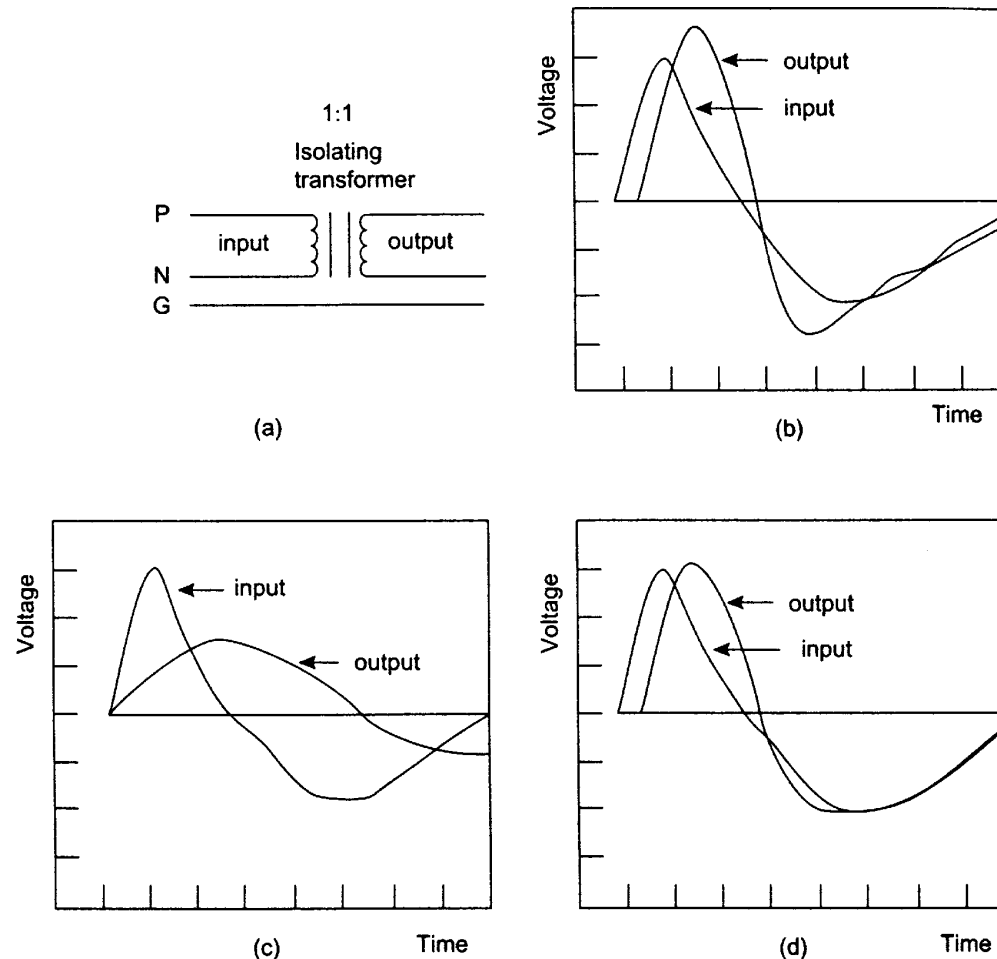


Figure 7-3 Propagation of a 6-kV peak 0.5- μ s rise-time transient voltage in (a) 1:1 isolating transformer with the (b) output terminals open, (c) output terminals terminated in 150- Ω 100-W load, and (d) output terminals terminated in 1500- Ω 10-W load






Characteristic of Filters


Low-Pass Filters

Capacitor Filter

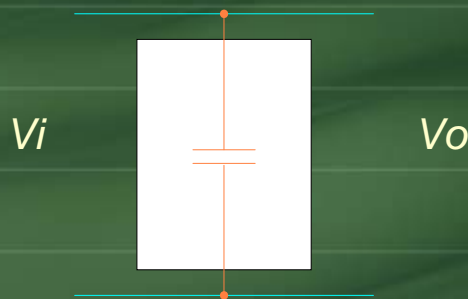


Transfer Function


$$\left| \frac{T(\omega)}{k} \right| = \frac{1}{1 + j \frac{\omega}{\omega_0}} \quad (dB)$$

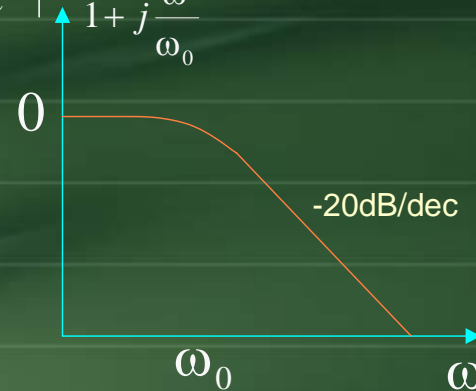



Insertion Loss

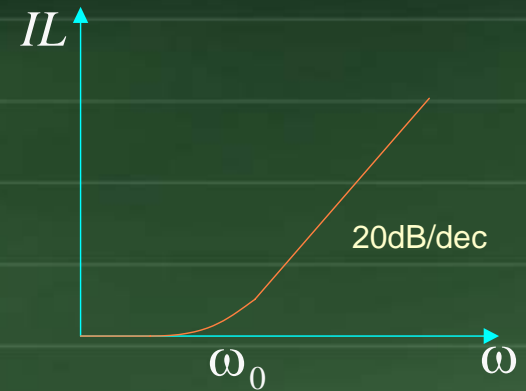

Inductor Filter

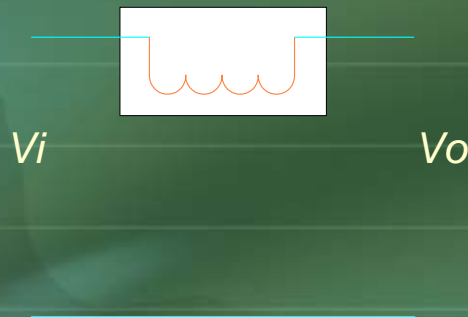

$$\left| \frac{T(\omega)}{k} \right| = \frac{1}{1 + j \frac{\omega}{\omega_0}} \quad (dB)$$

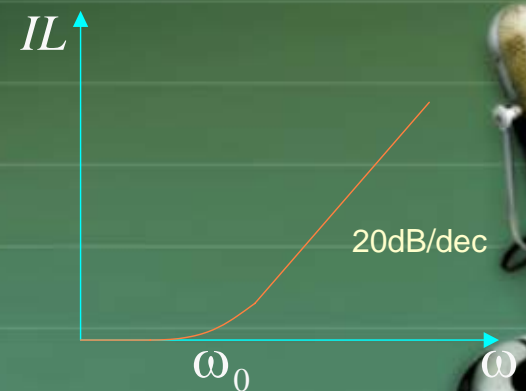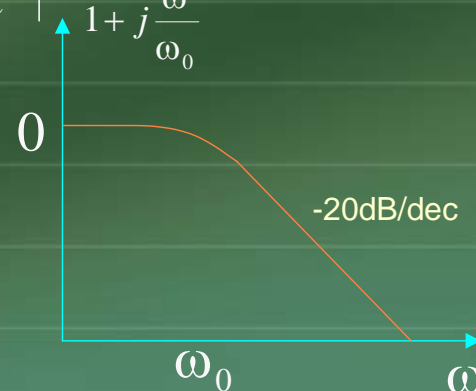





Characteristic of Filters

Low-Pass Filters

■ L-Section (LC) Filter

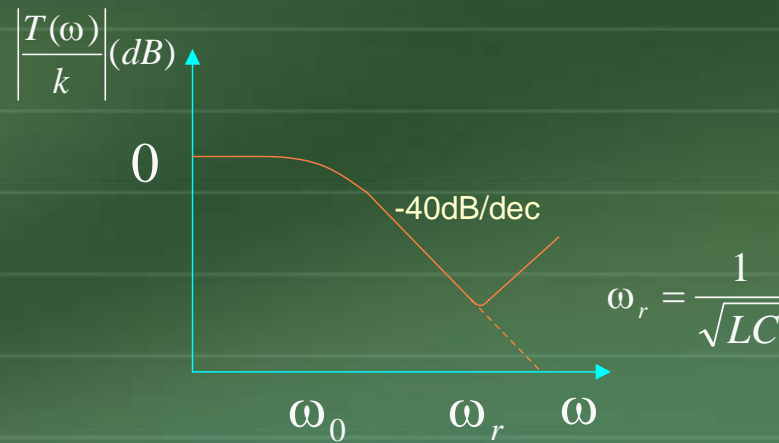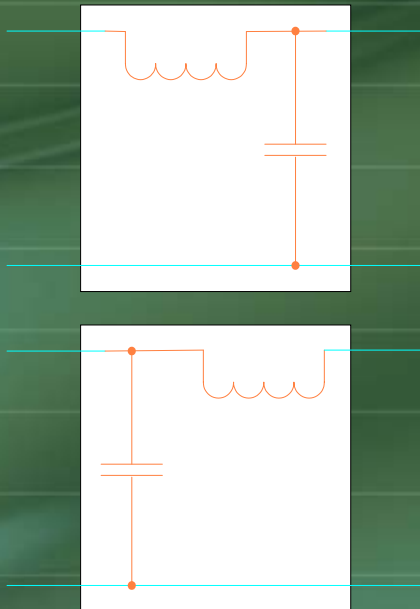- More filtering than a single C or L filter at high frequency
- Poor high frequency attenuation because of stray interturn capacitances. It may resonate when input signal is a transient.







Characteristic of Filters

Low-Pass Filters

π-Section Filter

- The most common used in practice

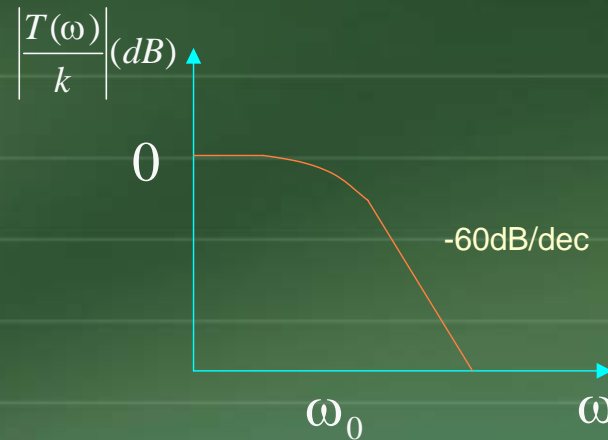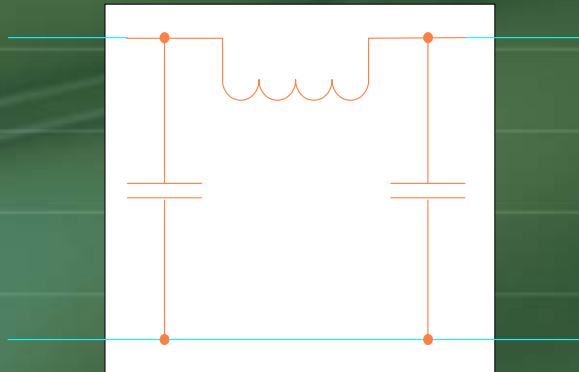





Characteristic of Filters

Low-Pass Filters

■ T-Section Filter

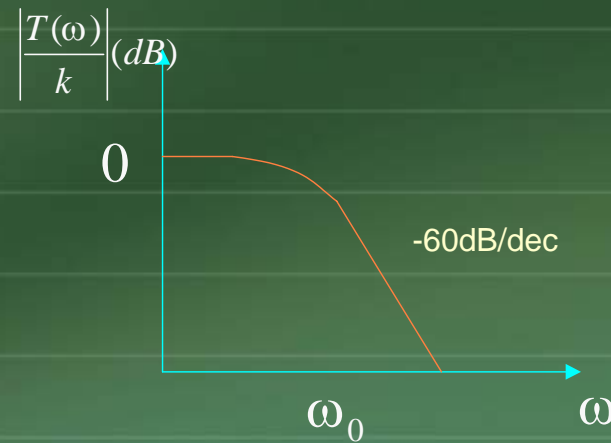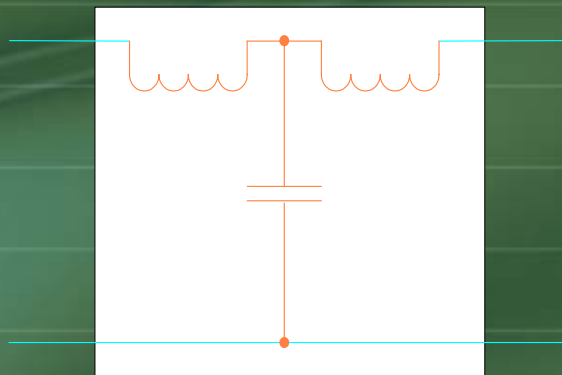- Requiring two inductors increases the size of the filter, but it is more effective in reducing transient interferences than π -section filter.






Characteristic of Filters

Low-Pass Filters

Active Filter

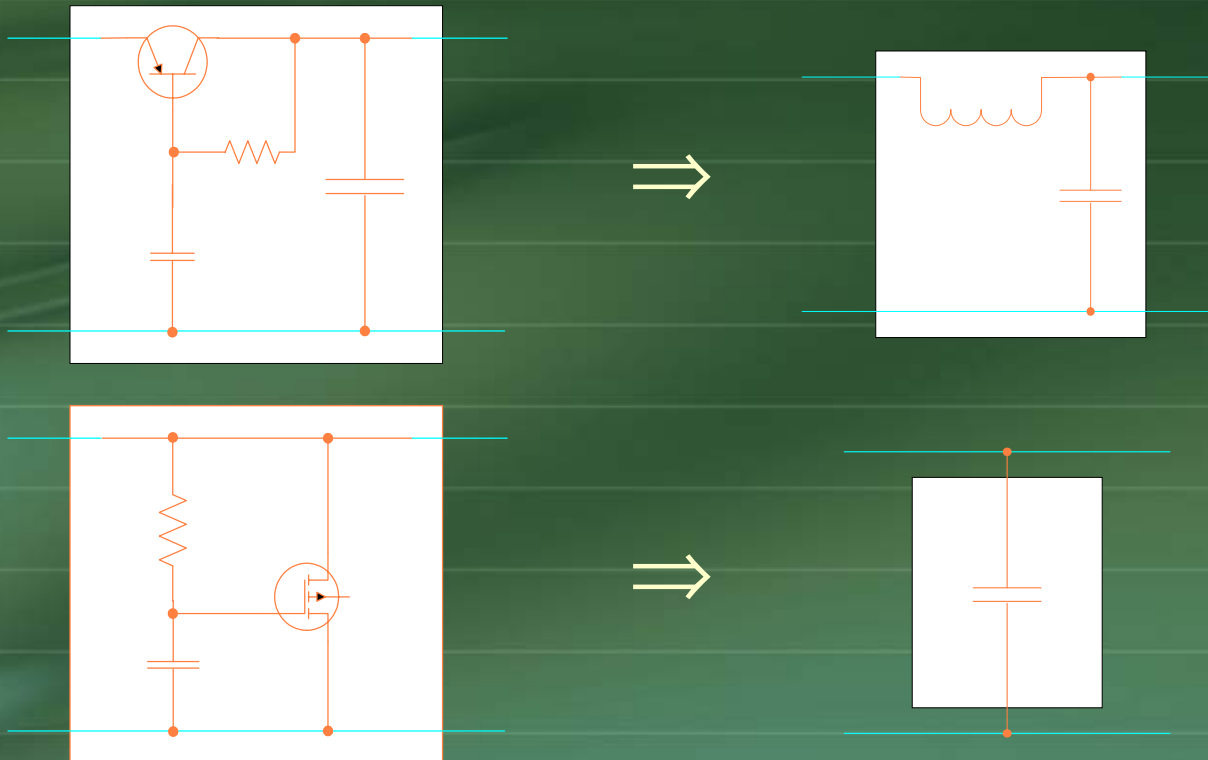
- It offers reasonable size when very low frequencies have to be filtered out.





參考資料：出自交大柯明道教授的網頁

VDD-to-VSS ESD Clamp Circuit

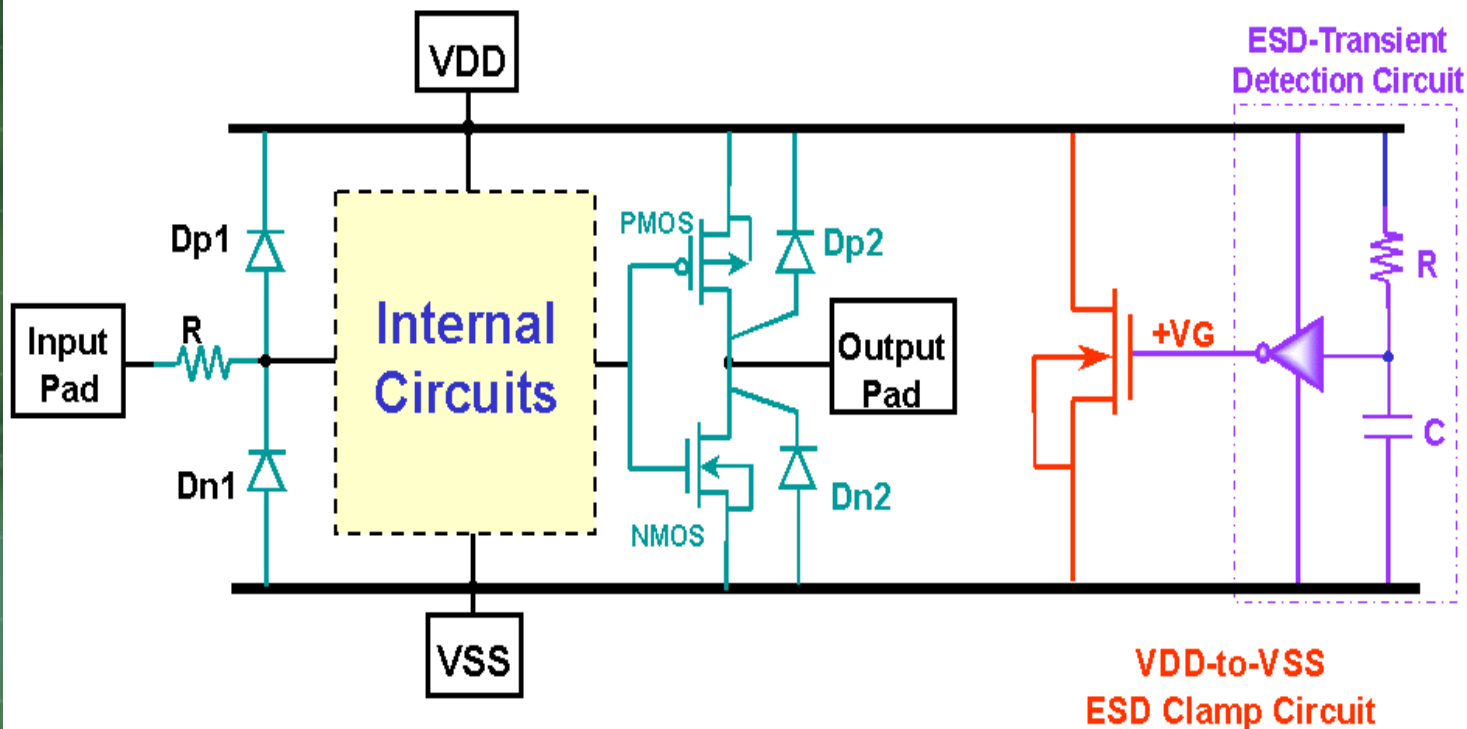

- The ESD voltage across the VDD and VSS power lines can be quickly discharged through the short-circuit path of the turned-on NMOS.





Characteristic of Filters

Low-Pass Filters

- Guidelines to decide the type of filter [2] 10-2
 - Low impedance in both directions
 - L filter or T-Section filter
 - High impedance in both directions
 - C filter or π -Section filter
 - Mismatched impedance in both directions
 - L-Section (LC) filter





Characteristic of Filters


High-Pass Filters

- A standard low-pass filter transforms into a high-pass filter when each inductor is replaced with a capacitor.

$$C_{hp} = \frac{1}{L_{lp}}$$

$$L_{hp} = \frac{1}{C_{lp}}$$


$$\left| \frac{T(\omega)}{k} \right| = \frac{1}{k} \cdot \left| \frac{V_o}{V_i} \right| = \left| \frac{1}{1 - j \frac{\omega_0}{\omega}} \right| (dB)$$

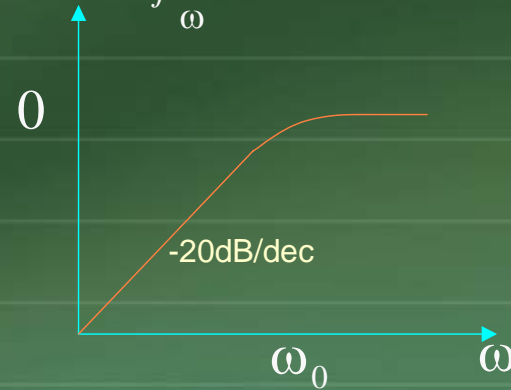



Agenda

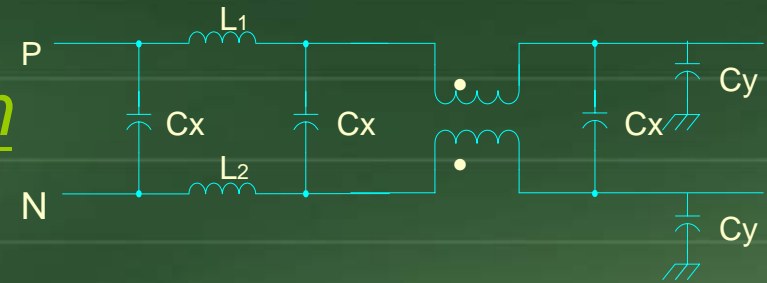
- Characteristics of Filters
 - Impedance Mismatch Effects
 - Low-Pass Filters
 - High-Pass Filters
- *Power Line Filter Design*
 - Common-Mode Filter
 - Differential-Mode Filter
 - Combined CM and DM Filter
 - Inductor Design
- Filter Installation





Power Line Filter Design

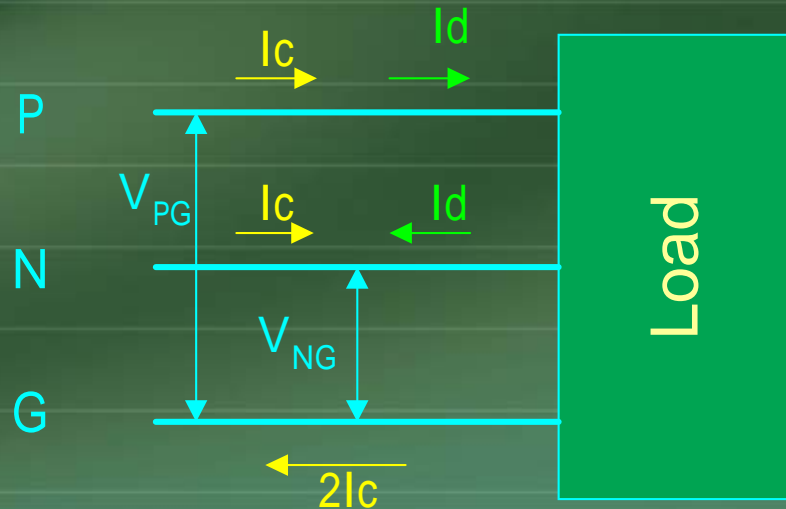- Basic differences between a power line filter and a communication circuit filter
 - The input impedance of a power line filter is almost never impedance match because of load changing.
 - Power line filters are strongly biased by the power line current.
- Common-Mode(CM) and Differential-Mode(DM)







Power Line Filter Design

Common-Mode Filter

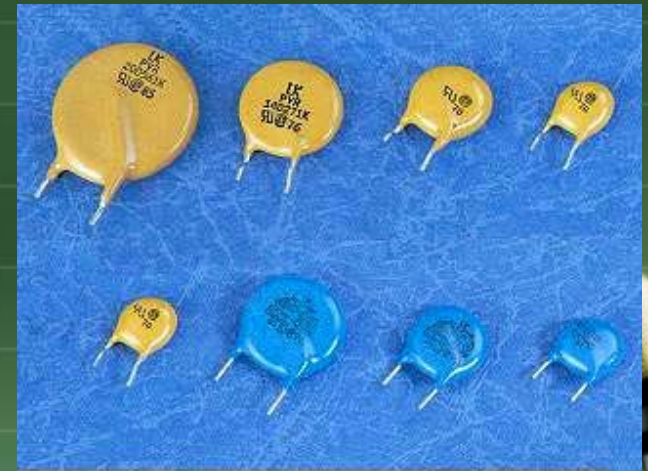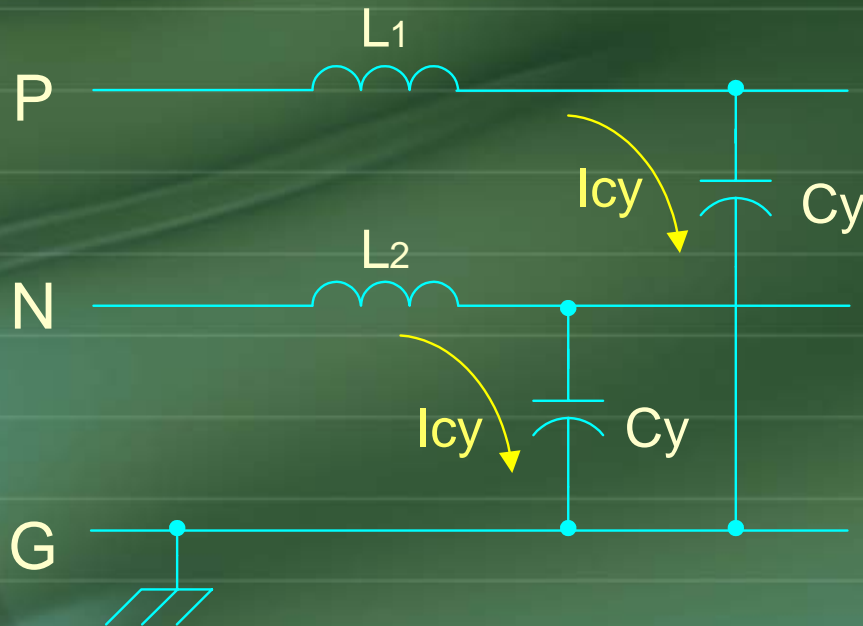- Phase-to-ground CM filter
 - Limit C_y maximum value, so the high leakage current I_{cy} depends on the line voltage







Power Line Filter Design

Common-Mode Filter

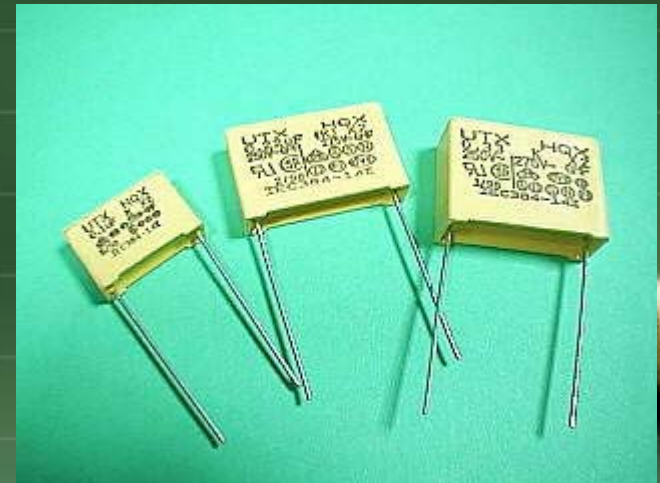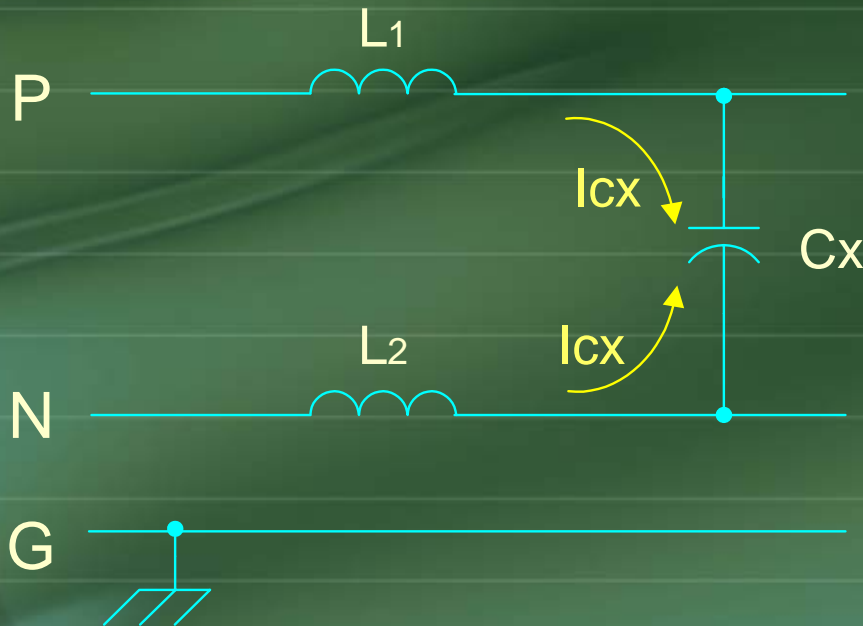
- Phase-to-phase CM filter
 - C_x must be less than $0.5\mu\text{f}$ to avoid shock hazard I_{cX} .





Power Line Filter Design


Common-Mode Filter

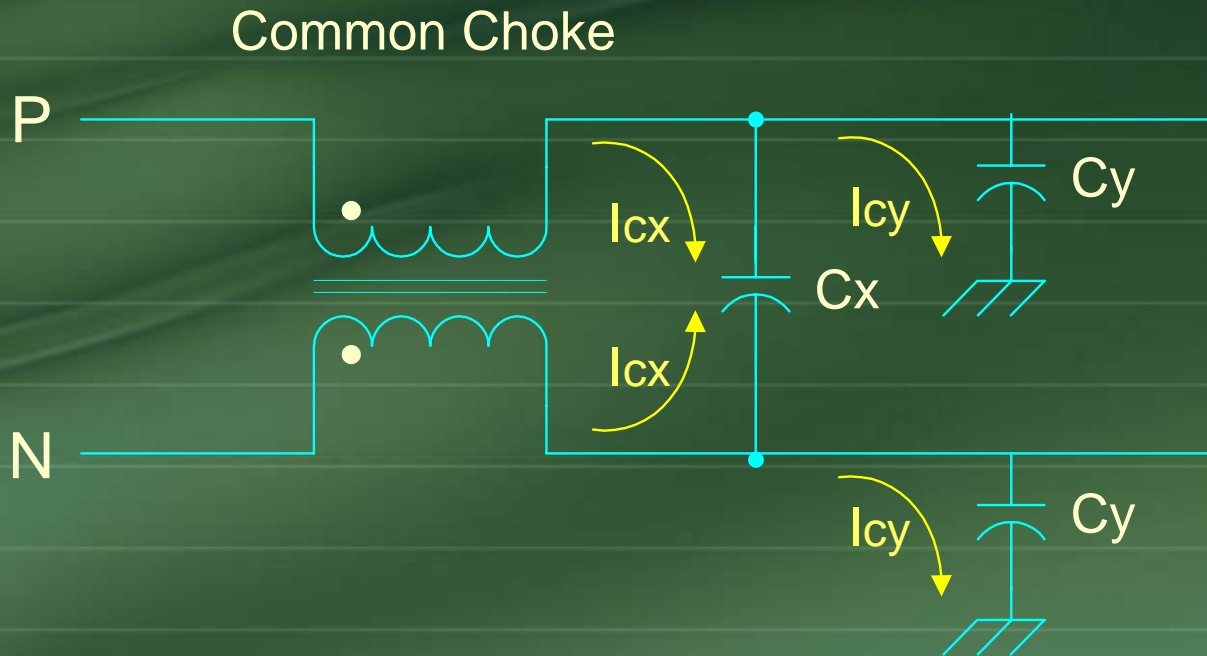



Power Line Filter Design


Differential-Mode Filter

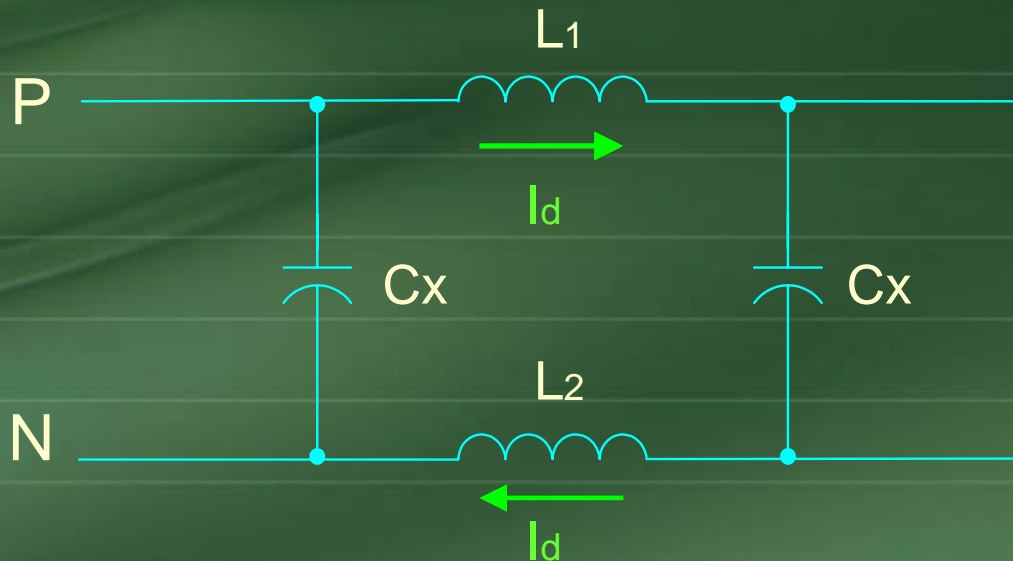



Power Line Filter Design

Combined CM and DM Filter

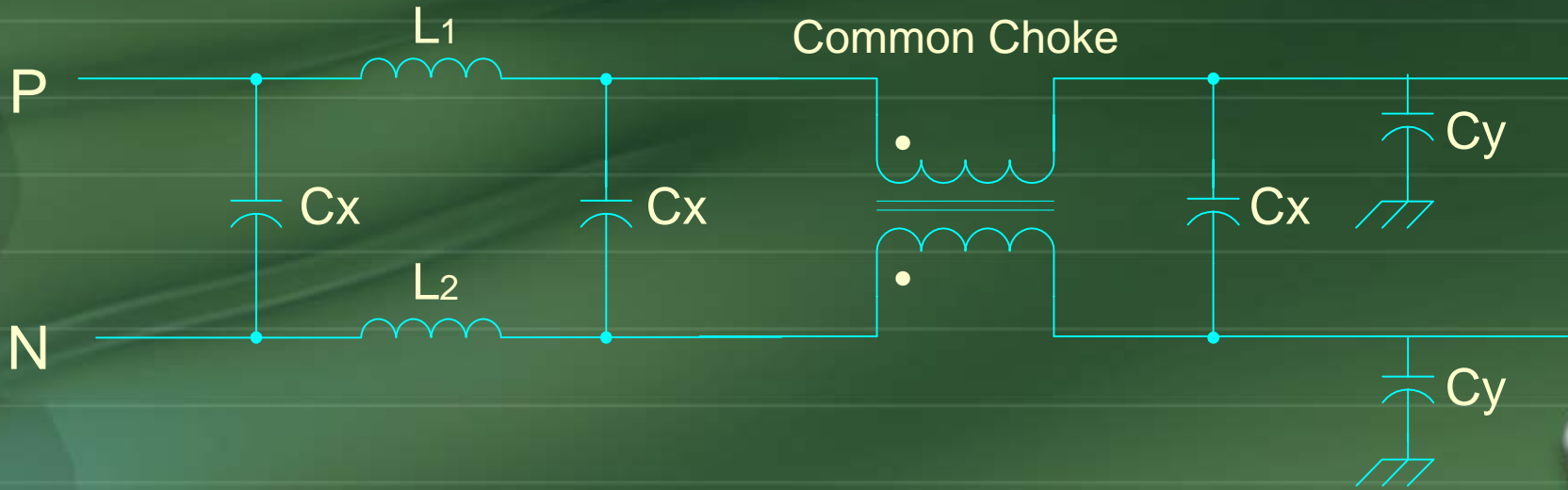




Power Line Filter Design

Inductor Design (Common Choke)

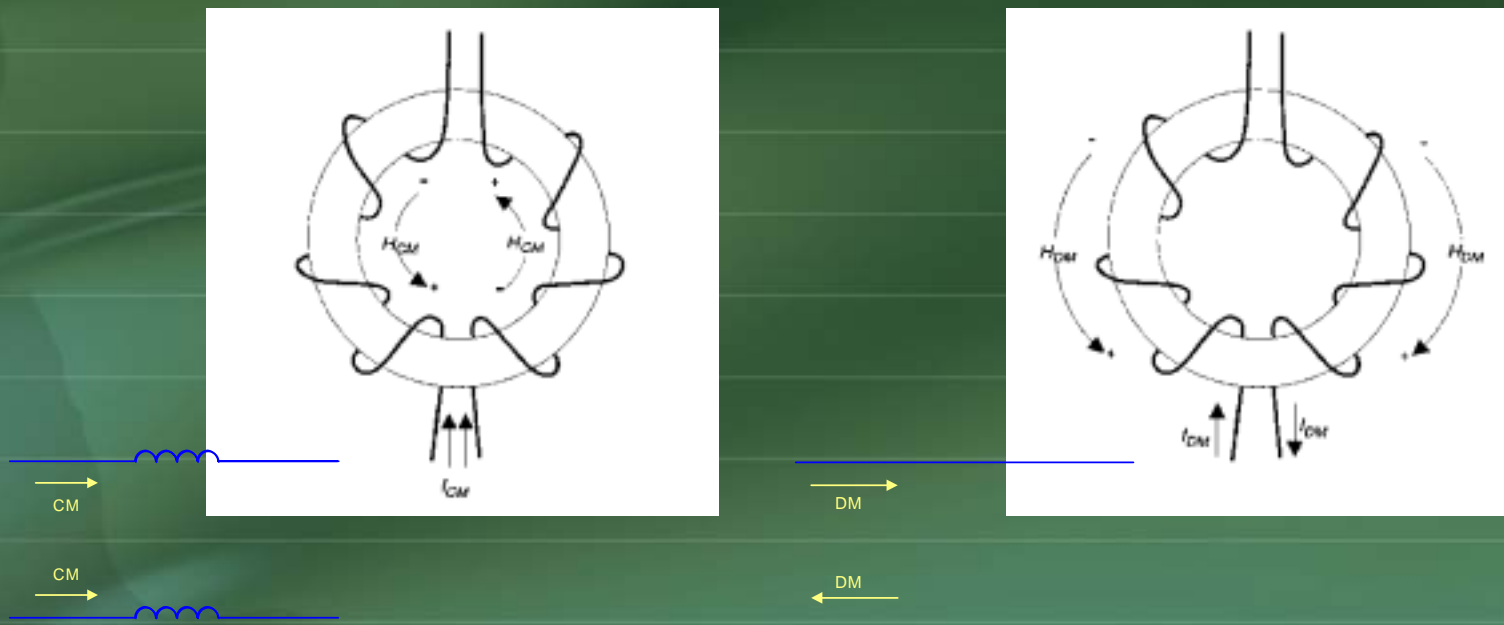- CM choke is the only technique that does not require a ground to function, and by the nature of its operation does not affect the differential-mode current.
- The winding should be done with minimum inter-winding capacitance, or with minimum potential difference between adjacent windings.






Agenda

- Characteristics of Filters
 - Impedance Mismatch Effects
 - Low-Pass Filters
 - High-Pass Filters
- Power Line Filter Design
 - Common-Mode Filter
 - Differential-Mode Filter
 - Combined CM and DM Filter
 - Inductor Design
- *Filter Installation*






Filter Installation

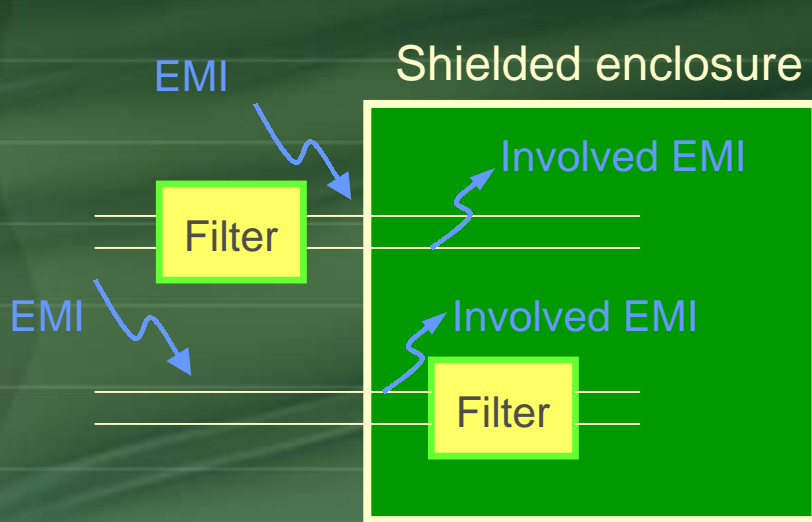

Poor filter installation

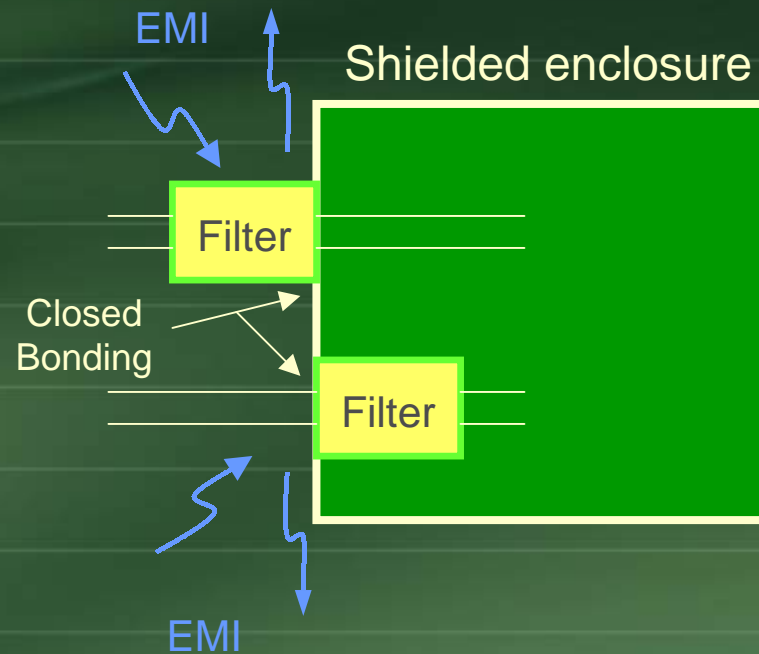



Appropriate filter installation






Filter Installation

Feed-through capacitor

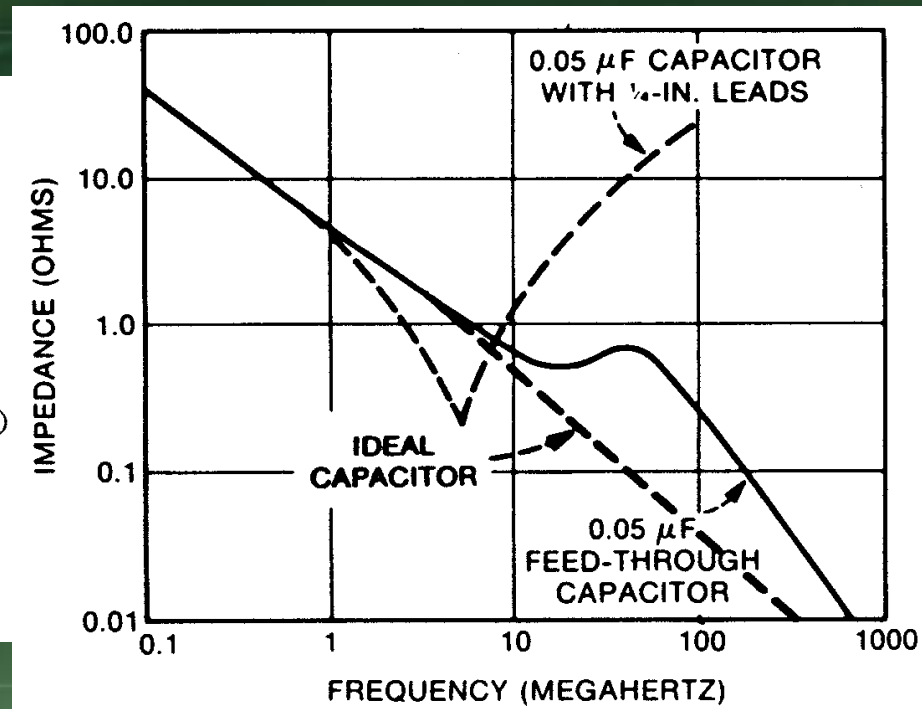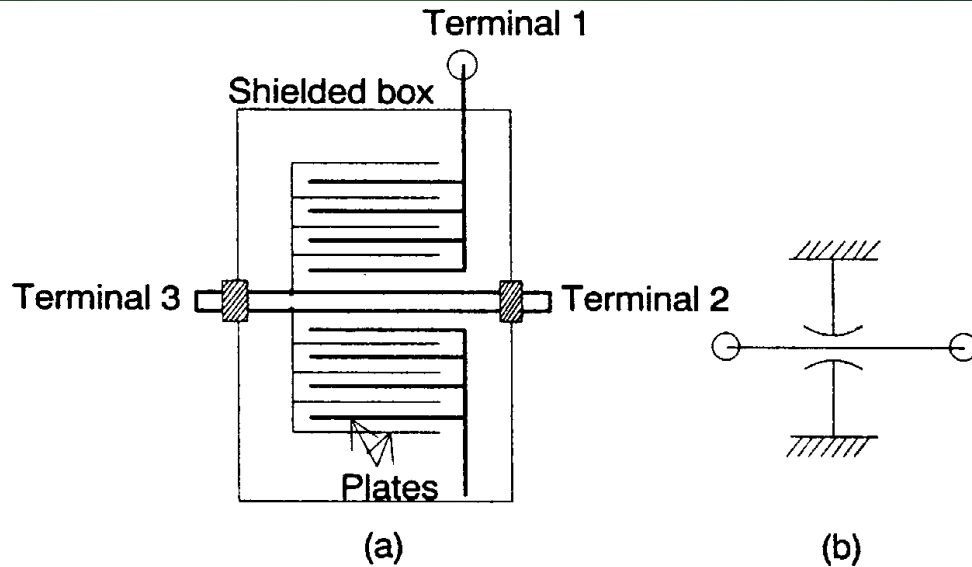




Filter Installation

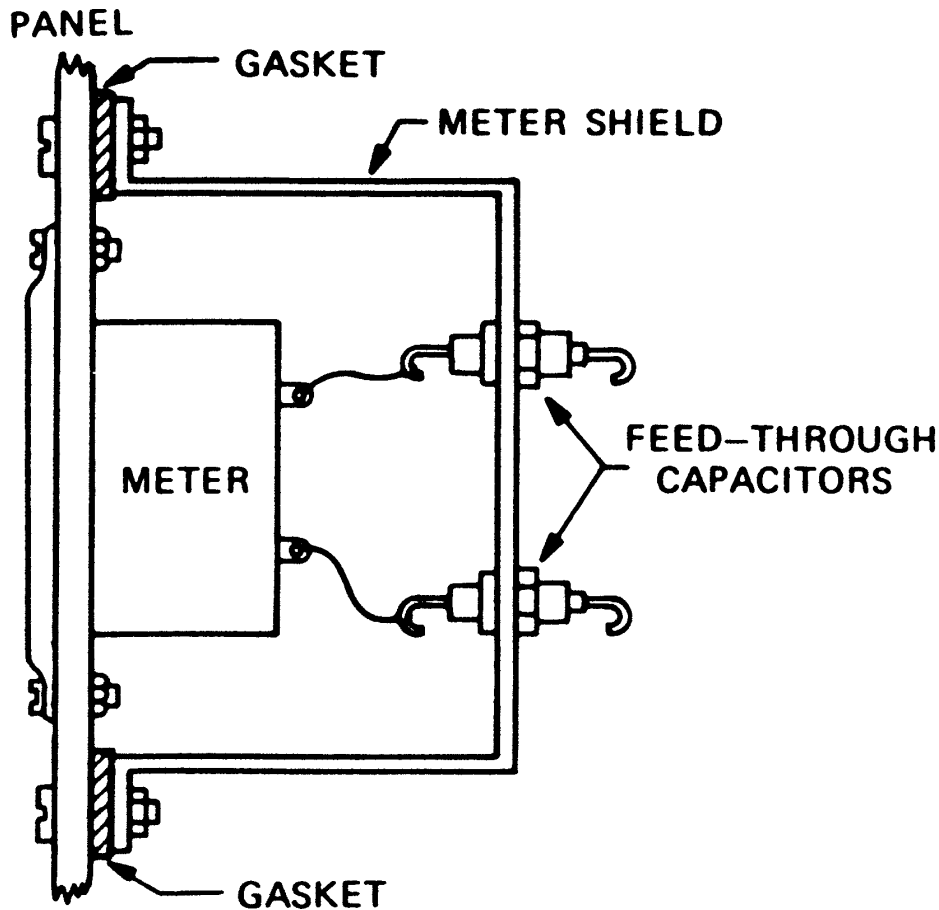

Shielded enclosure wall

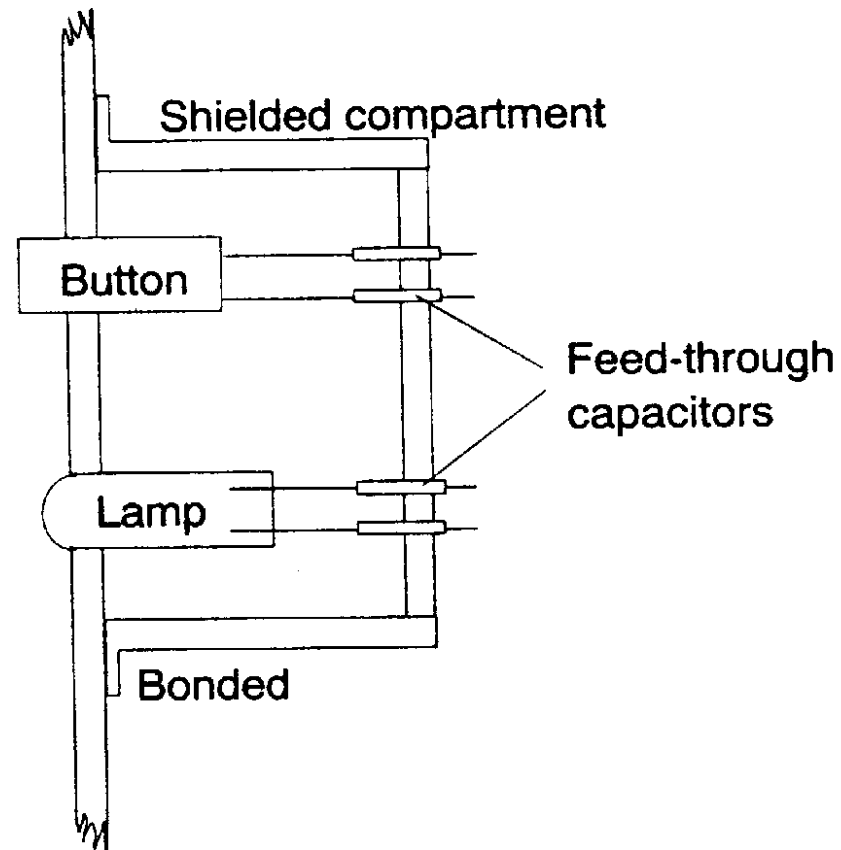



Summary

- ❑ What is the effect for impedance mismatch at the filter output ?
- ❑ What are LP / HP filters and their characteristics ?
- ❑ How to eliminate CM and DM noise ?
- ❑ How to design the power line filter ?

