

Power Integrity Concepts for High-Speed Design on Multi- Layer PCBs

Chulsoon Hwang

Missouri EMC Laboratory

hwangc@mst.edu




PI Module – Physics

- The PDN problem and some preliminaries
 - What PI design impacts
 - Design choices
 - A quick reminder of
 - circuit element behavior with frequency
 - current physics


● Charge delivery physics for PI design

- W
- PL
- fill
- De

 

PDN Problem



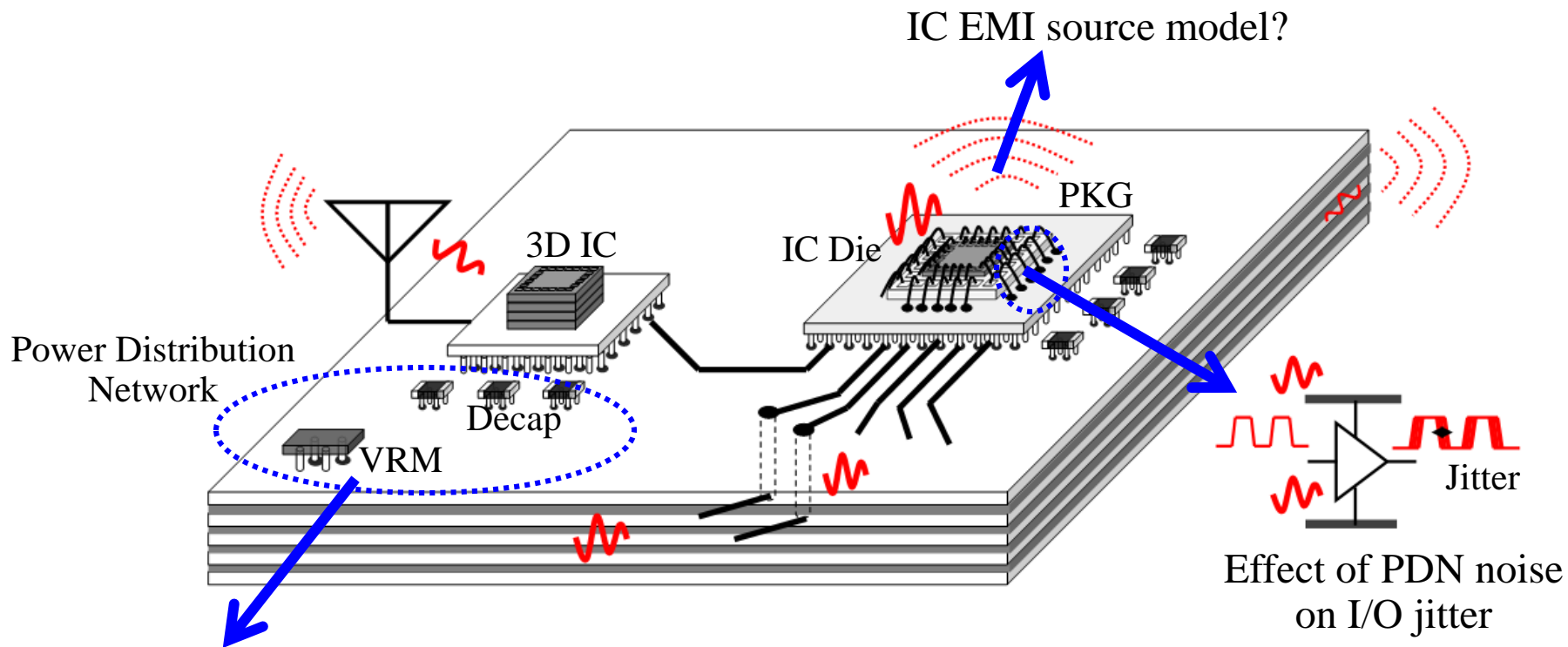
High-speed, integrated, and mixed electronic system



Power Distribution Network

- VRM
- Decoupling capacitors
- Power net area fills

Geometry and Inductance Decomposition

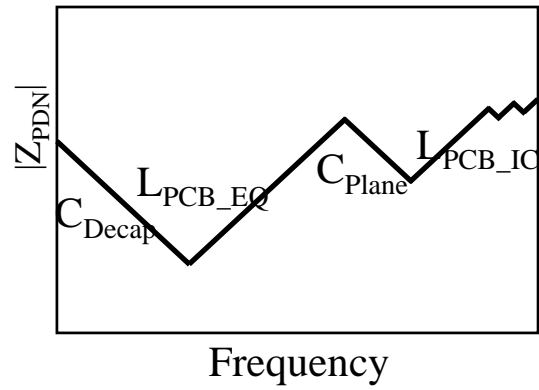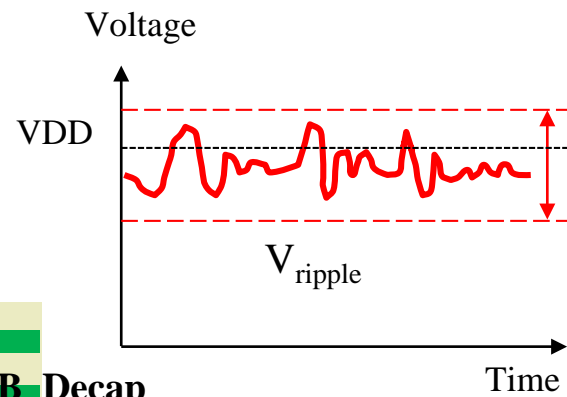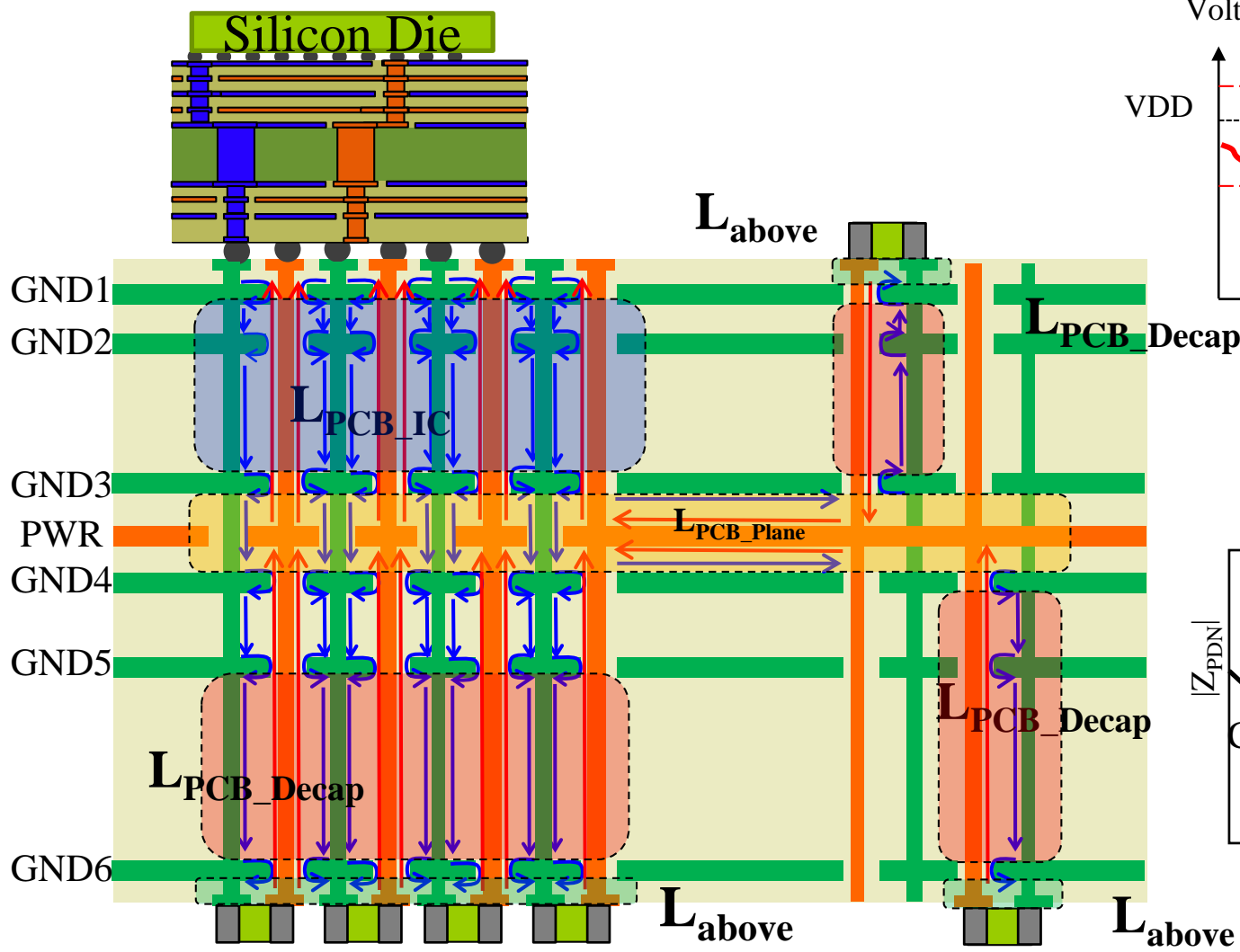

PCB PDN Design Considerations

2a. Decoupling capacitors

- top
- bottom,
- beneath IC?

2b. Decoupling capacitor connection -

- PWR/GND via geometry
- Package size

1. Power plane(s)

- location in stack
- spacing to power return plane
- total area fill
- special materials

Effect of other ground/reference planes?


2a. Decoupling capacitors

- value(s)
- Number (total C)


2c. Decoupling capacitor layout

- How close to IC?
- Shape – ring IC, on one side?

Decaps

 


IC pins






 


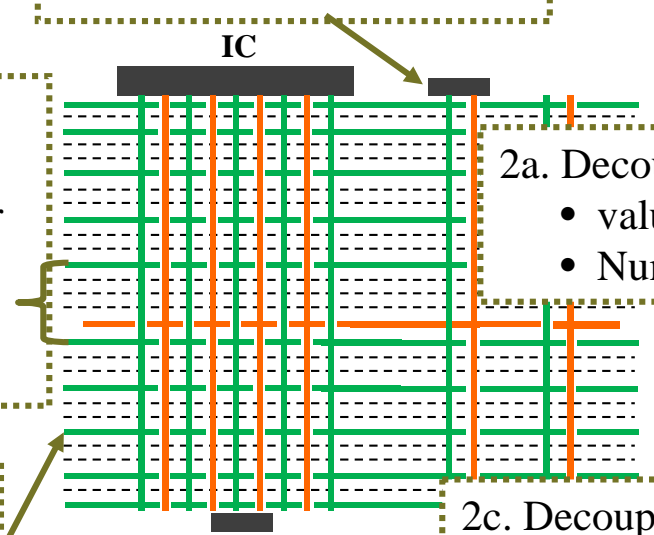3. IC PWR/GND

- Number pins
- pin pattern
- Pitch
- on-package decaps



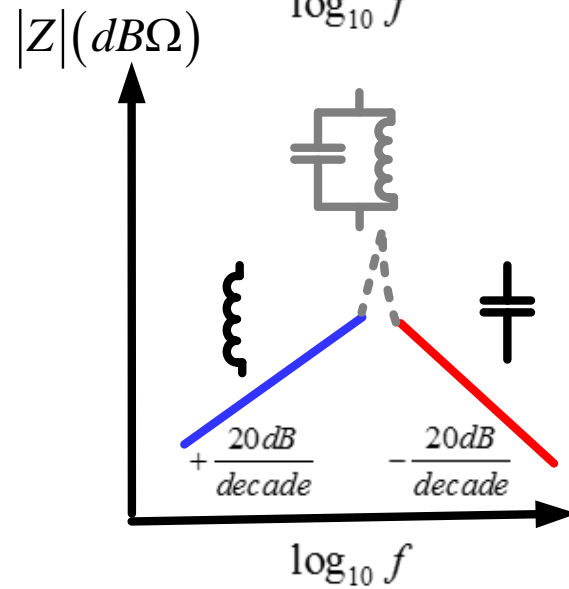  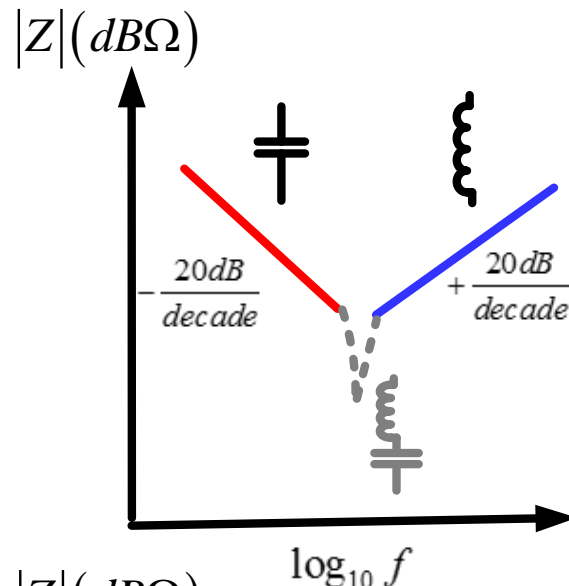 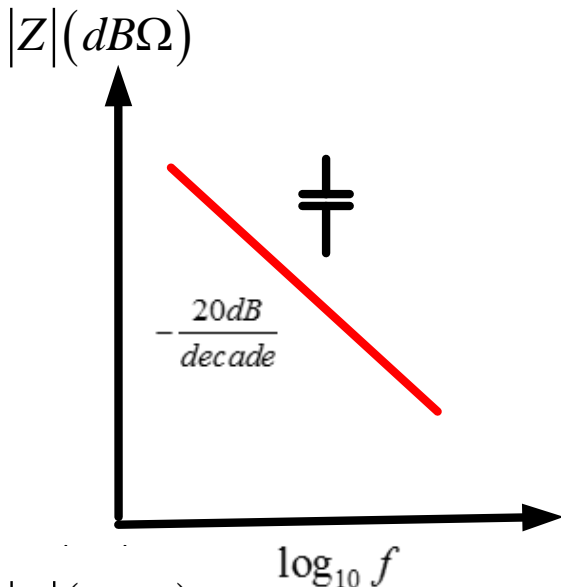

Reminder – Circuit Model Behavior with Frequency



Reminder: Current Behavior


— Conduction current – carried by electrons $\vec{J}_{cond} \equiv \sigma \vec{E}$
- - - Displacement current – carried by $\vec{J}_{displ} = \epsilon \frac{d\vec{E}}{dt}$

—→ impeded by 
 —→ admitted by

Signal


Current on a line for high-speed data

 Model with lumped elements if geometry electrically short





PI Module – Physics

 - The PDN problem and some preliminaries
- Charge delivery physics for PI design
- Why Z_{target} is used – an FPGA example
- PDN design – multi-layer PCBs with power layer area fills
- Design flow for package/PCB PI co-design




Logic Transitions and Current Draw

  - Shoot-thru current (and everything else we can't account for)
- Load charging current
- Load discharge current




LO to HI

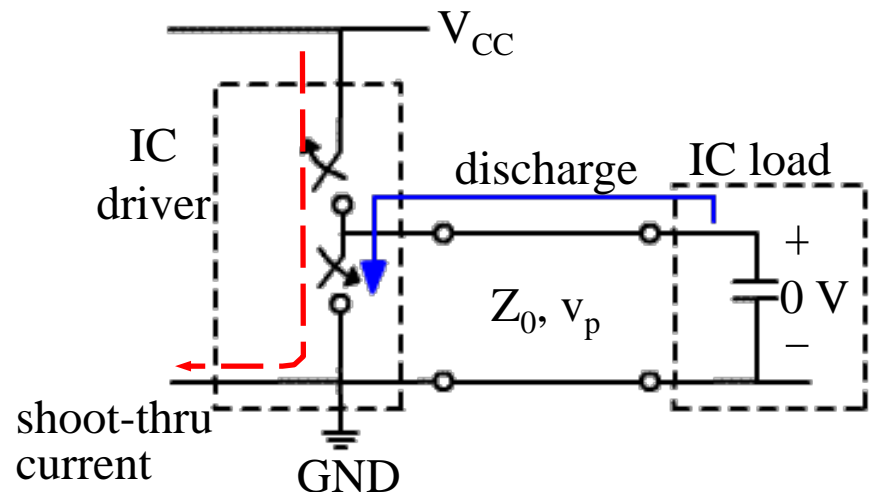


HI to LO

This charge to support IC switching must be provided by the PDN – package, PCB
 PI - 9


 
Voltage Switching/Dynamic Current Draw Disturbances



 Dynamic current on power net causes disturbance and can lead to faulty switching, a source of jitter, and trouble in general




T_1 and T_2 are not simultaneous

 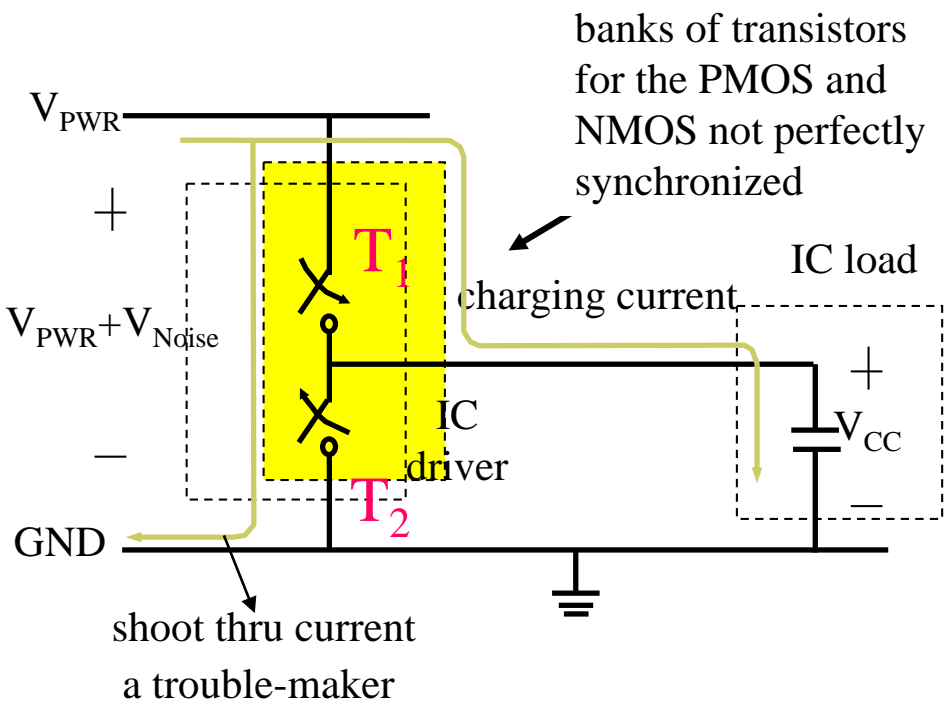


The Objective and Guiding Physics: Conduction Current Path results in Inductance

Looking from the IC

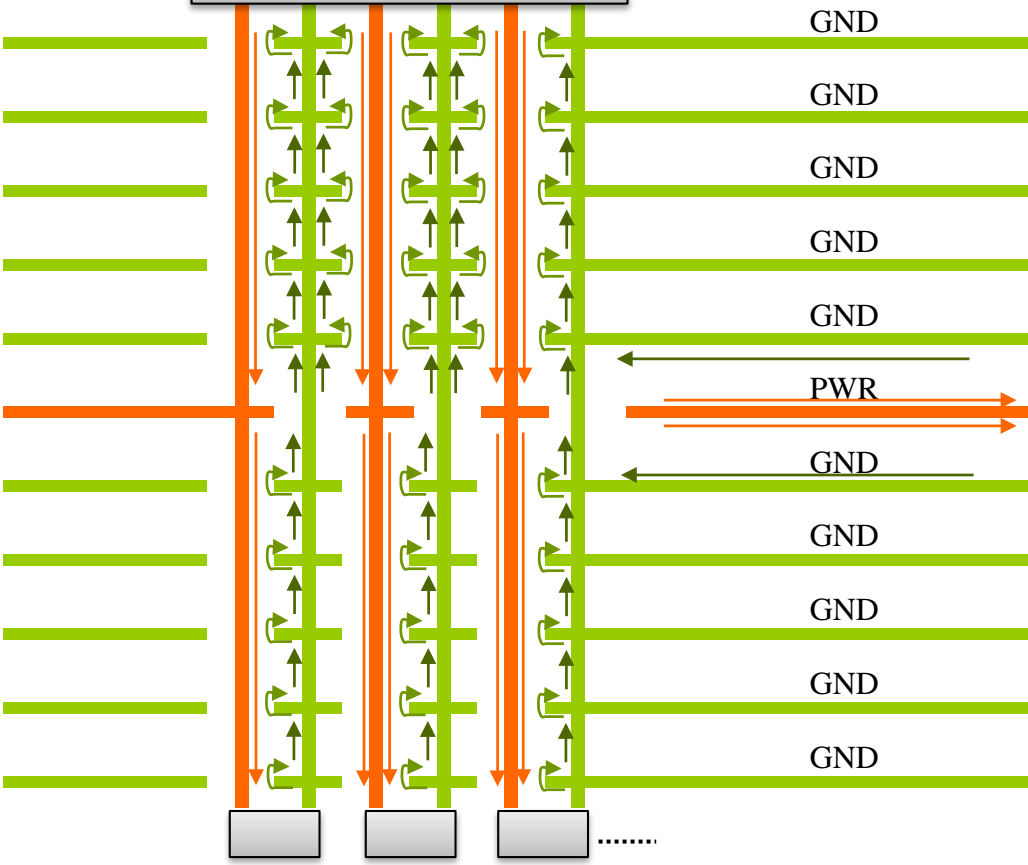

Decoupling capacitors sharing IC vias

Top decoupling capacitors

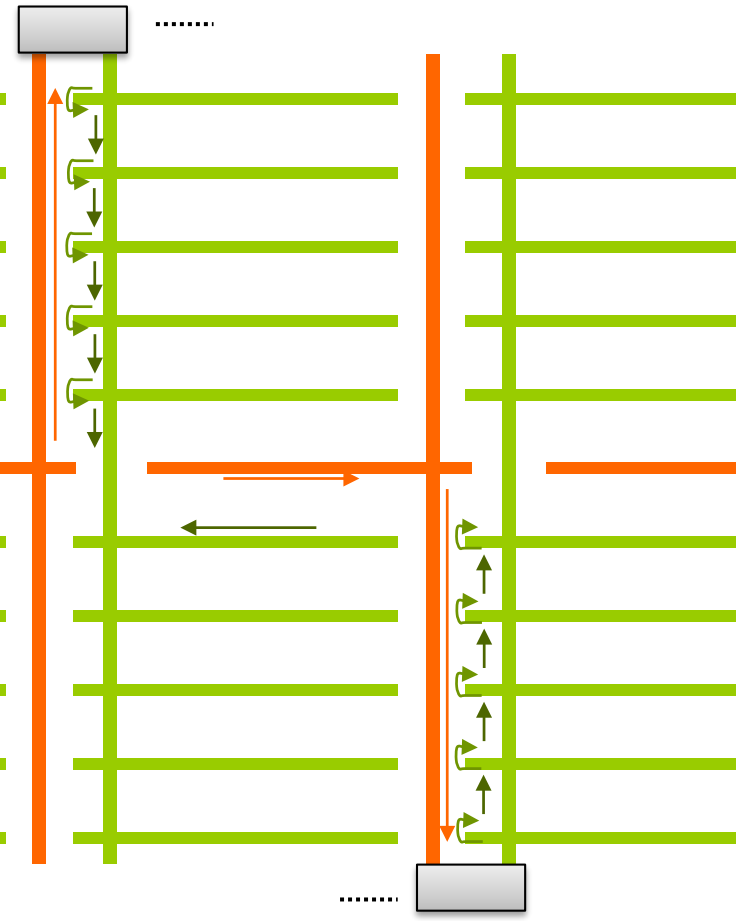


Bottom decoupling capacitors

The Objective and Guiding Physics: Conduction Current Path results in Inductance

Looking from the IC



Top decoupling capacitors

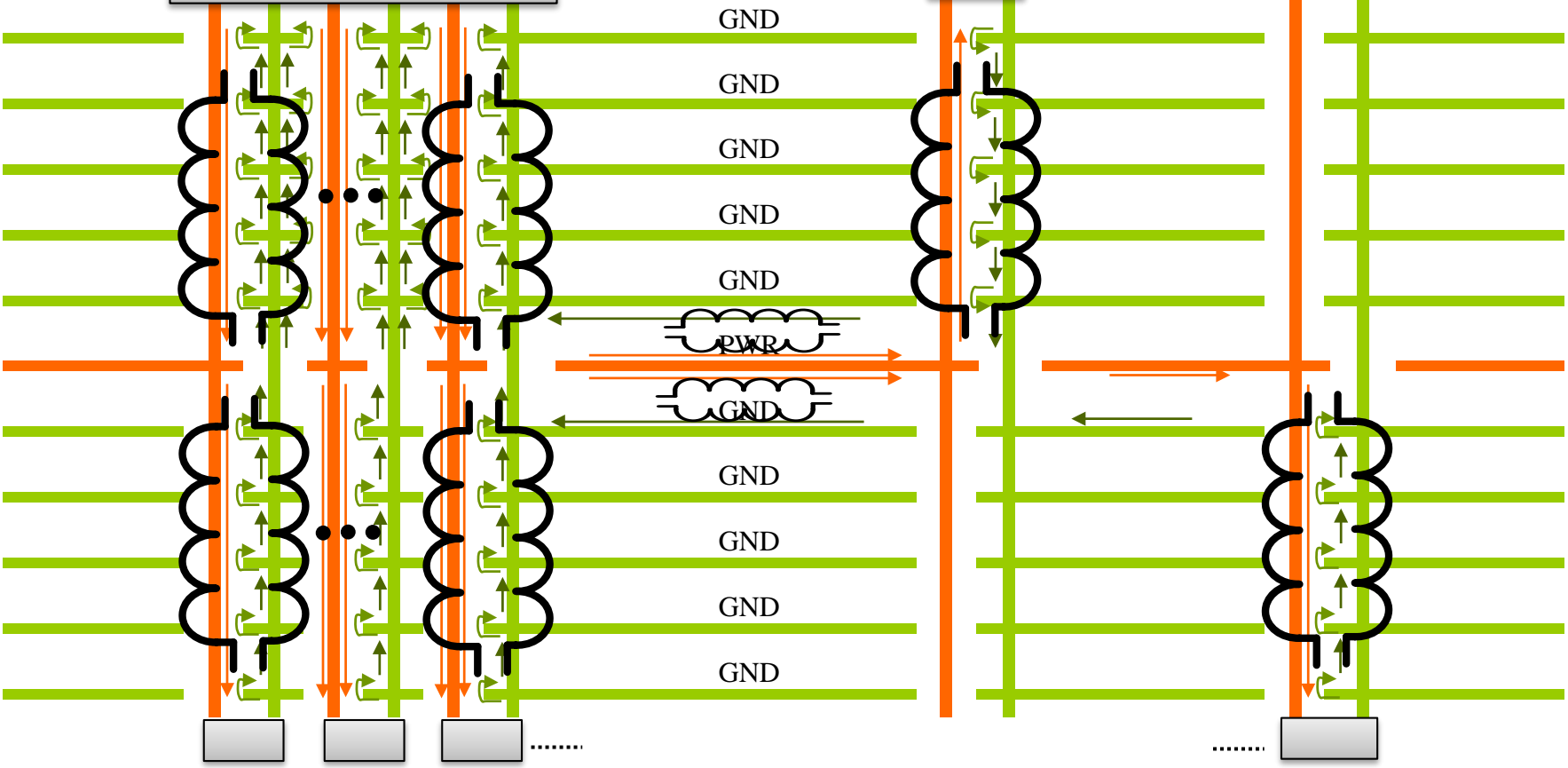


Decoupling capacitors sharing IC vias

Bottom decoupling capacitors

Key Point – Current Path and Inductance

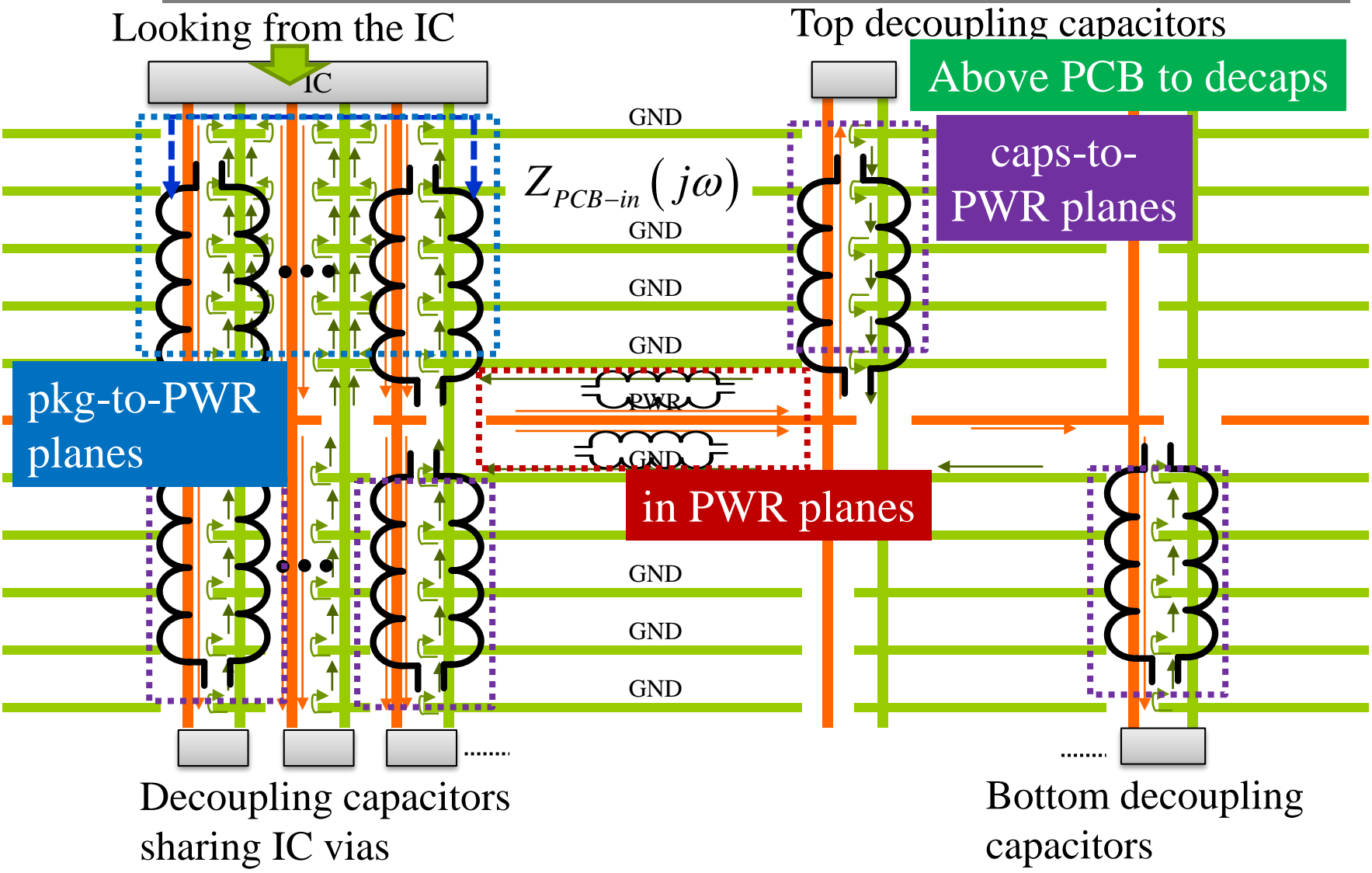Four contributions (current path pieces) to the $Z_{P\text{DN}}$ inductance




The Objective and Guiding Physics: Current Path results in Inductance

And a (relatively) Simple Z_{PDN}

Z_{PDN} 17 IC Power Pins

PCB Example
 (no package or
 die here)

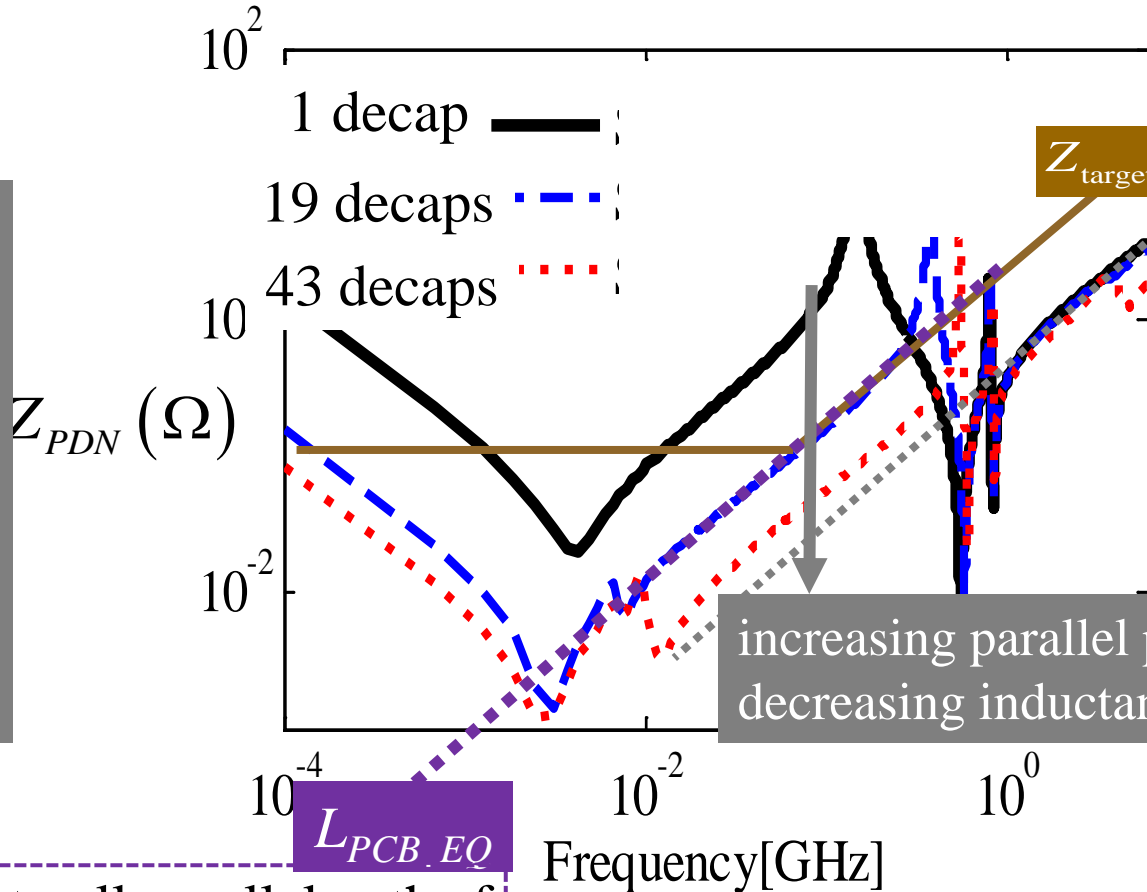Engineer
 L_{PCB_IC} and
 L_{PCB_EQ} to
 meet the
 target
 impedance



L_{PCB_IC}
 Due to vias
 in PCB
 connecting
 package to
 PCB PDN
 area fills

increasing parallel paths,
 decreasing inductance

$L_{PCB_IC} + L$ due to all parallel paths for
 decoupling capacitors

Ideally for PDN Design

1. Develop noise voltage specifications for the PCB or at the package connections (specs in TD, but can transform to FD)


$$V(\omega) = Z_{PDN}(\omega) \times I_{IC}(\omega)$$

2. Calculate the dynamic current draw

3. THEN the PCB/package PDN $Z_{PDN}(j\omega)$ can be engineered to meet noise voltage specifications

- Plane stackup, area fills, materials
- Number of decoupling capacitors
- Location, pattern, values and package size of SMT decoupling capacitors

The Reality for Dynamic Current Draw

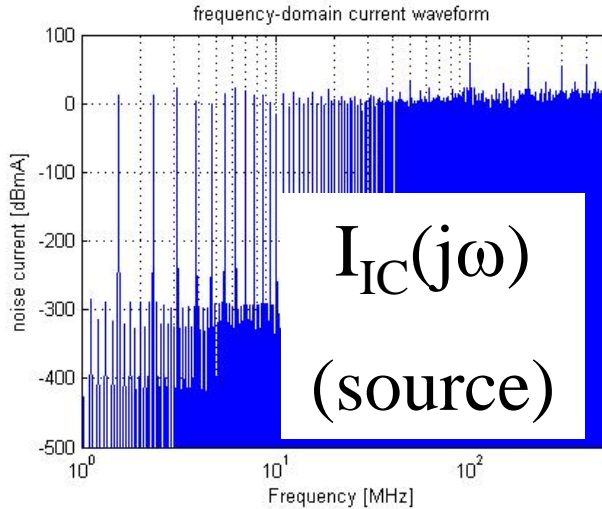


X

Determining the dynamic current draw is difficult


- Tool – in-house or commercial
- Approximate current draw waveform – pulse width, pulse amplitude, pulse sequence

and then specify Z_{target}

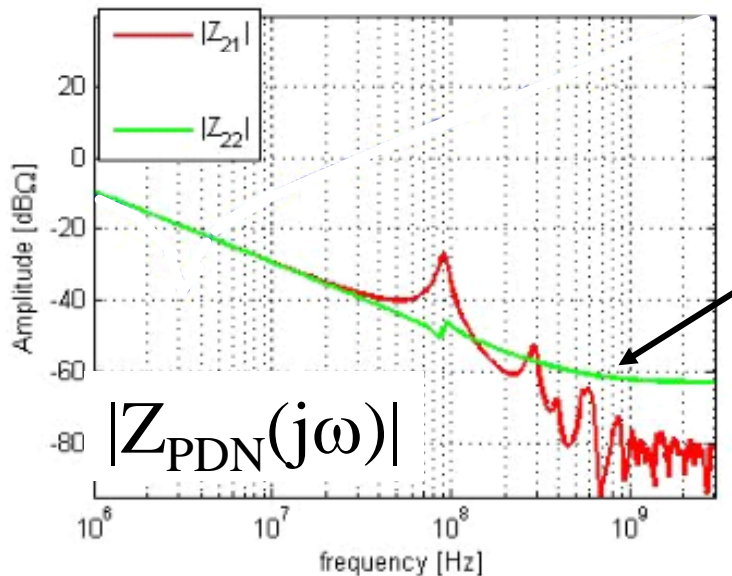

$$V_{PDN}(\omega) = Z_{PDN}(\omega) \times I_{IC}(\omega)$$
 
$$v_{PDN}(t) = F^{-1} \{ V_{PDN}(j\omega) \}$$




Engineering $|Z_{PDN}(j\omega)|$ - the Alternative

- ## Choices for PCB PDN design
- Layer stackup, area fill dimensions, and plane separation (maybe)
 - Number, value, pattern, location (top/bottom), proximity

work at these design decisions with a limited knowledge of $I_{IC}(\omega)$

$$V_{PDN}(\omega) = Z_{PDN}(\omega) \times I_{IC}(\omega)$$



Select $|Z_{PDN}(j\omega)|$ to meet noise voltage specifications

 

The concept of target impedance – not entirely satisfactory, but since the physics are dominated by inductance, there will be a limiting value. PI - 17


Key Point – Use Z_{target} for Design

 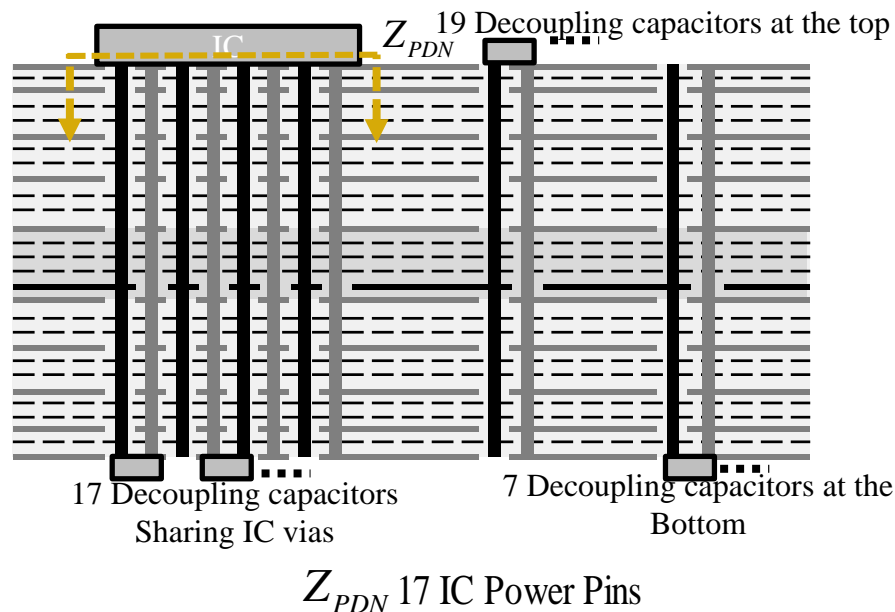- Design choices (related to geometry)
 - Layer of power net area fill on PCB (and GND power return)
 - Decoupling capacitors will be driven by achieving a specified Z_{target}
- The PDN impedance behavior in frequency is dominated by inductance (with some lumped element resonances) and use design choices to lower inductance in a frequency range corresponding to current path geometry




PI Module – Physics

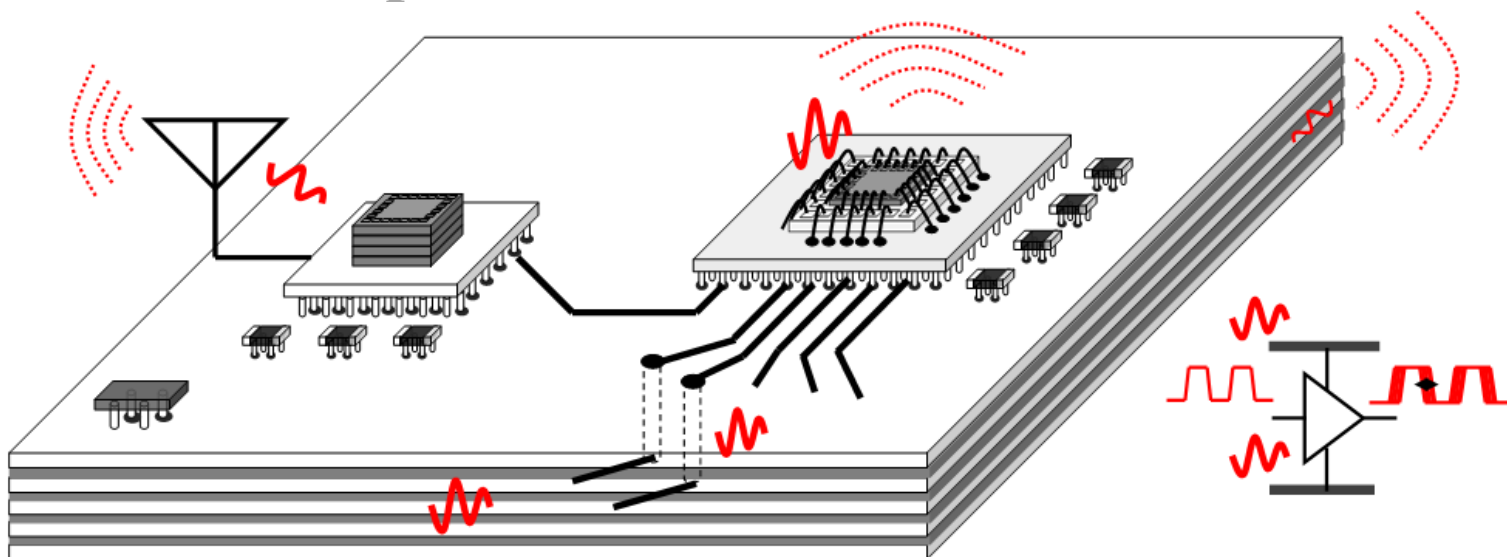- The PDN problem and some preliminaries
- Charge delivery physics for PI design
- PDN design – multi-layer PCBs with power layer area fills
- Design flow for package/PCB PI co-design
- an FPGA example



 Power Plane and Capacitor Location Matrix




— Power Net under test

— Reference Net

— Floating Net


L_{high} – Power Plane Location in Layer Stack

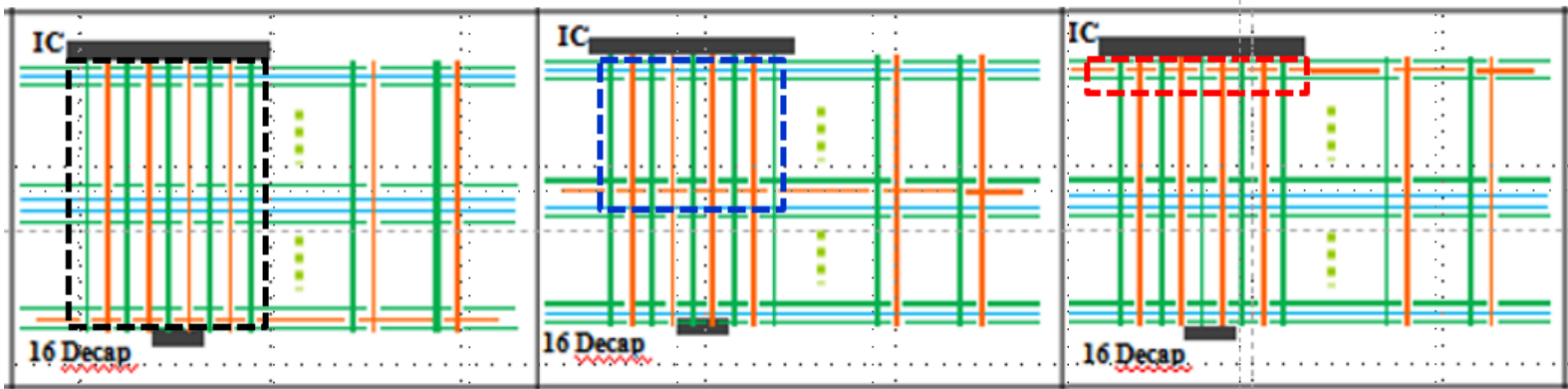Power planes – bottom Power planes – middle Power planes – top



— Power Net under test — Reference Net — Floating Net


Z_{PDN} Bottom Caps - Under the IC

 



Decreasing current path and inductance from package balls to PDN power layer net

Power layer closest to the IC minimizes IC to power plane inductance. (Recall that $j\omega L_{PCB_IC}$ is the impedance limit above a few MHz.)



Capacitor Location – Top, Bottom, at IC

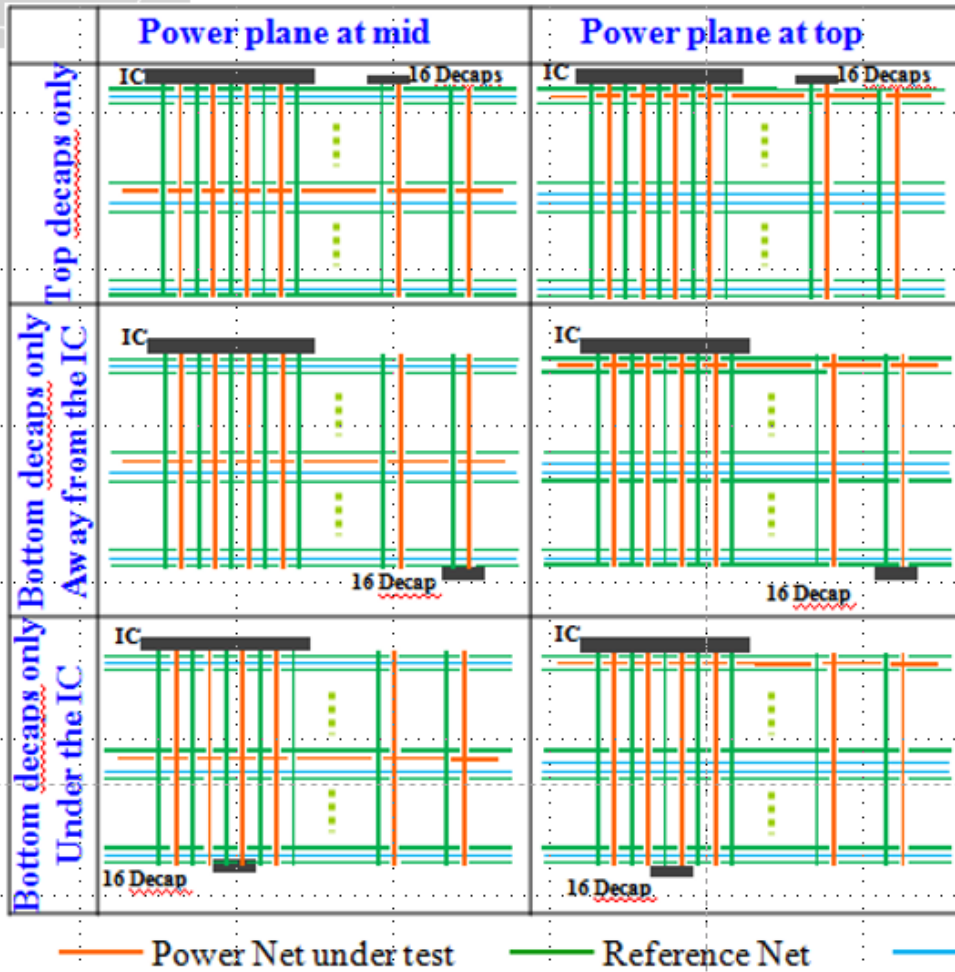

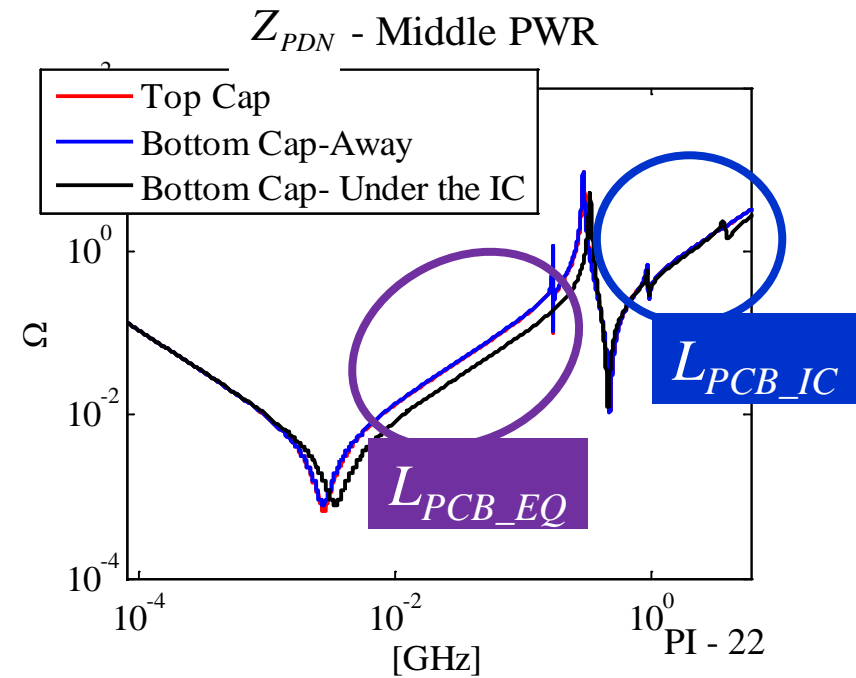 Capacitors placed on the side closest to the power plane reduces the inductance from the capacitor to power plane and L_{EQ} . The current path length/area is smallest.





  L_{EQ} – Power Plane Location in Layer Stack



L_{PCB_EQ} is also decreasing because the L from the decoupling capacitors to the power planes AND the package balls to the power planes is decreasing

Key Points

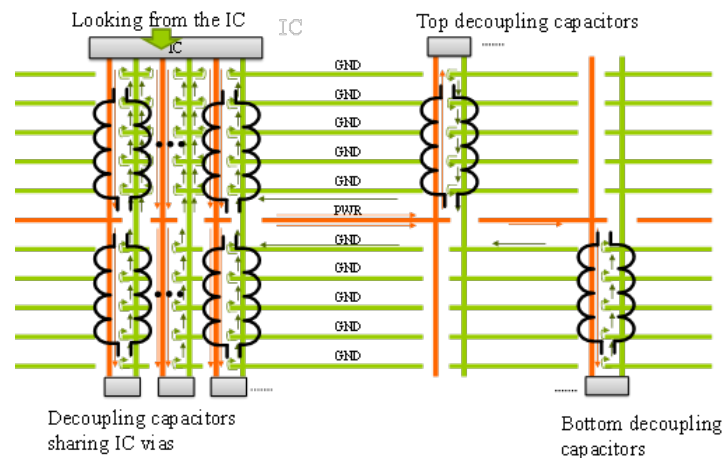 

- The shape of the Z_{PDN} curve is relatively simple, even though the geometry of the PDN on a multi-layer PCB is complicated
- The current-path physics governing the impedance are dominated by inductance and lumped element resonances above approximately 1 MHz
- The inductance is dominated by the current path – geometry “length/area” (series inductance), and the number of parallel paths (parallel inductance) and this will drive the design approach (“small loops and many loops”)




- Where power layers are located in stackup
- Package ball pitch
- Decoupling capacitor interconnect

- Number of PWR/GND vias in package
- Number of decoupling capacitors

PI Module – Physics

 - The PDN problem and some preliminaries
- Charge delivery physics for PI design
- PDN design – multi-layer PCBs with power layer area fills
- SMT decoupling
- Design flow for package/PCB PI co-design




Two Approaches for SMT Decoupling

- Use an array of capacitor values:
 - This may be the best known approach in the signal integrity design community
 - Rationale: to maintain a flat impedance profile below a target impedance over a wide frequency range
 - Typically a logarithmically spaced (10, 22, 47, 100, 220, 470nF, etc.) array of 3 values per decade.
- Use a large capacitor value in the package size
 - This is less well-known, but an approach in the EMI design community
 - Rationale: to keep impedance as low as possible, less emphasis on a target impedance and a flat profile

Decoupling Strategy – Geometry

Capacitor Description					# of Caps		
Value (nF)	ESR (mΩ)	ESL (nH)	Inter-connect (nH)	Type	A	B	B1
3.30E+06	60	15	2	E-lytic	1	1	1
100000	11	1.4	2	1812	4	16	16
47000	12	1.4	2	1812	4		
22000	14	1.4	2	1812	4		
10000	16	1.4	2	1812	4		
4700	16	0.5	1.6	0603	4	24	
2200	19	0.5	1.6	0603	4		
1000	23	0.5	1.6	0603	4		
470	29	0.5	1.6	0603	4		
220	23	0.5	1.6	0603	4		
100	30	0.5	1.6	0603	4		
47	40	0.4	1.35	0402	4	20	44
22	55	0.4	1.35	0402	4		
10	75	0.4	1.35	0402	4		
4.7	104	0.4	1.35	0402	4		
2.2	211	0.4	1.35	0402	4		
Total # of Decoupling Capacitors =					61	61	61
Total Capacitance (milliF) =					4.05	5.01	4.90

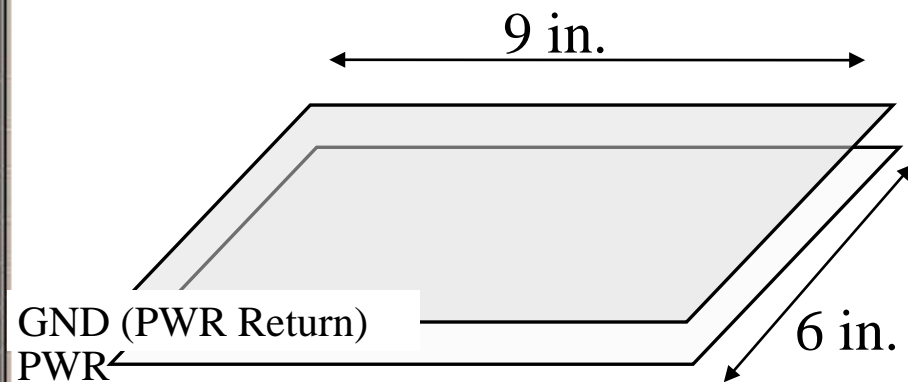


$t=10$ mils.

$\tan \delta = 0.02$

$\epsilon_r=4.5$




Approaches for SMT Decoupling Values

 

- Approach A : values of decoupling capacitors logarithmically spaced, i.e. 3 values per decade: 10, 22, 47, 100, etc.
- Approach B : largest values of decoupling available in two package sizes, i.e., 0603 and 0402
- Approach B1 : largest values of decoupling available in one package size, i.e., 0402.


Both approaches can meet the design specs relative to the target impedance

Practices for Mounting SMT Capacitors


 
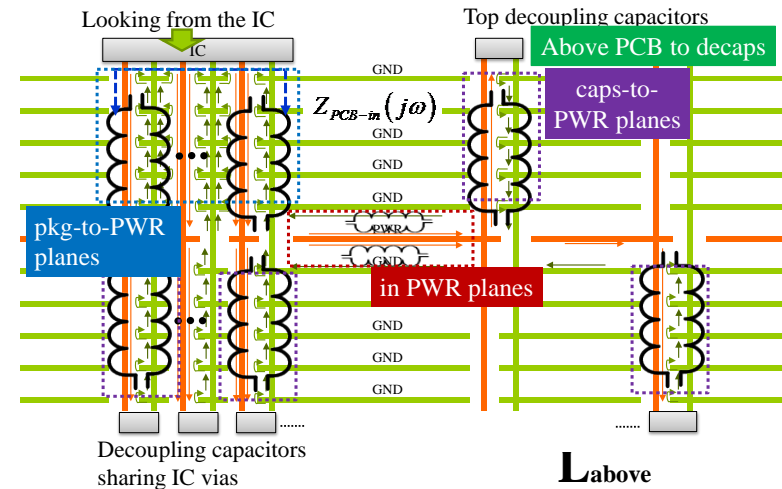
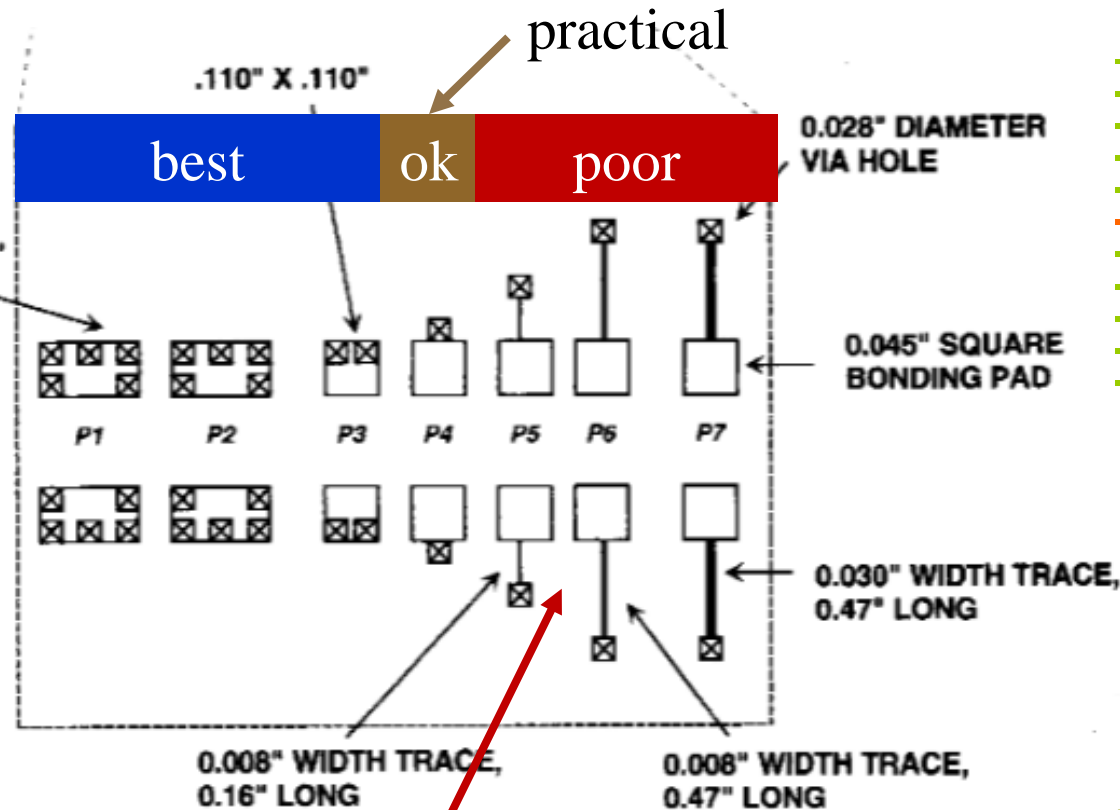


Adding trace length, adds inductance to the interconnect:

 - "loop area" above the planes – L_{above}
- Area between the power and GND return vias vertically connecting to the PWR planes





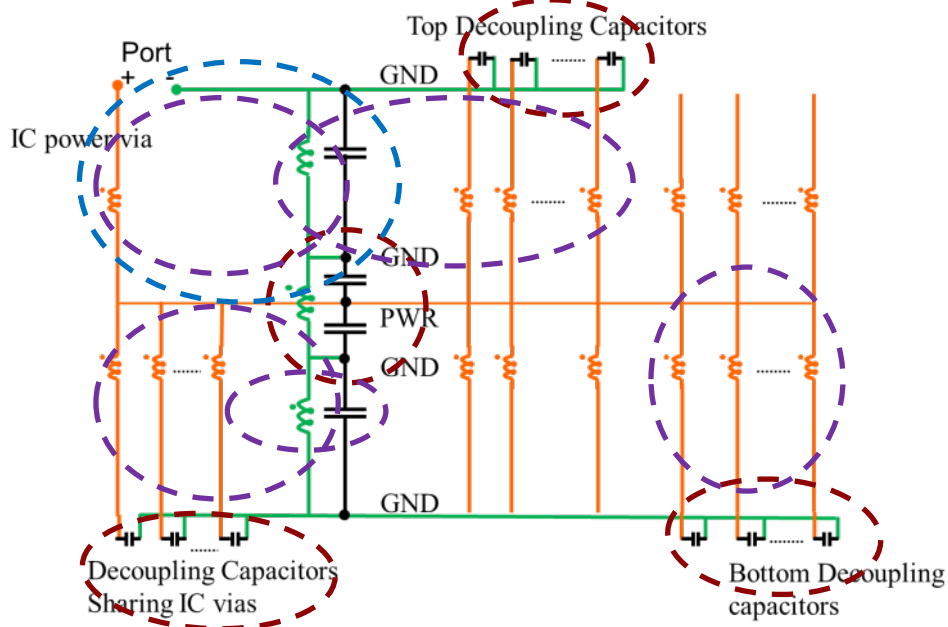 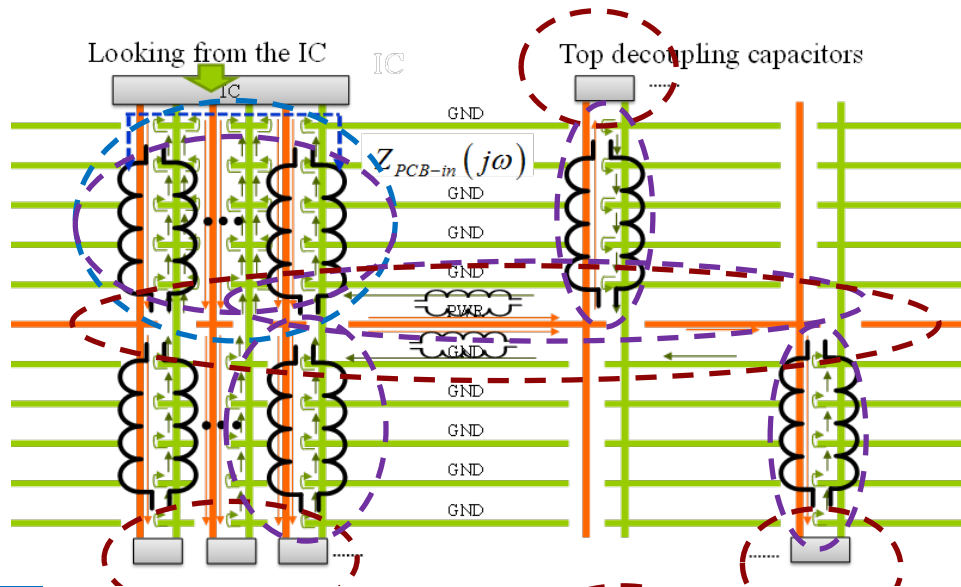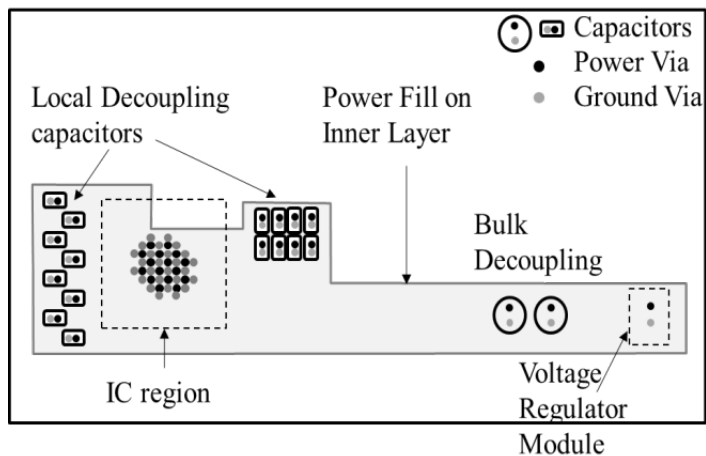Design Geometry, Current Path, and Z_{PDN}





Design Implications

 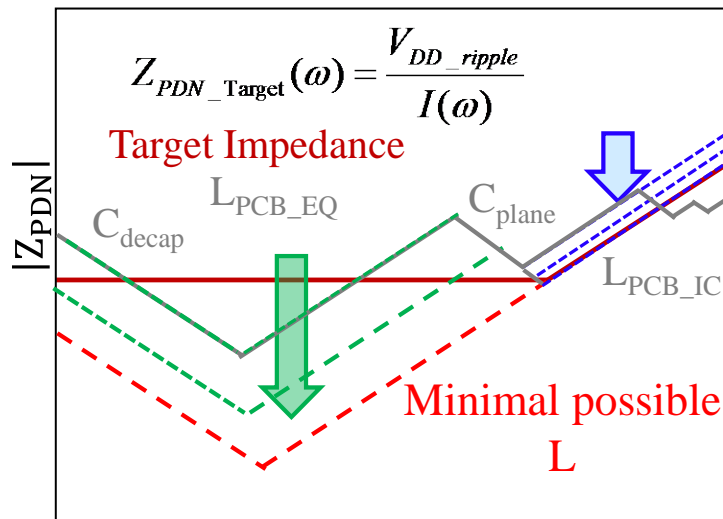- PWR/GND plane pair nearer to the IC in stackup will minimize L_{PCB_IC} from package balls to power net area fill (smaller loop)
- PWR/GND plane pairs closely spaced will reduce L_{PCB_plane} .
- Place caps close to the power layer to minimize the inductance from the capacitor to the power net area fill layer, i.e., L_{PCB_decaps} . (minimize the loop)




Design Implications

- Placing caps on the underside of PCB opposite package can benefit the design
 - if the path(s) from the package to bottom of the PCB is comparable to the pkg/planes/decap path due to mutual inductance of the via grid power pattern
 - Unless the pkg/planes/decap path is shorter due to PWR/GND near package in stackup
- Power and ground vias placed adjacent to the caps reduces the inductance in the current return path (or in the bonding pads). (smaller loops)
- Capacitor arrangements that utilize mutual inductance, e.g., doublet, or 3-terminal capacitor, can significantly reduce L_{PCB_decaps} .
- Using a large capacitance value in a given package size can meet the low-frequency target impedance, and inductance can be reduced by adding more capacitors. (many parallel paths)

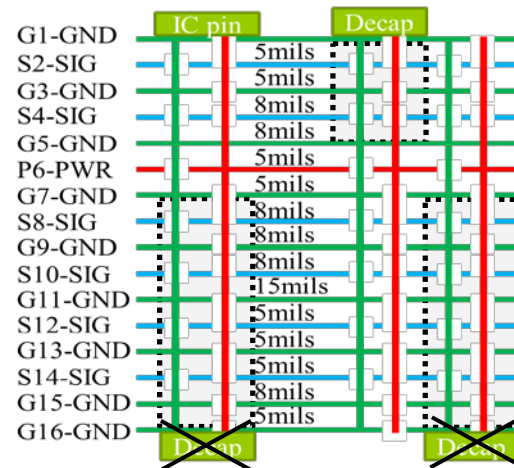 



PI Module – Physics

 - The PDN problem and some preliminaries
- Charge delivery physics for PI design
- PDN design – multi-layer PCBs with power layer area fills
- Time-domain and frequency domain through a circuit model
- Design flow for package/PCB PI co-design
- an FF ~






Circuit Model for PCB PDN

Based on physics-based circuit model

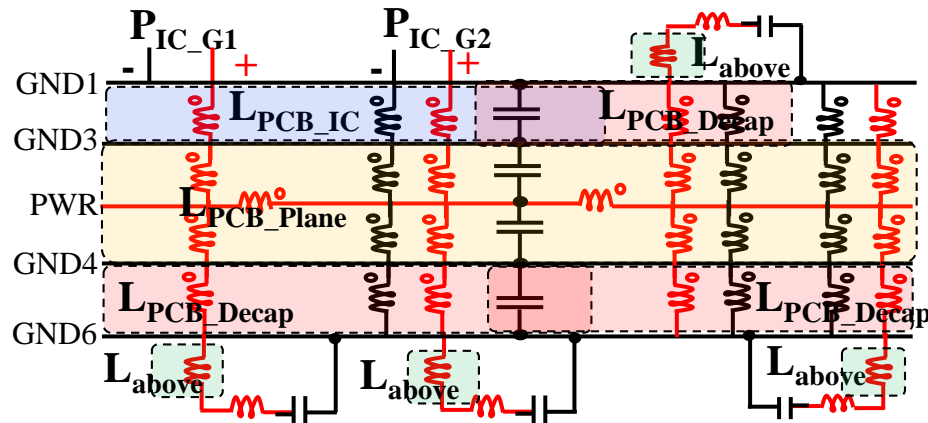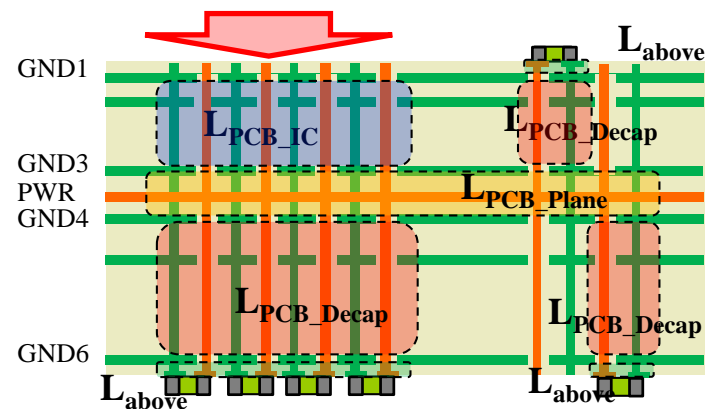

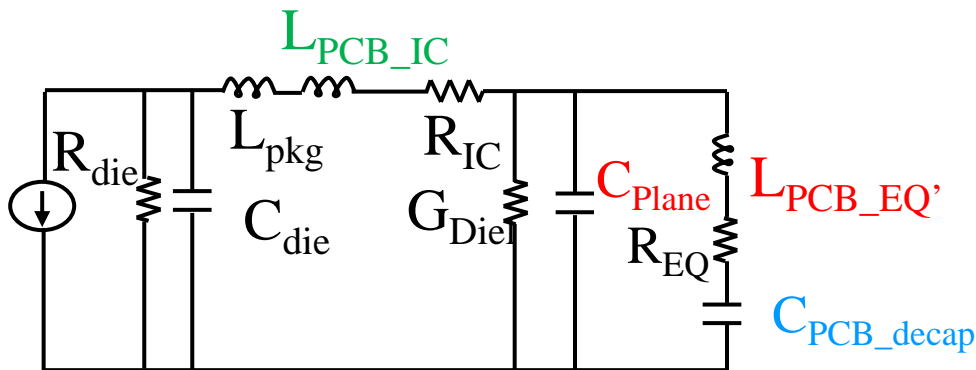  
Topologically correct behavioral circuit model




$$L_{PCB_EQ}' = L_{PCB_Decap} + L_{above} + L_{PCB_Plane}$$

V_{ripple} Calculation


Voltage ripple specification

 




Switching current profile

 






Voltage ripple simulation

 


Voltage ripple mathematical calculation

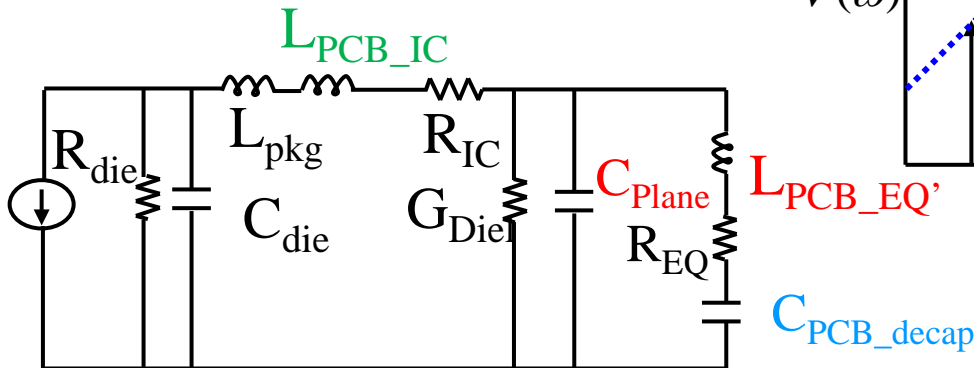  

Voltage Ripple Separation

    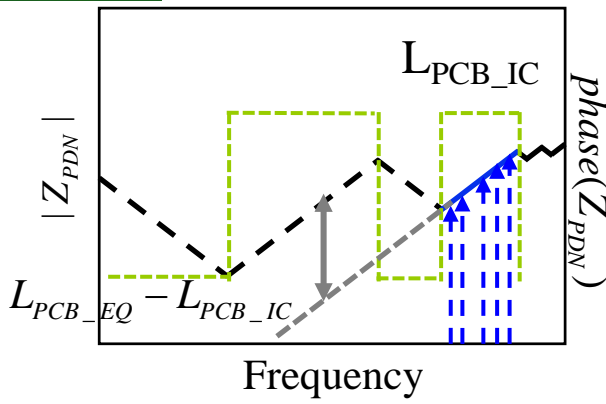


Minimal possible L


 


PI Module – Appendix

 - The PDN problem and some preliminaries
- Charge delivery physics for PI design
- PDN design – multi-layer PCBs with power layer area fills
- **Design flow for package/PCB PI co-design**
- an FPGA example



A Systematic Approach for Achieving PI

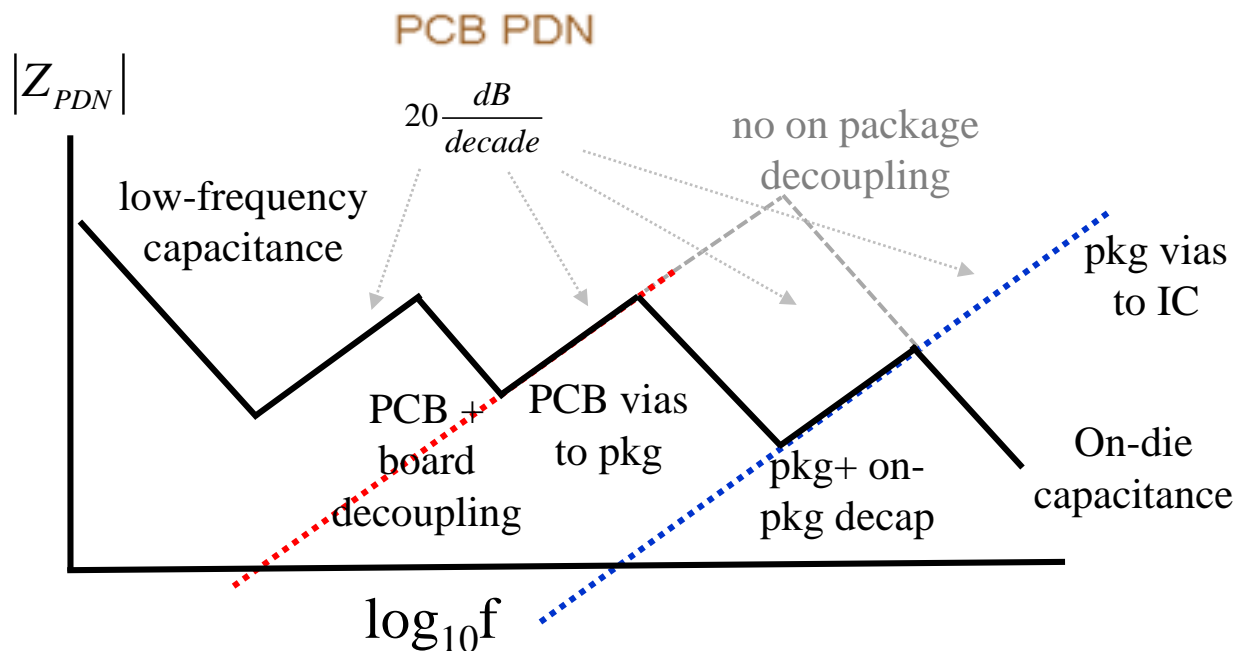 

PCB PDN Design Considerations

2a. Decoupling capacitors

- top
- bottom,
- beneath IC?

2b. Decoupling capacitor connection -

- PWR/GND via geometry
- Package size

1. Power plane(s)

- location in stack
- spacing to power return plane
- total area fill
- special materials

2a. Decoupling capacitors


- value(s)
- Number (total C)

2c. Decoupling capacitor layout

- How close to IC?
- Shape – ring IC, on one side?

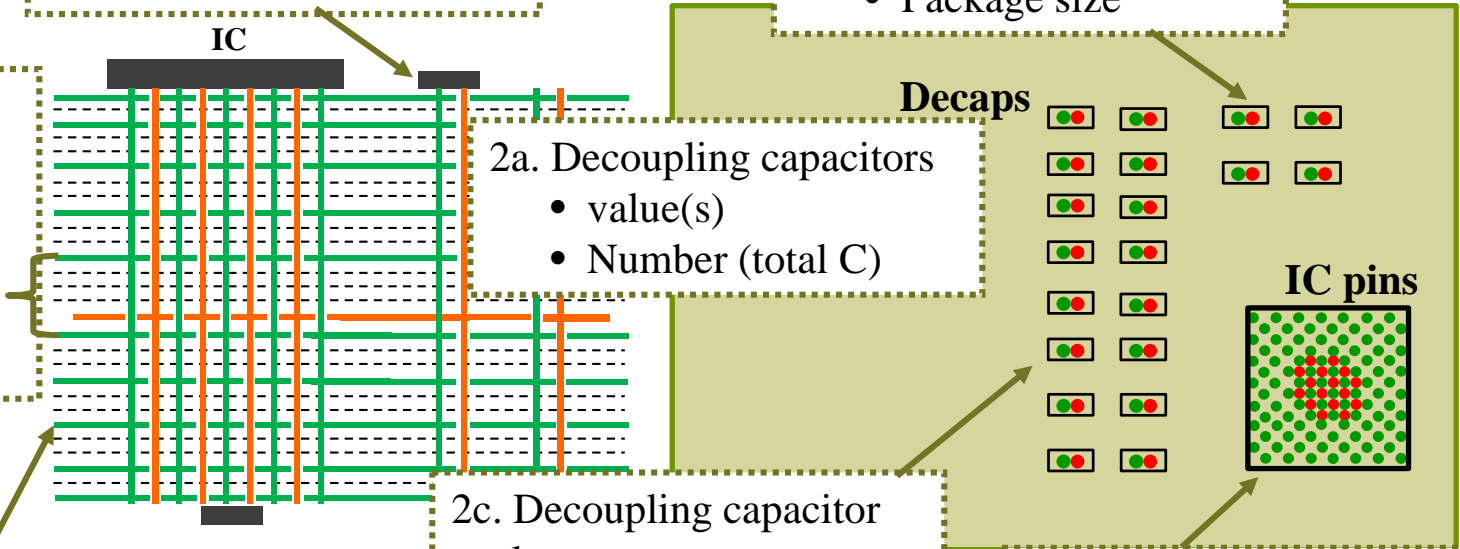3. IC PWR/GND

- Number pins
- pin pattern
- Pitch
- on-package decaps



— PWR
 — GND




Design Flow – Package

DC power determines minimum number power interconnects (IR drop, current)

Package ball **pitch** determines minimum achievable high-frequency Z_{target}

Choose **number (and pattern)** PWR/GND vias to meet high-frequency target impedance for specified **PCB power area fill layer** $\rightarrow L_{PCB_IC}$

Trade-off

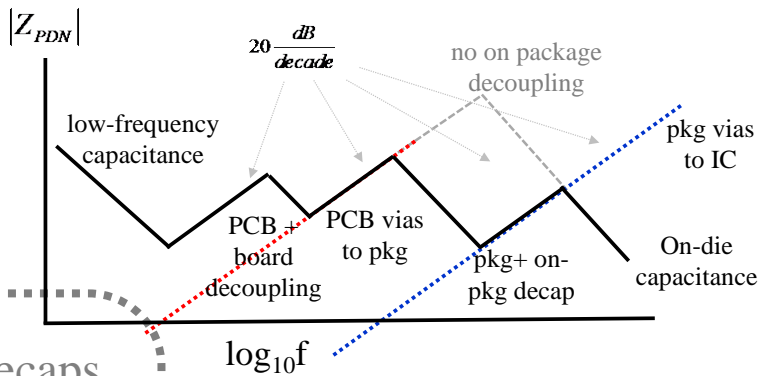  


On-package decaps reduce minimum overall achievable high-frequency target impedance seen by IC

* PCB/package co-design step

Design Flow – PCB

 Peak voltage ripple/droop determines Z_{target}



IC/ASIC PWR/GND pin-out number (and pattern) determines minimal $\rightarrow L_{high}$

Choose PWR/GND area fill layer to meet high-frequency target impedance $\rightarrow L_{high}$

Number of decaps and placement determines $\rightarrow L_{EQ}$ to meet Z_{target}

value of decaps determines low-frequency impedance to meet Z_{target}

