

Power Plane and Decoupling Optimization

Isaac Waldron




Overview

- Frequency- and time-domain power distribution system specifications
- Decoupling design example
 - Bare board
 - Added capacitors
 - Buried Capacitance
- Conclusion




Frequency Domain PDS Targets

 - Excessive impedance seen by a device drawing power from a PDS will cause power voltage to fluctuate
- On a board, impedance must be below target from DC to several hundred MHz
- Working in the frequency domain allows quick estimation of power quality



PDS Components

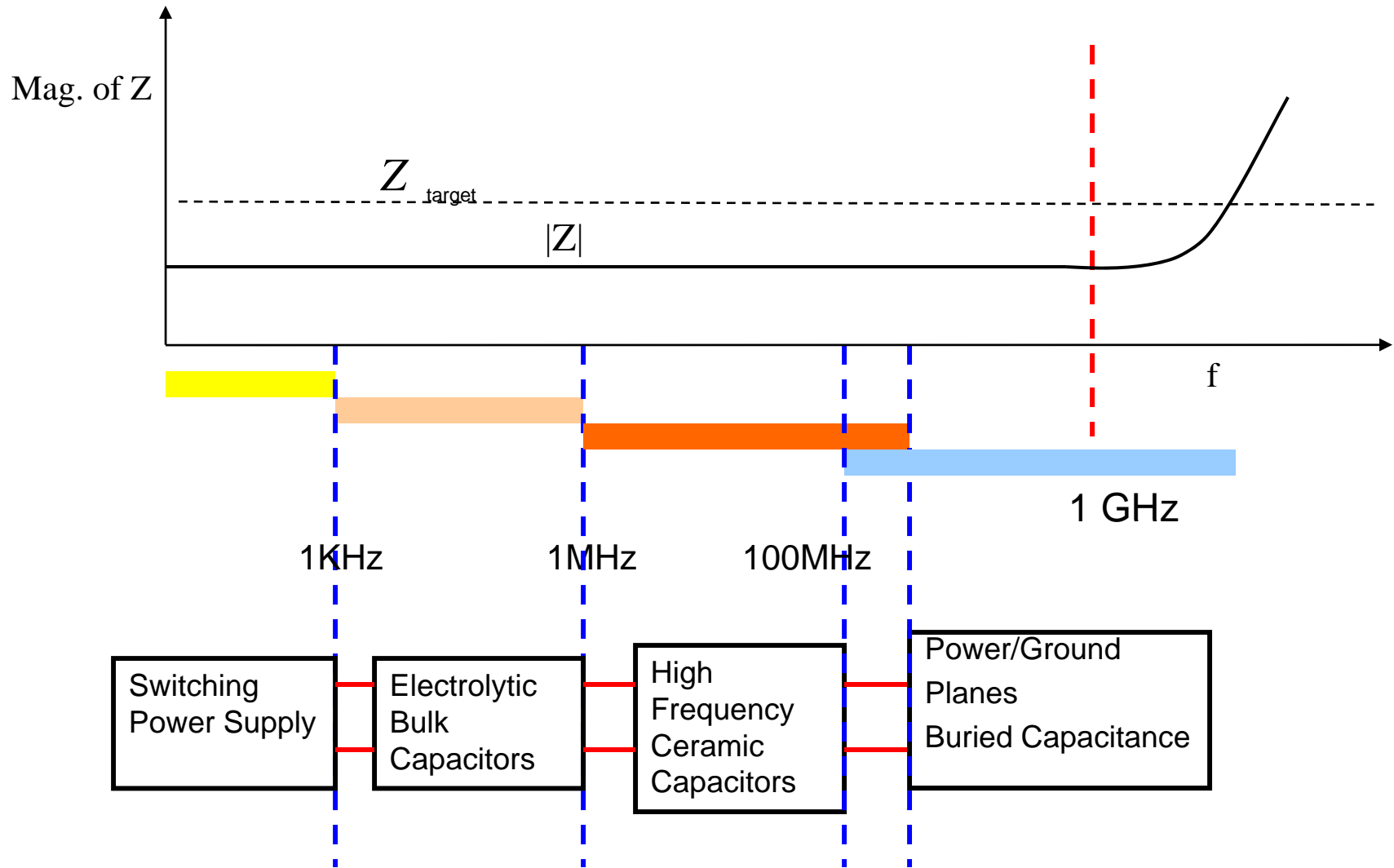


Time Domain PDS Targets


- S-parameters and impedance are calculated in the frequency domain
- Device specifications are typically given in the time domain
- Example: maximum VCC excursion 10% of nominal value
 - 1.8 V VCC has an allowable range of 1.62 V to 1.98 V



PDS Design Flow

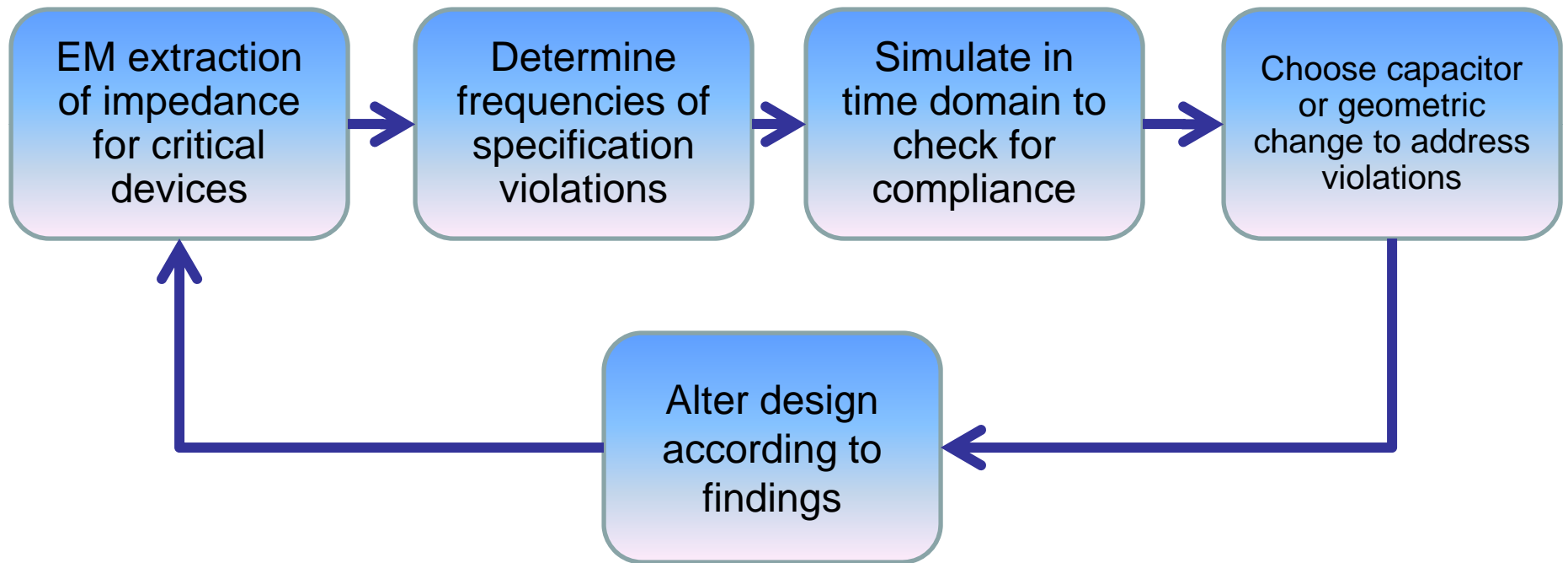

Board Imported from Layout


 


Measuring impedance at the six VCC pins on U41




Defining the Target Impedance

Package Model

  

Driver

VRM

 

- To define the target impedance we need to consider two factors:


- Peak current
 - Determines maximum impedance
- Spectral power
 - Determines cutoff frequency



Peak Current


- Peak current 37.87 mA
- Six drivers and 0.18 V maximum voltage swing:
 
$$\frac{0.18 \text{ V}}{6(37.87 \text{ mA})} = 800 \text{ m}\Omega$$




Driver Spectrum

95% of driver power is below 667 MHz

 

PDS Design Flow

 


Bare Board

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:04:51


Target
impedance 800
mOhm to 667
MHz

 




Bare Board



PDS Design Flow

 

Time Domain Schematic

 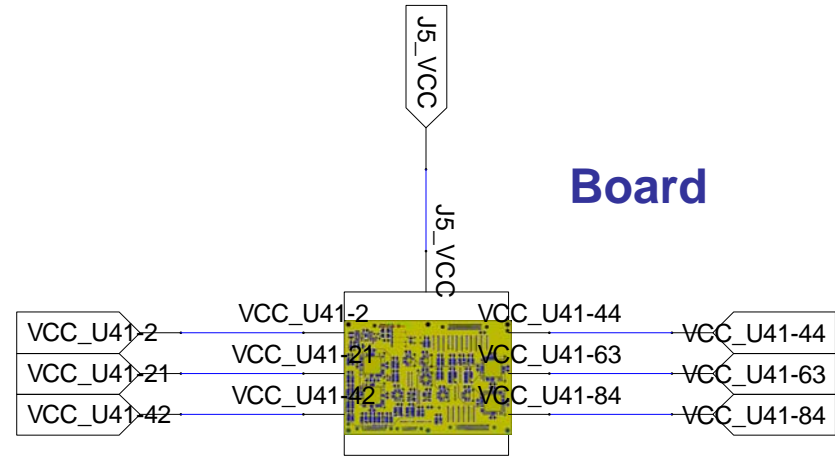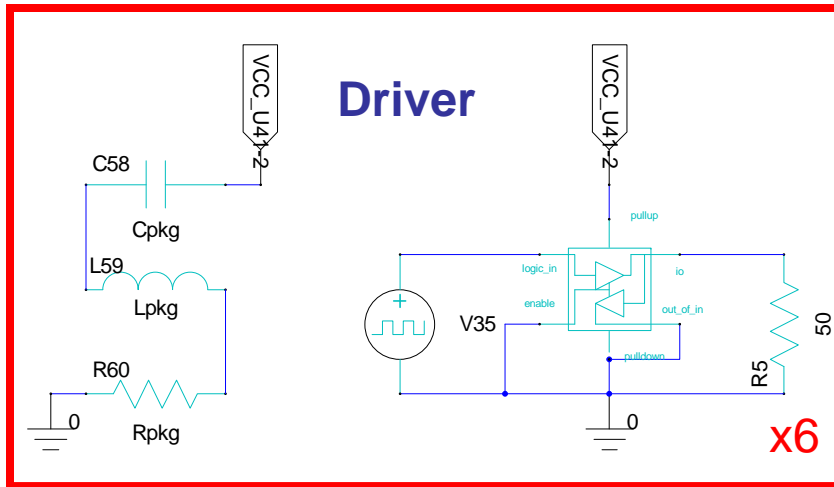


800 Mbps data rate

DDR2 IBIS driver into ideal termination used as load for PDS


Package decoupling modeled using a capacitor w/ ESR, ESL



Switching Power Noise

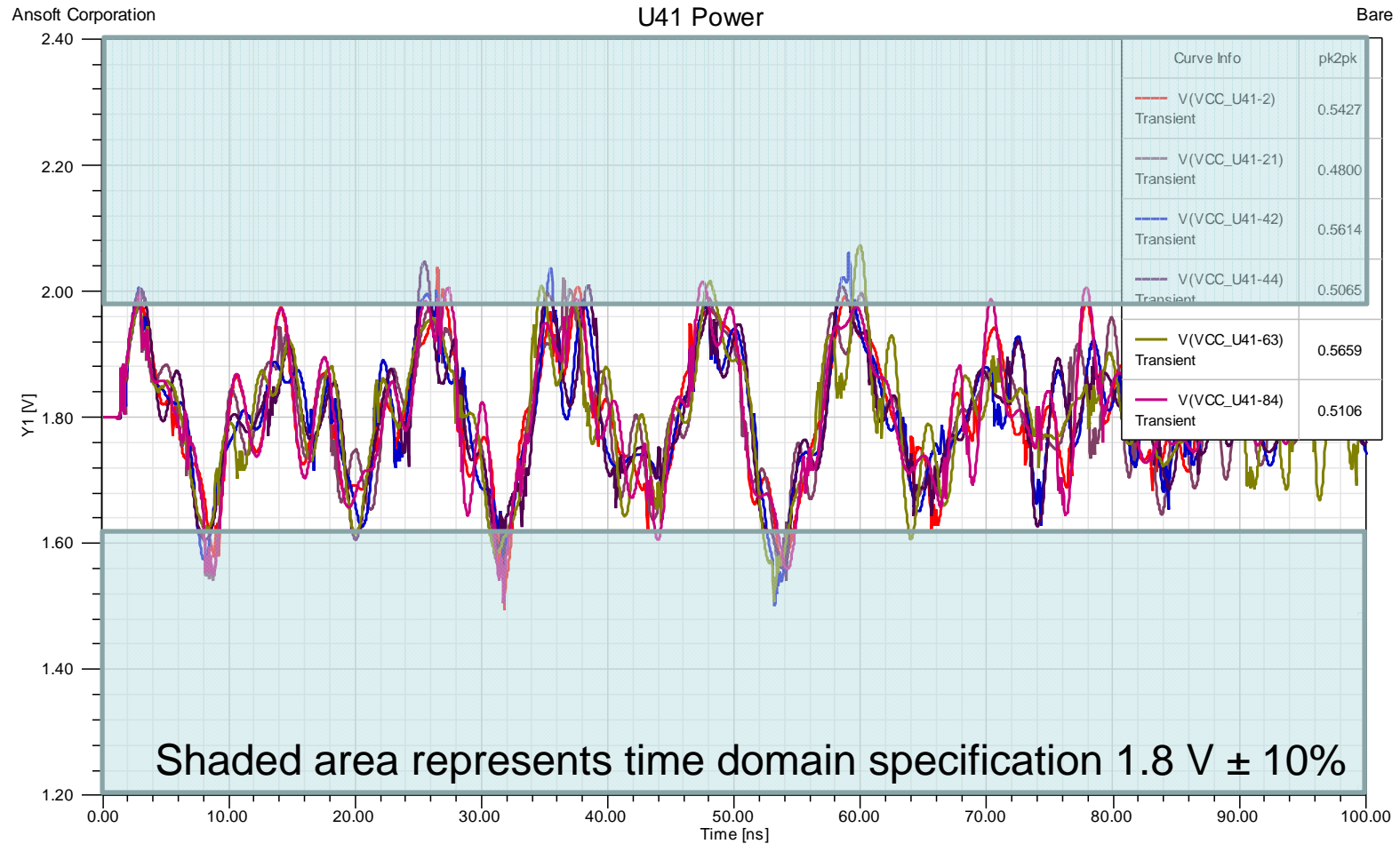


Spectral Analysis

 


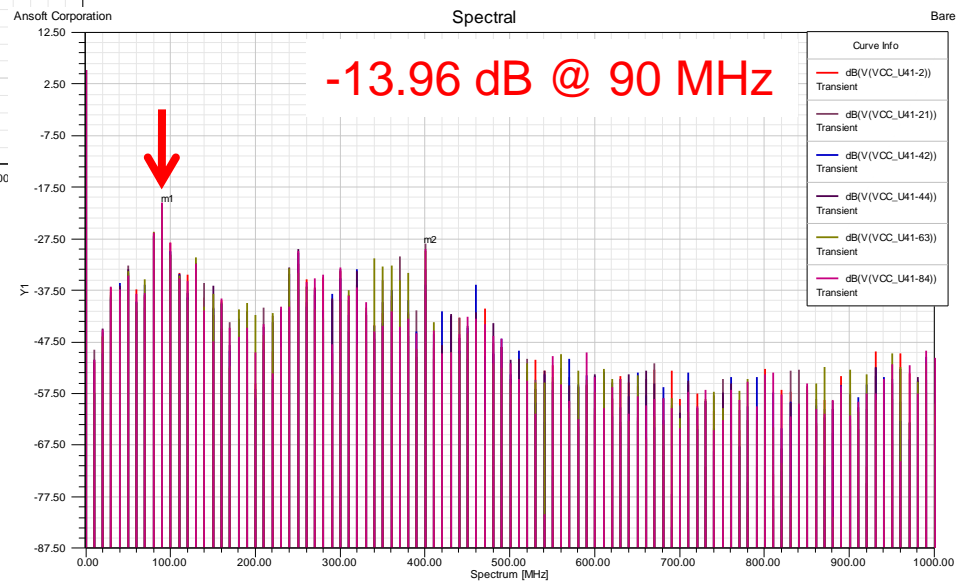11-12 ns period corresponds to frequency of 80-90 MHz

This is confirmed by the spectral plot and correlates with the ideal driver simulation shown earlier (peak @ 83 MHz)




PDS Design Flow

 


Adding Bulk Capacitors

 Added two 47 uF capacitors as specified by VRM manufacturer



PDS Design Flow

 


Bare Board vs. Bulk Capacitors

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:12:06

Target
impedance 800
mOhm to 667
MHz

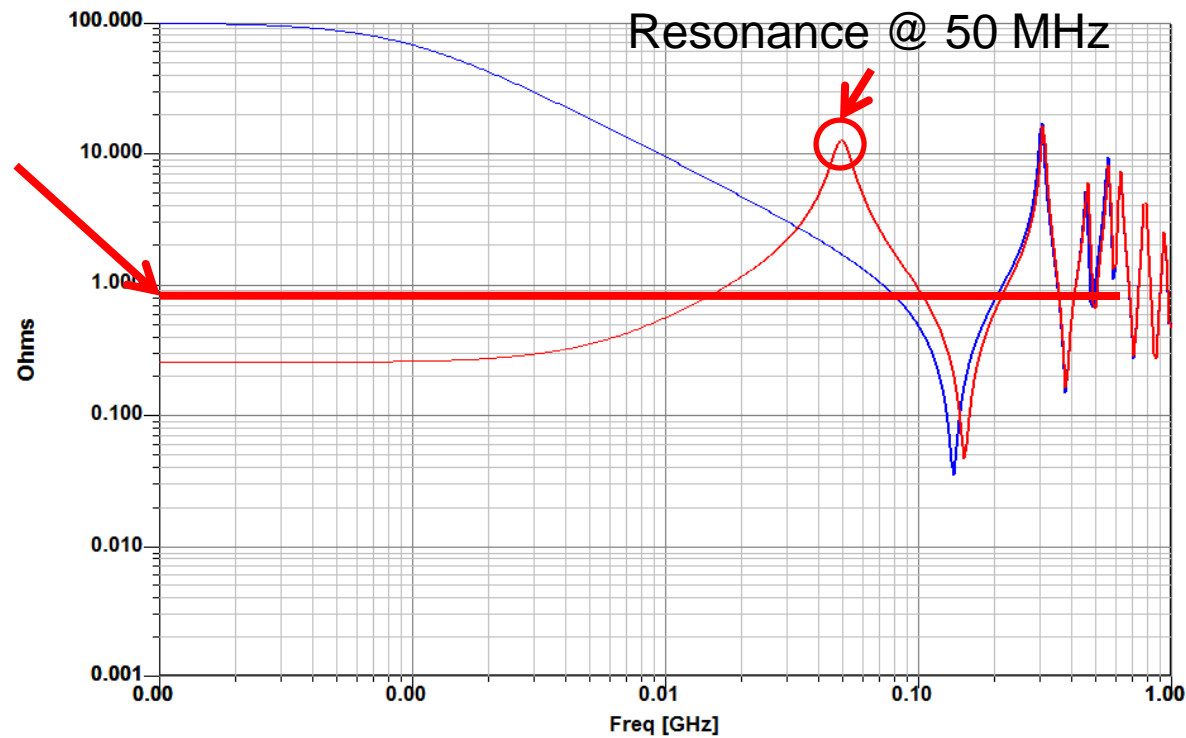

Bare Board
**Board w/
Bulk Caps**




Bulk Capacitors

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:13:41


Target
impedance 800
mOhm to 667
MHz

 


Board w/
Bulk Caps




PDS Design Flow

 

Switching Power Noise

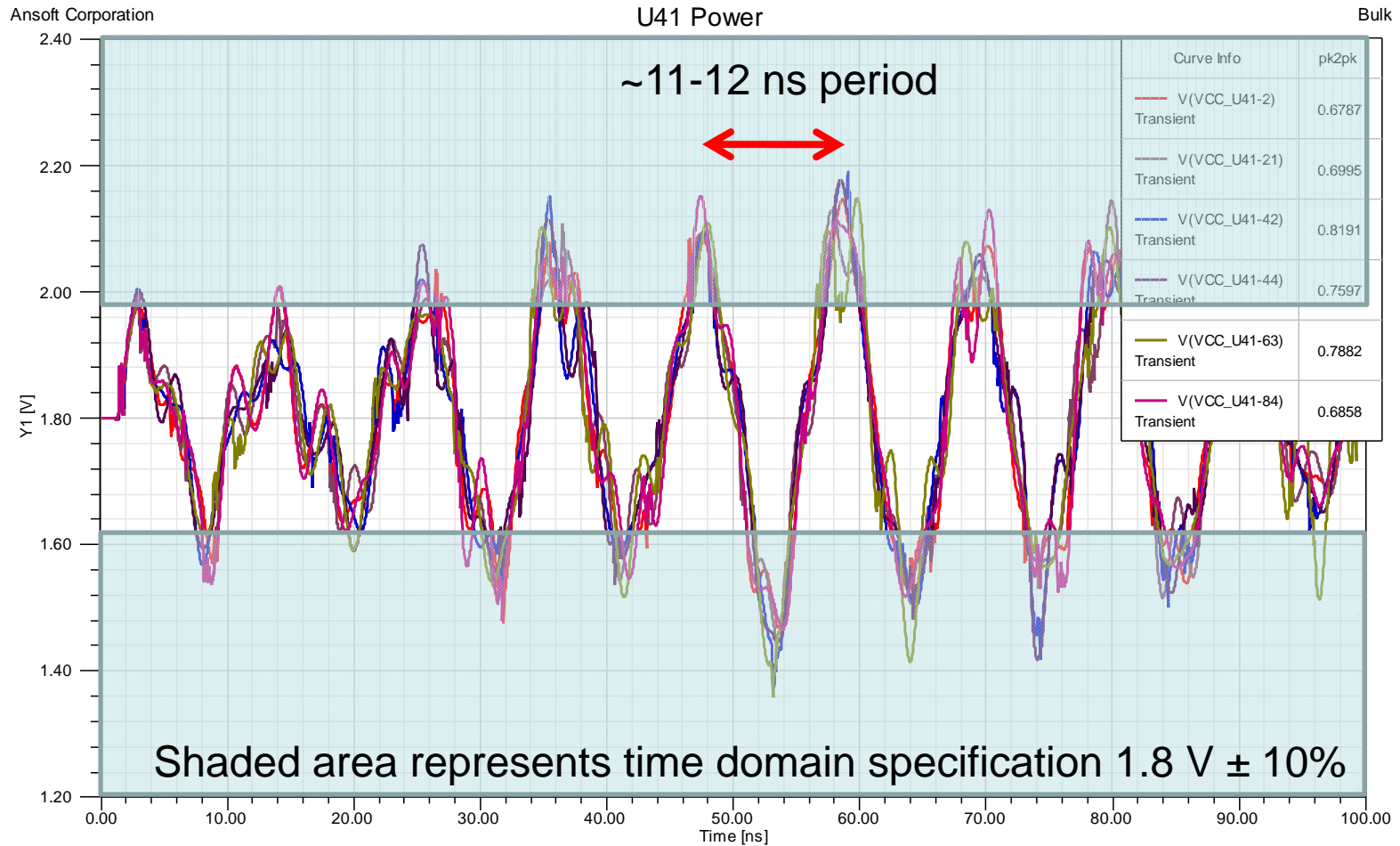


Spectral Analysis

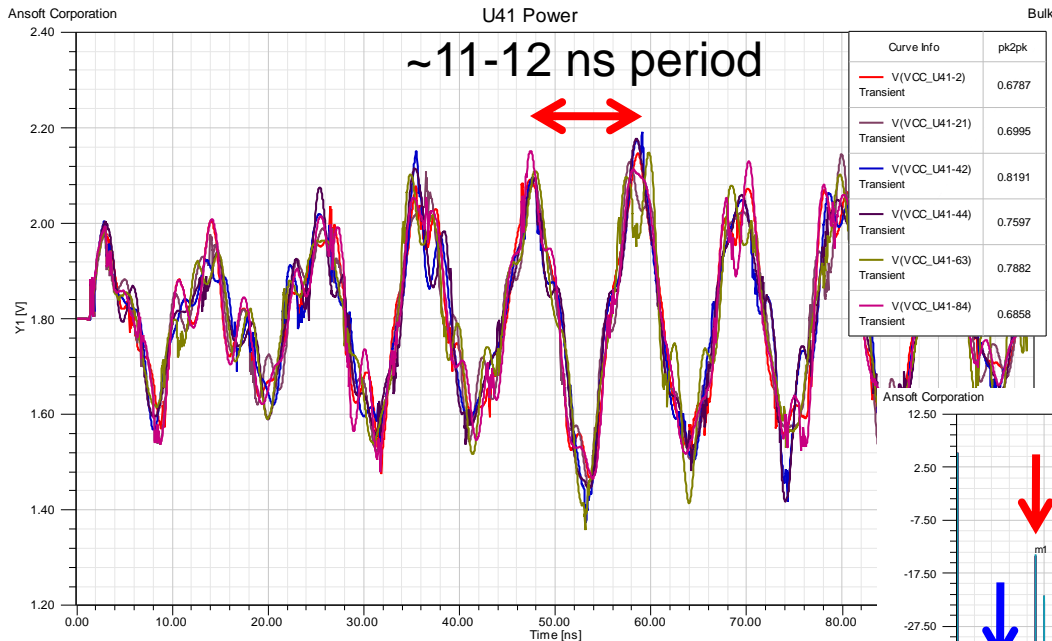


Same 11-12 ns period as exhibited by bare board

 
Note that resonance @ 50 MHz is not excited due as indicated by low spectral content at that frequency



Resonance at 50 MHz

 

PDS Design Flow

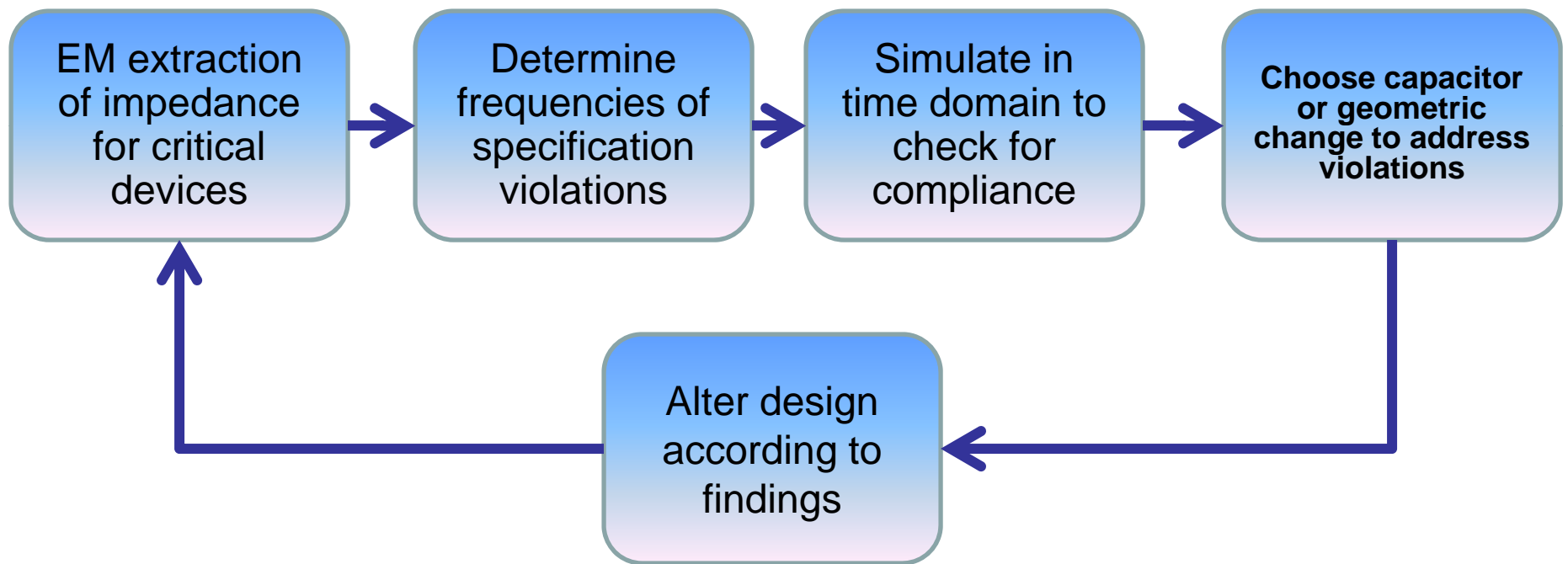


Choosing a Capacitor

- To reduce the effect of a resonance, choose a capacitor with a low impedance at the resonant frequency

28 May 2008

Ansoft Corporation
08055C223KA Z Parameter Magnitude Plot
0805

10:00:06

 


Added HF Capacitors

- 52 20 nF capacitors were added across the board to reduce high-frequency impedance and to cancel resonance at 50 MHz



PDS Design Flow

 


Bulk vs. HF Capacitors 1

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:14:54

Target
impedance 800
mOhm to 667
MHz

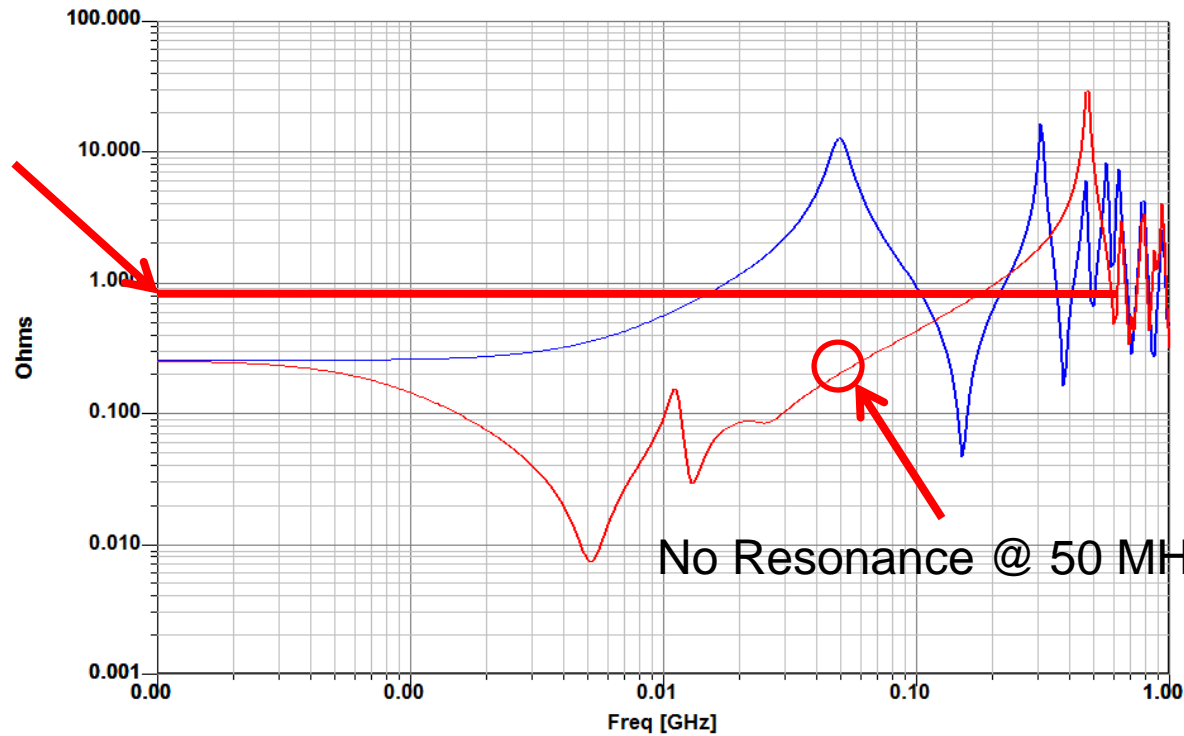

Board w/
Bulk Caps
Board w/
HF Caps 1

No Resonance @ 50 MHz




HF Capacitors 1

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:16:08


Target
impedance 800
mOhm to 667
MHz

 


Board w/
HF Caps 1




PDS Design Flow

 

Switching Power Noise

 


PDS Design Flow

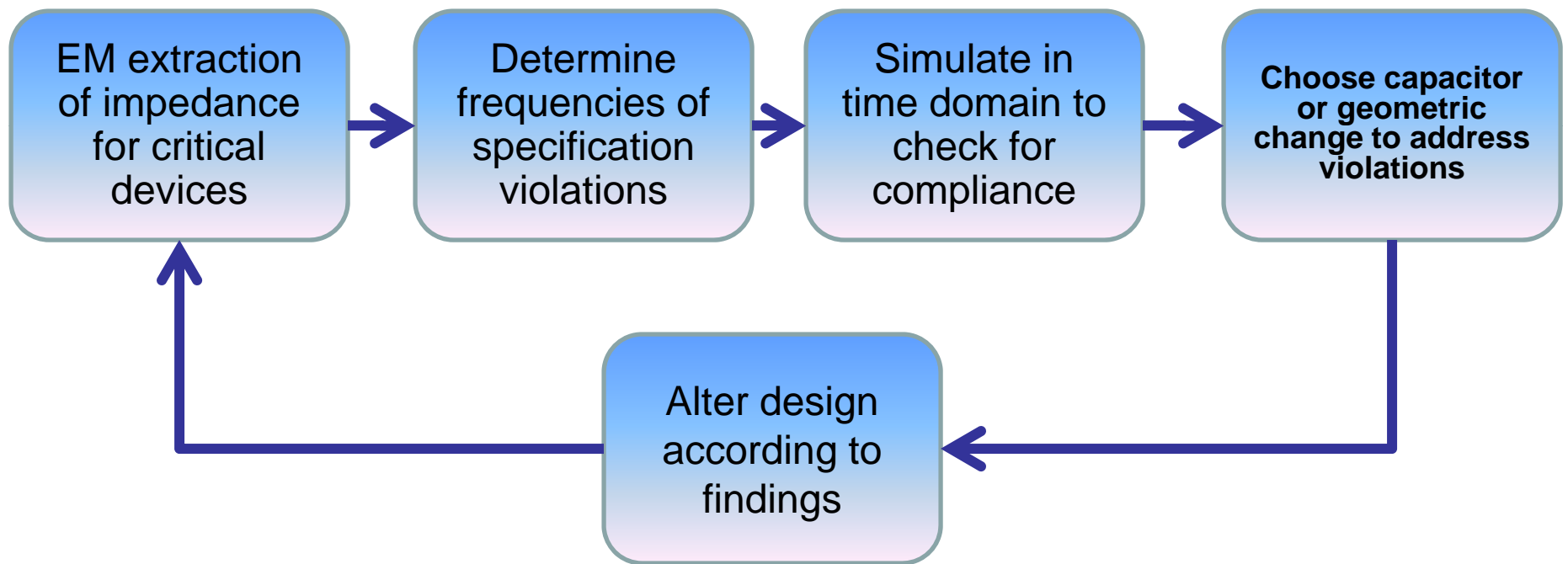


Extending Low Impedance

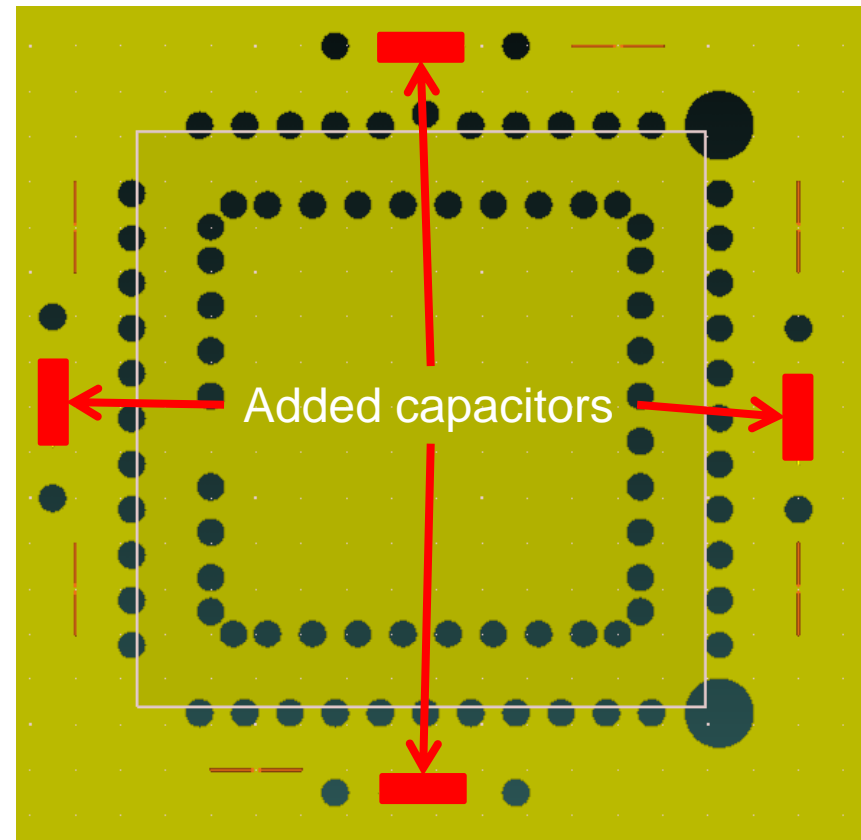- 10 1.2 nF capacitors were added across the board to extend minimum high-frequency impedance
- 1.2 nF capacitor was chosen due to low impedance at 200 MHz
- 4 of these were located near U41



PDS Design Flow

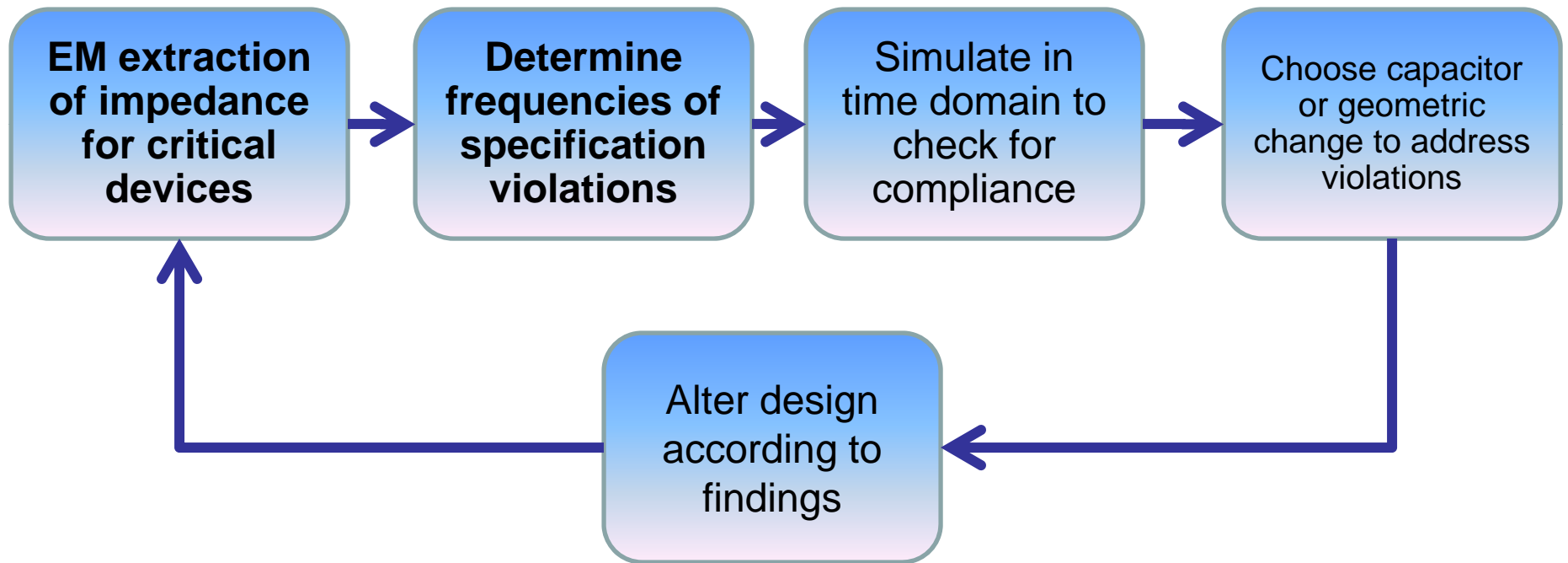


HF 1 vs. HF 2

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:17:25

Target
impedance 800
mOhm to 667
MHz

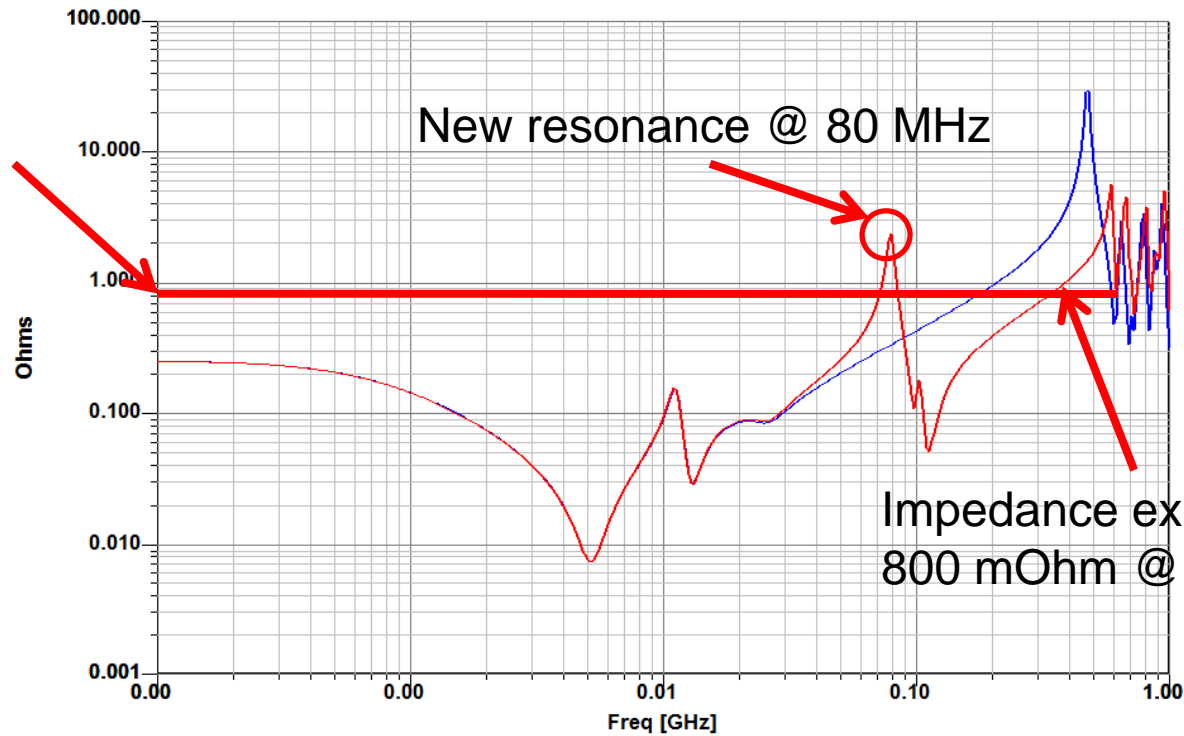

Board w/
HF Caps 1
Board w/
HF Caps 2




HF 2

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:18:05


Target
impedance 800
mOhm to 667
MHz

 


Board w/
HF Caps 2




PDS Design Flow

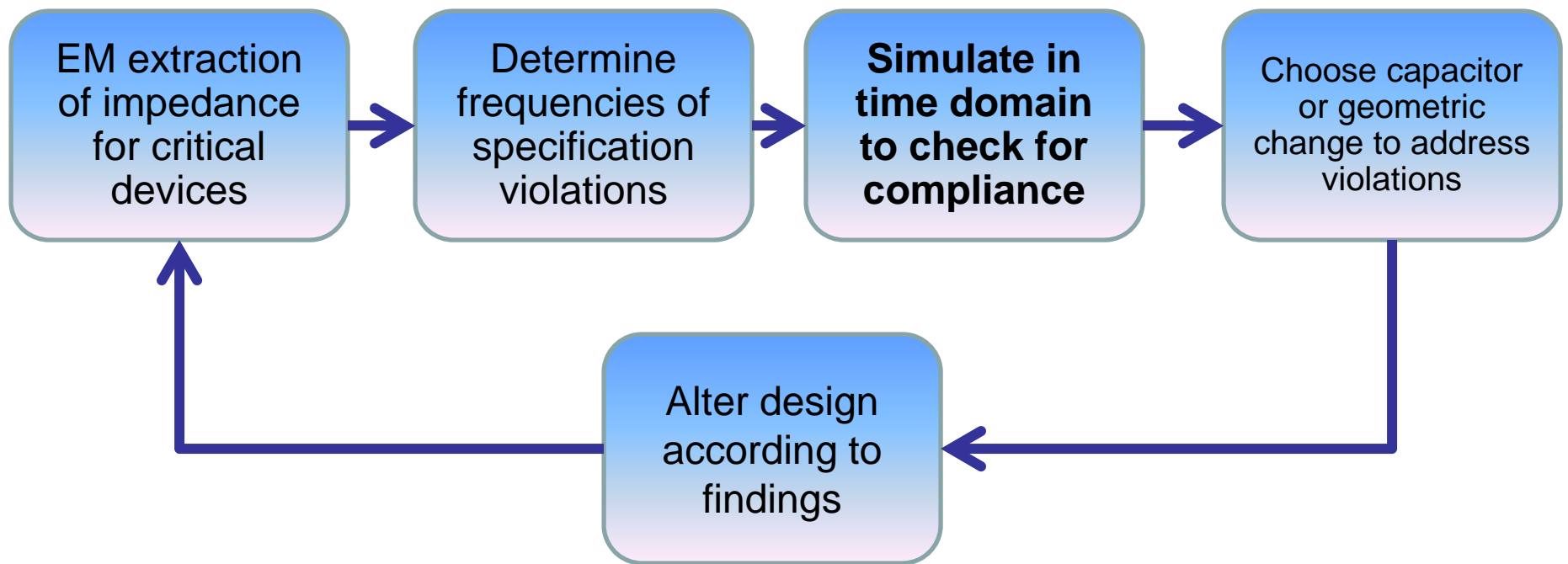


Switching Power Noise

 

Resonance at 80 MHz

 


PDS Design Flow

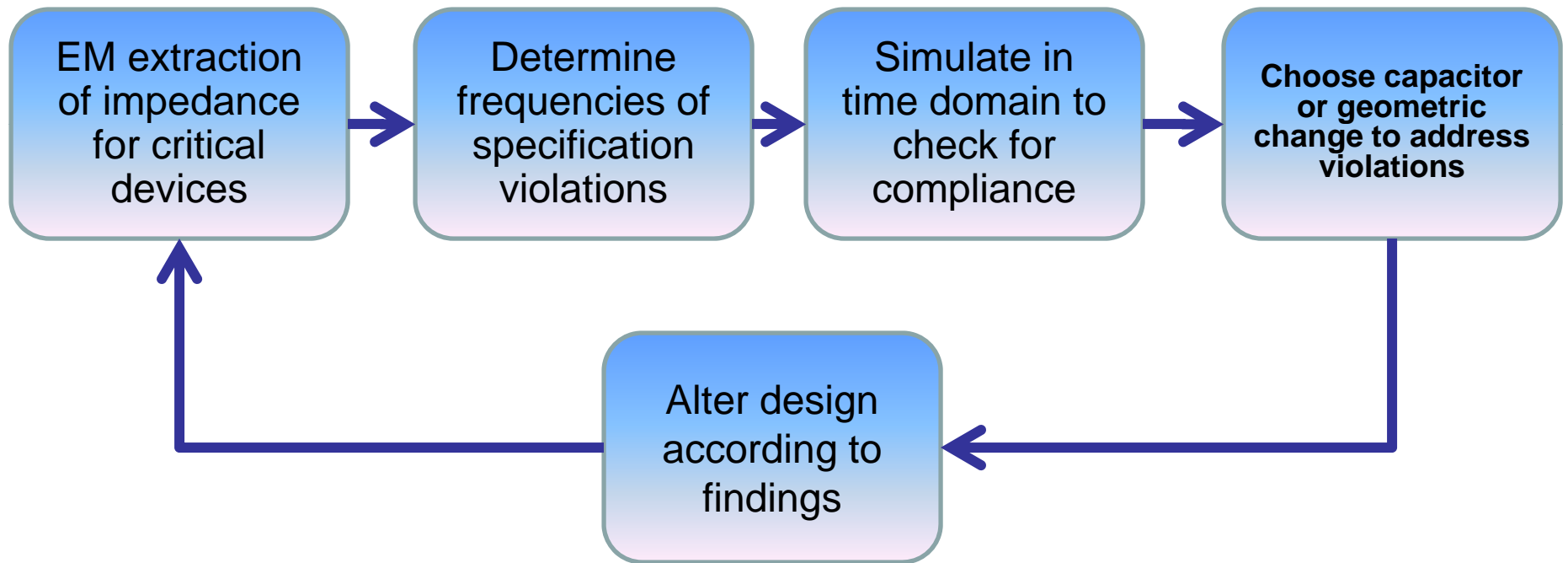

Removing a Resonance

 - Six 8 nF capacitors were added near U41 to cancel resonance at 80 MHz




Choosing a Capacitor

- To reduce the effect of a resonance, choose a capacitor with a low impedance at the resonant frequency


28 May 2008

Ansoft Corporation
08055C822KA Z Parameter Magnitude Plot
0805

10:02:58

 

PDS Design Flow

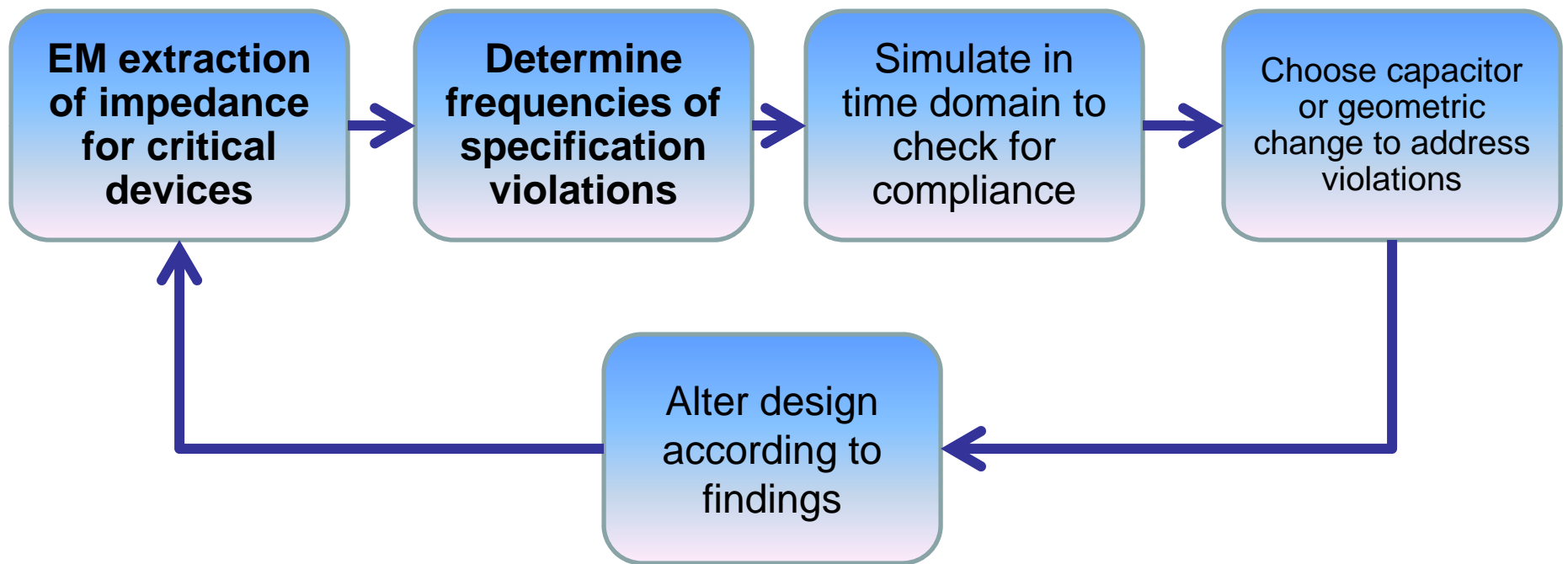


HF 2 vs. HF 3

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:19:32

Target
impedance 800
mOhm to 667
MHz

 

Board w/
HF Caps 2
Board w/
HF Caps 3

Impedance crosses
800 mOhm @ 500
MHz

No resonance @ 80 MHz




HF 3

29 Apr 2008

Ansoft Corporation
U41 Impedance
power_integrity

10:20:27


Target
impedance 800
mOhm to 667
MHz

 


Board w/
HF Caps 3




PDS Design Flow

 

Switching Power Noise

 

PDS Design Flow

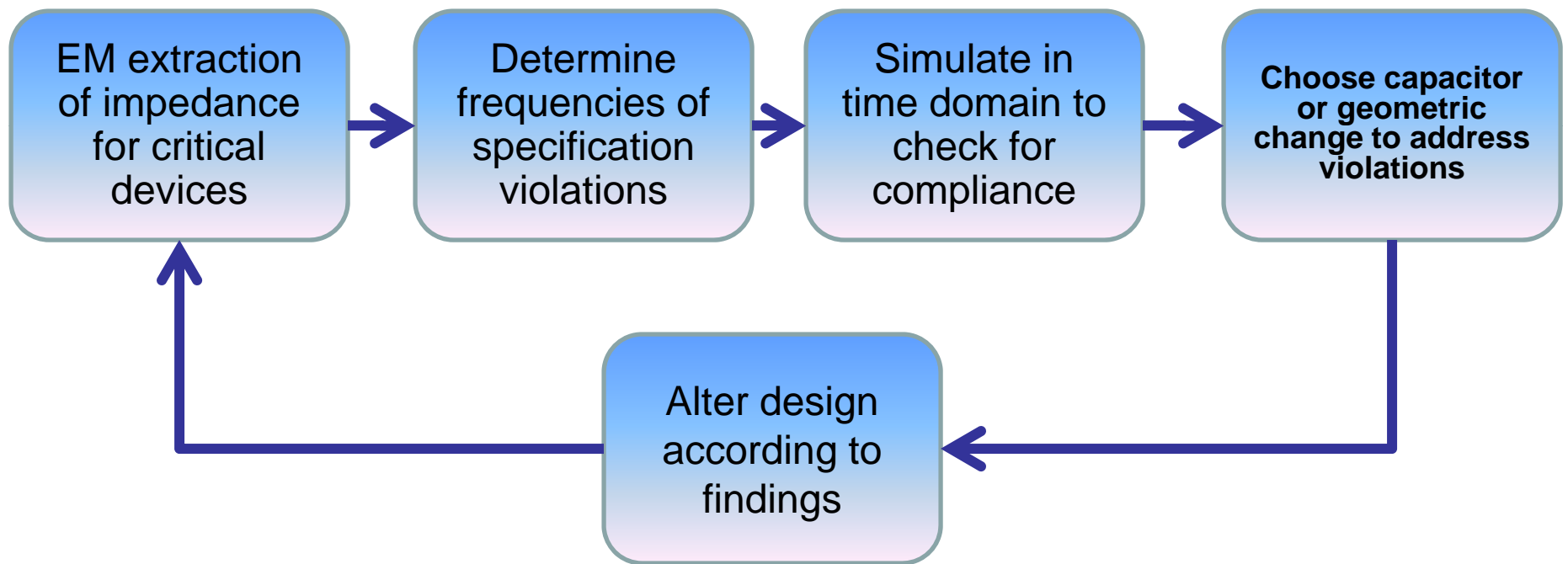


Buried Capacitance


- Due to parasitic inductance it will be impossible to further decouple the board with capacitors
- Using a thinner dielectric layer between power and ground planes introduces additional capacitance and reduces high frequency impedance

Capacitance of parallel plates:

$$C = \epsilon \frac{A}{d}$$

 

PDS Design Flow

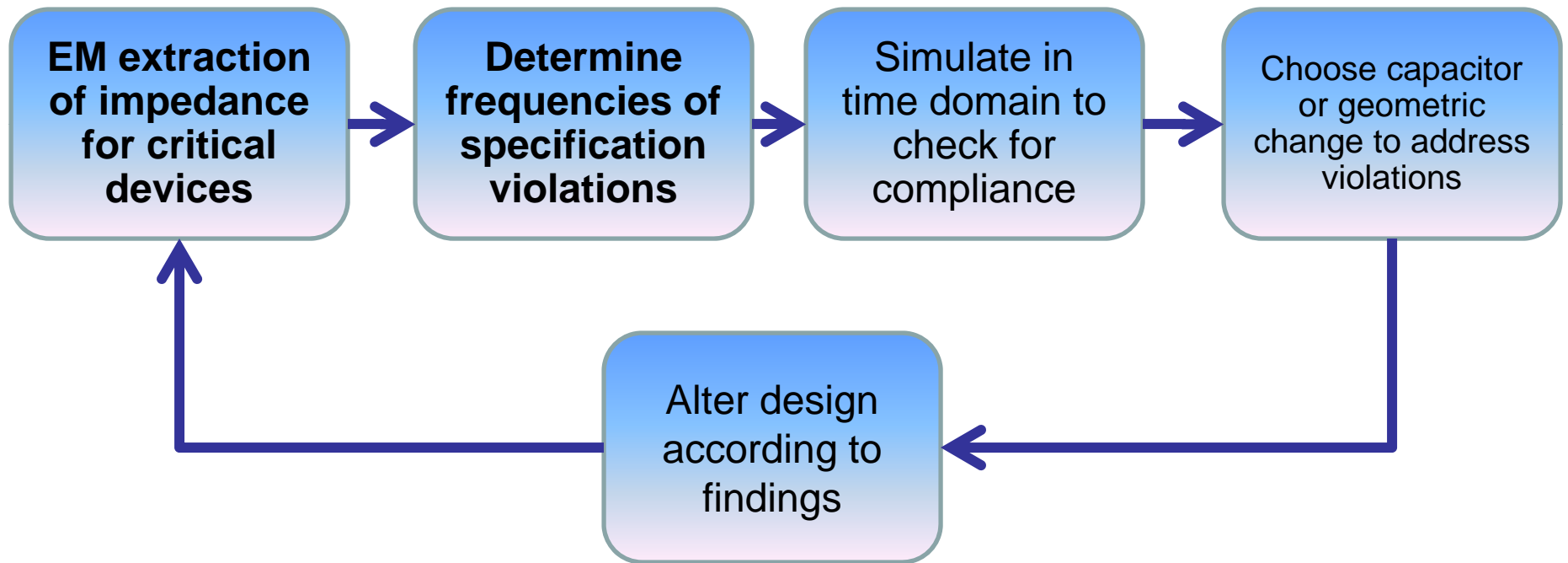


HF 3 vs. Buried Capacitance

03 Jun 2008

Ansoft Corporation
U41 Impedance
power_integrity_buriedcap2

14:10:36

Target
impedance 800
mOhm to 667
MHz

 

Board w/
HF Caps 3
Board w/
Buried
Capacitance




Buried Capacitance

03 Jun 2008

Ansoft Corporation
U41 Impedance
power_integrity_buriedcap2

14:13:00


Target
impedance 800
mOhm to 667
MHz

 


Board w/
Buried
Capacitance



PDS Design Flow

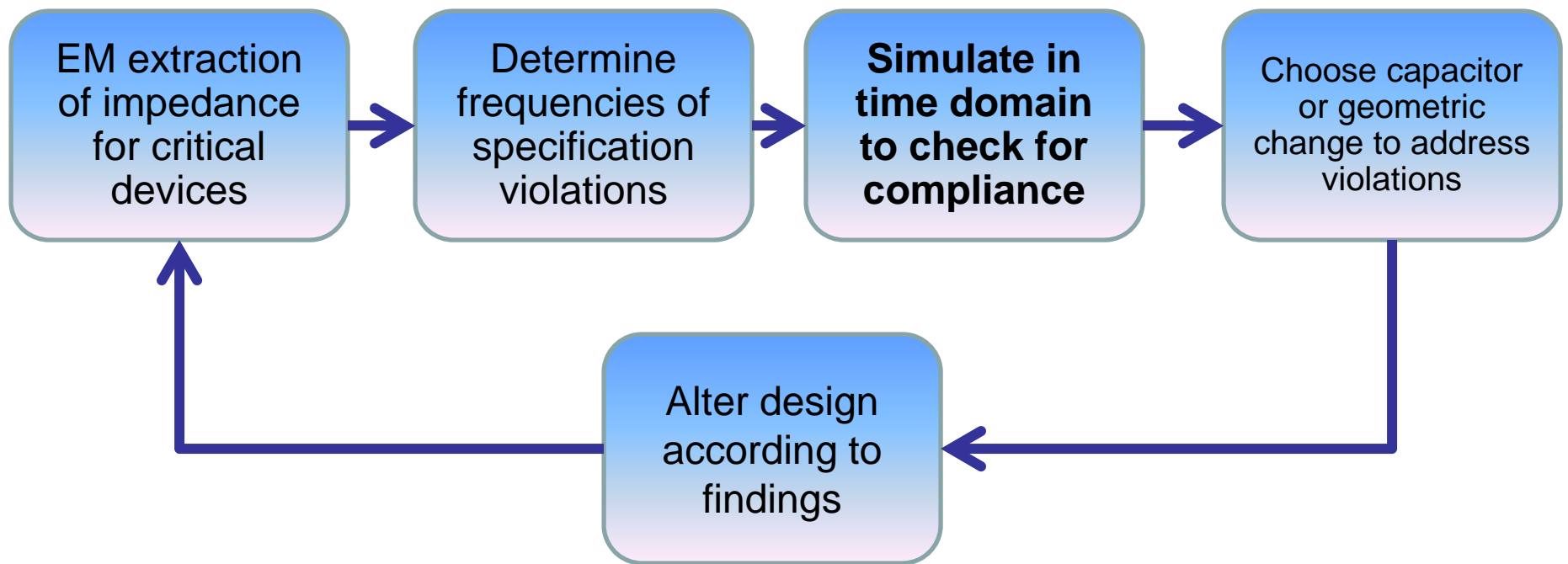

Switching Power Noise

 

Conclusion

- Ansoft software allows PCB engineers to design effective decoupling solutions for their PCBs
- Impedance and resonant mode simulations connect the frequency domain to the spatial domain and allow selection of capacitor value and placement
- *Frequency domain* extractions are useful for quickly optimizing PDS designs, but *time domain* simulations are necessary to ensure compliance with device specs

